

---

COMP 303

Computer Architecture

Lecture 5

---



# Unsigned Binary Integers

- Unsigned binary numbers are typically used to represent computer addresses or other values that are guaranteed not to be negative.
- An n-bit unsigned binary integer  $A = a_{n-1} a_{n-2} \dots a_1 a_0$  has a value of

$$\sum_{i=0}^{n-1} a_i \cdot 2^i$$

- What is 1011 as an unsigned integer?
- An n-bit unsigned binary integer has a range from 0 to  $2^n - 1$ .
- What is the value of the 8-bit unsigned integer 10000001?



# Signed Binary Integers

- Signed binary numbers are typically used to represent data that is either positive or negative.
- The most common representation for signed binary integers is the two's complement format.
- An n-bit 2's comp. binary integer  $A = a_{n-1} a_{n-2} \dots a_1 a_0$  has a value of

$$-a_{n-1} \cdot 2^{n-1} + \sum_{i=0}^{n-2} a_i \cdot 2^i$$

- What is 1011 as a 2's comp. integer?
- An n-bit 2's comp. binary integer has a range from  $-2^{n-1}$  to  $2^{n-1} - 1$ .
- What is the value of the 2's comp. Integer 10000001?



# Two's Complement Negation

- To negate a two's complement integer, invert all the bits and add a one to the least significant bit.
- What are the two's complements of

$$\begin{array}{r} 6 = 0110 \longrightarrow 1001 \\ + \quad 1 \\ \hline 1010 = -6 \end{array}$$

$$\begin{array}{r} -4 = 1100 \longrightarrow 0011 \\ + \quad 1 \\ \hline 0100 = 4 \end{array}$$

- What is the value of the two's complement integer 11111111111111101 in decimal?
- What is the value of the unsigned integer 11111111111111101 in decimal?



# Two's Complement Addition

- To add two's complement numbers, add the corresponding bits of both numbers with carry between bits.

- For example,

3 = 0011	-3 = 1101	-3 = 1101	3 = 0011
+ 2 = 0010	+ -2 = 1110	+ 2 = 0010	+ -2 = 1110
<hr/>	<hr/>	<hr/>	<hr/>
5 = 0101	-5 = 1011	-1 = 1111	1 = 0001

- Unsigned and two's complement addition are performed exactly the same way, but how they detect overflow differs.



# Two's Complement Subtraction

- To subtract two's complement numbers we first negate the second number and then add the corresponding bits of both numbers.

- For example:

$$\begin{array}{r} 3 = 0011 \\ - 2 = 0010 \\ \hline \end{array}$$



$$\begin{array}{r} 3 = 0011 \\ + -2 = 1110 \\ \hline 1 = 0001 \end{array}$$



# Overflow

- When adding or subtracting numbers, the sum or difference can go beyond the range of representable numbers.
- This is known as overflow. For example, for two's complement numbers,

5 = 0101	-5 = 1011	5 = 0101	-5 = 1011
+ 6 = 0110	+ -6 = 1010	- -6 = 1010	- +6 = 0110
-----	-----	-----	-----
-5 = 1011	5 = 0101	-5 = 1011	5 = 0101

- Overflow creates an incorrect result that should be detected.



# 2's Comp - Detecting Overflow

- When adding two's complement numbers, overflow will only occur if
  - the numbers being added have the same sign
  - the sign of the result is different

- If we perform the addition

$$\begin{array}{r} a_{n-1} a_{n-2} \dots a_1 a_0 \\ + b_{n-1} b_{n-2} \dots b_1 b_0 \\ \hline = s_{n-1} s_{n-2} \dots s_1 s_0 \end{array}$$

- Overflow can be detected as

$$V = a_{n-1} \cdot b_{n-1} \cdot \overline{s_{n-1}} + \overline{a_{n-1}} \cdot \overline{b_{n-1}} \cdot s_{n-1}$$

- Overflow can also be detected as

$$V = c_n \otimes c_{n-1}, \text{ where } c_{n-1} \text{ and } c_n \text{ are the carry in and carry out of the most significant bit.}$$



# Unsigned - Detecting Overflow

- For unsigned numbers, overflow occurs if there is carry out of the most significant bit.

$$V = c_n$$

- For example,

$$\begin{array}{r} 1001 = 9 \\ + 1000 = 8 \\ \hline 0001 = 1 \end{array}$$

- With the MIPS architecture
  - Overflow exceptions occur for two's complement arithmetic
    - add, sub, addi
  - Overflow exceptions do not occur for unsigned arithmetic
    - addu, subu, addiu



# Shift Operations

- The MIPS architecture defines various shift operations:

(a) `sll r1, r2, 3`      `r2 = 10101100`      (shift left logical)

`r1 = 01100000`

- shift in zeros to the least significant bits

(b) `srl r1, r2, 3`      `r2 = 10101100`      (shift right logical)

`r1 = 00010101`

- shift in zeros to the most significant bits

(c) `sra r1, r2, 3`      `r2 = 10101100`      (shift right arithmetic)

`r1 = 11110101`

- copy the sign bit to the most significant bits

- There are also versions of these instructions that take three register operands.



# Logical Operations

- In the MIPS architecture logical operations (and, or, xor) correspond to bit-wise operations.

(a) and r1, r2, r3      r3 = 1010      (r1 is 1 if r2 and r3 are both one)

                         r2 = 0110

                         r1 = 0010

(b) or r1, r2, r3      r3 = 1010      (r1 is 1 if r2 or r3 is one)

                         r2 = 0110

                         r1 = 1110

(c) xor r1, r2, r3      r3 = 1010      (r1 is 1 if r2 and r3 are different)

                         r2 = 0110


                         r1 = 1100

- Immediate versions of these instructions are also supported.


 
# ALU Interface

- We will be designing a 32-bit ALU with the following interface.



**Z = 1, if Result=0**  
**V = 1, if Overflow**  
**C<sub>32</sub> = 1, if Carry-Out**

ALUOp	Function
000	AND
001	OR
010	ADD
110	SUBTRACT
111	SET-ON-LESS-THAN



# Set-on-less-than

- The set-on-less instruction

slt \$s1, \$s2, \$s3

sets \$s1 to '1' if ( $\$s2 < \$s3$ ) and to '0' otherwise.

- This can be accomplished by

- subtracting \$s3 from \$s2
- setting the least significant bit to the sign bit of the result
- setting all other bits to zero
- if overflow occurs the sign bit needs to be inverted

- For example,


$$\begin{array}{r} \$s2 = 1010 \\ -\$s3 = \underline{1011} \\ \hline = 1111 \\ \$s1 = 0001 \end{array}$$
$$\begin{array}{r} \$s2 = 0111 \\ -\$s3 = \underline{0100} \\ \hline = 0011 \\ \$s1 = 0000 \end{array}$$



# Full Adder

- A fundamental building block in the ALU is a full adder (FA).
- A FA performs a one bit addition.

$$a_i + b_i + c_i = 2c_{i+1} + s_i$$

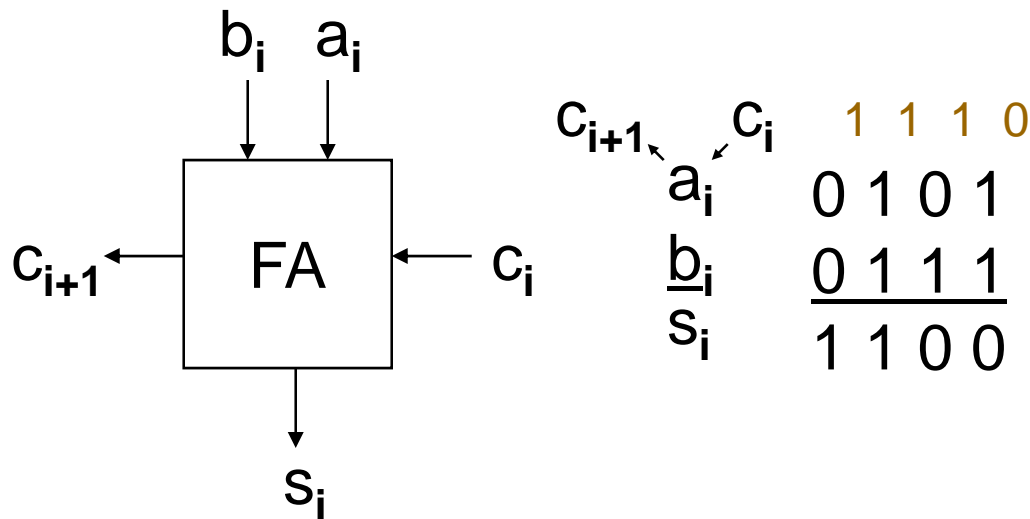



# Full Adder Logic Equations

- $s_i$  is '1' if an odd number of inputs are '1'.
- $c_{i+1}$  is '1' if two or more inputs are '1'.

$a_i$	$b_i$	$c_i$	$c_{i+1}$	$s_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$s_i = \bar{a}_i \bar{b}_i c_i + \bar{a}_i b_i \bar{c}_i + a_i \bar{b}_i \bar{c}_i + a_i b_i c_i$$

$$s_i = a_i \otimes b_i \otimes c_i$$

$$c_{i+1} = \bar{a}_i b_i c_i + a_i \bar{b}_i c_i + a_i b_i \bar{c}_i + a_i b_i c_i$$

$$c_{i+1} = a_i b_i + a_i c_i + b_i c_i$$

$$c_{i+1} = a_i b_i + c_i(a_i + b_i)$$

$$c_{i+1} = a_i b_i + c_i(a_i \otimes b_i)$$




# Full Adder Design

- One possible implementation of a full adder uses nine gates.

$$s_i = a_i \oplus b_i \oplus c_i$$

$$c_{i+1} = a_i b_i + c_i(a_i \oplus b_i)$$

 
$$a_i \oplus b_i = (a_i + b_i) \overline{a_i b_i}$$





 
# 1-Bit ALU

- The full adder, an xor gate, and a 4-to-1 mux are combined to form a 1-bit ALU.



ALUOp	Function
000	AND
001	OR
010	ADD
110	SUBTRACT
111	SET-ON-LESS-THAN

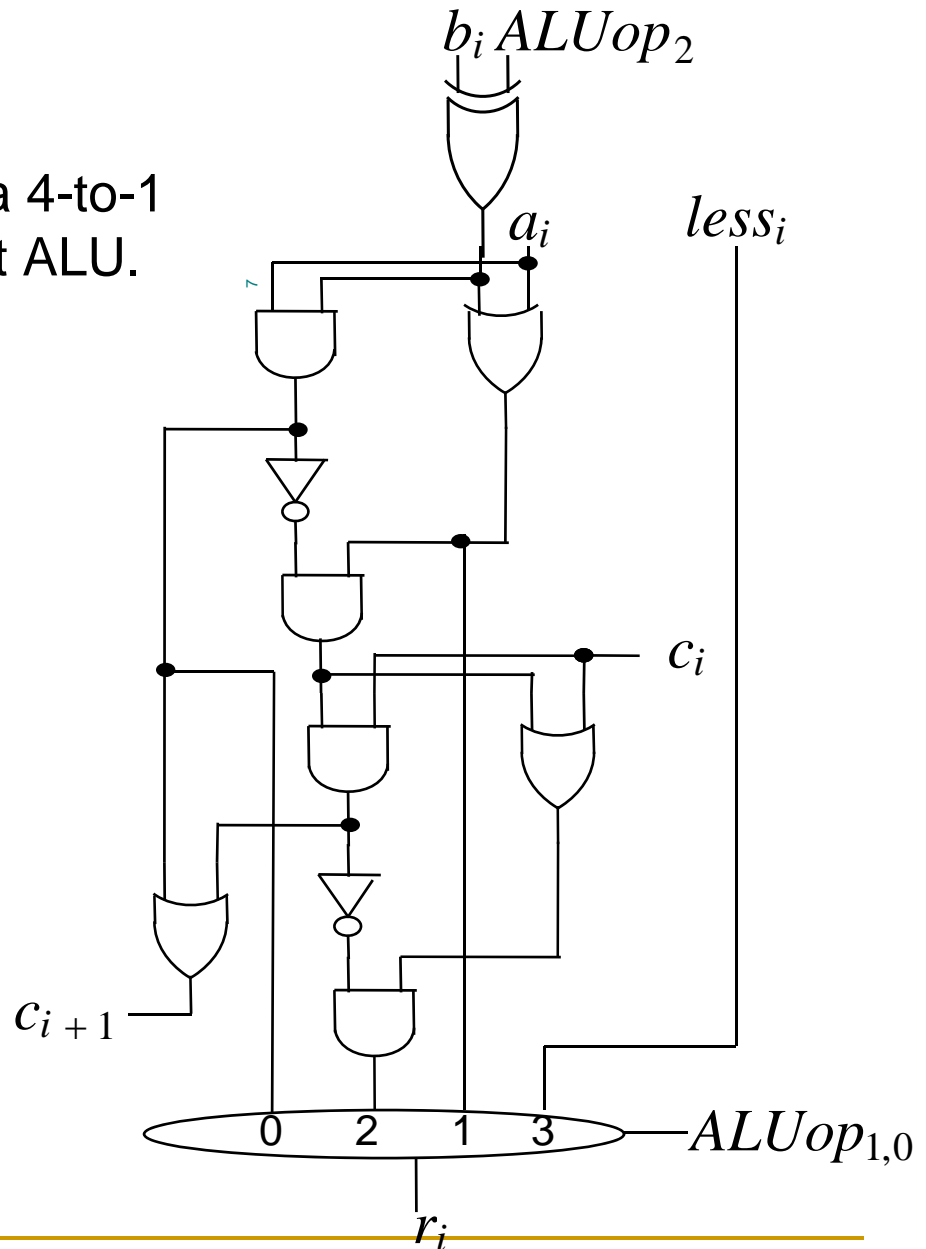




# 1-bit ALU for MSB

- The ALU for the MSB must also detect overflow and indicate the sign of the result.

$$V = c_n \otimes c_{n-1}$$


$$set = (A < B)$$

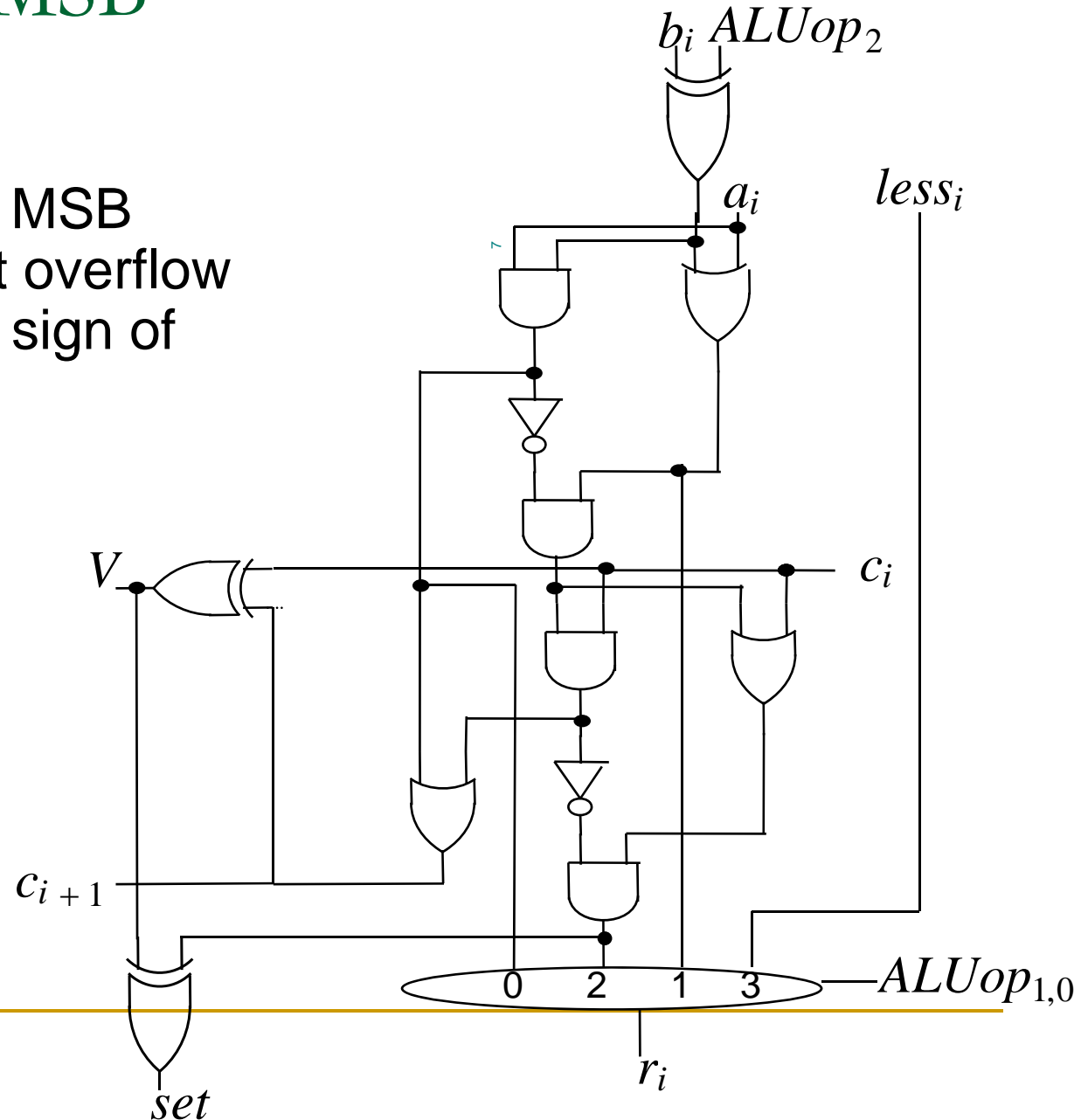


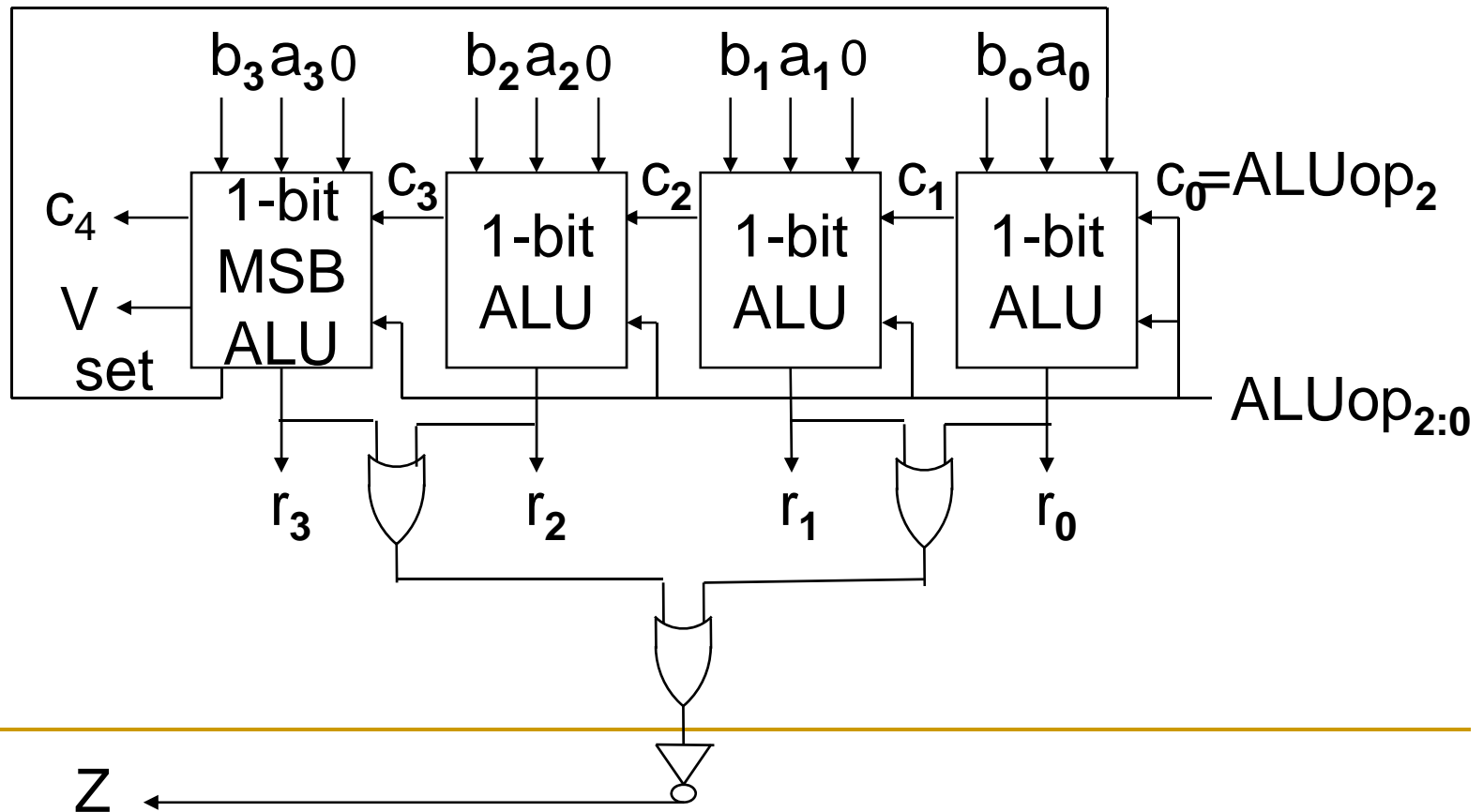
# Larger ALUs

- Three 1-bit ALUs, a 1-bit MSB ALU, and a 4-input NOR gate can be concatenated to form a 4-bit ALU.





# Gate Counts


## ■ Assume

- 4-input mux = 5 gates
- XOR gate = 3 gates
- AND/OR gate = 1 gate
- Inverter = 0.5 gates.

## ■ How many gates are required by

- A 1-bit ALU?
- A 4-bit ALU?
- A 32-bit ALU?
- An n-bit ALU?

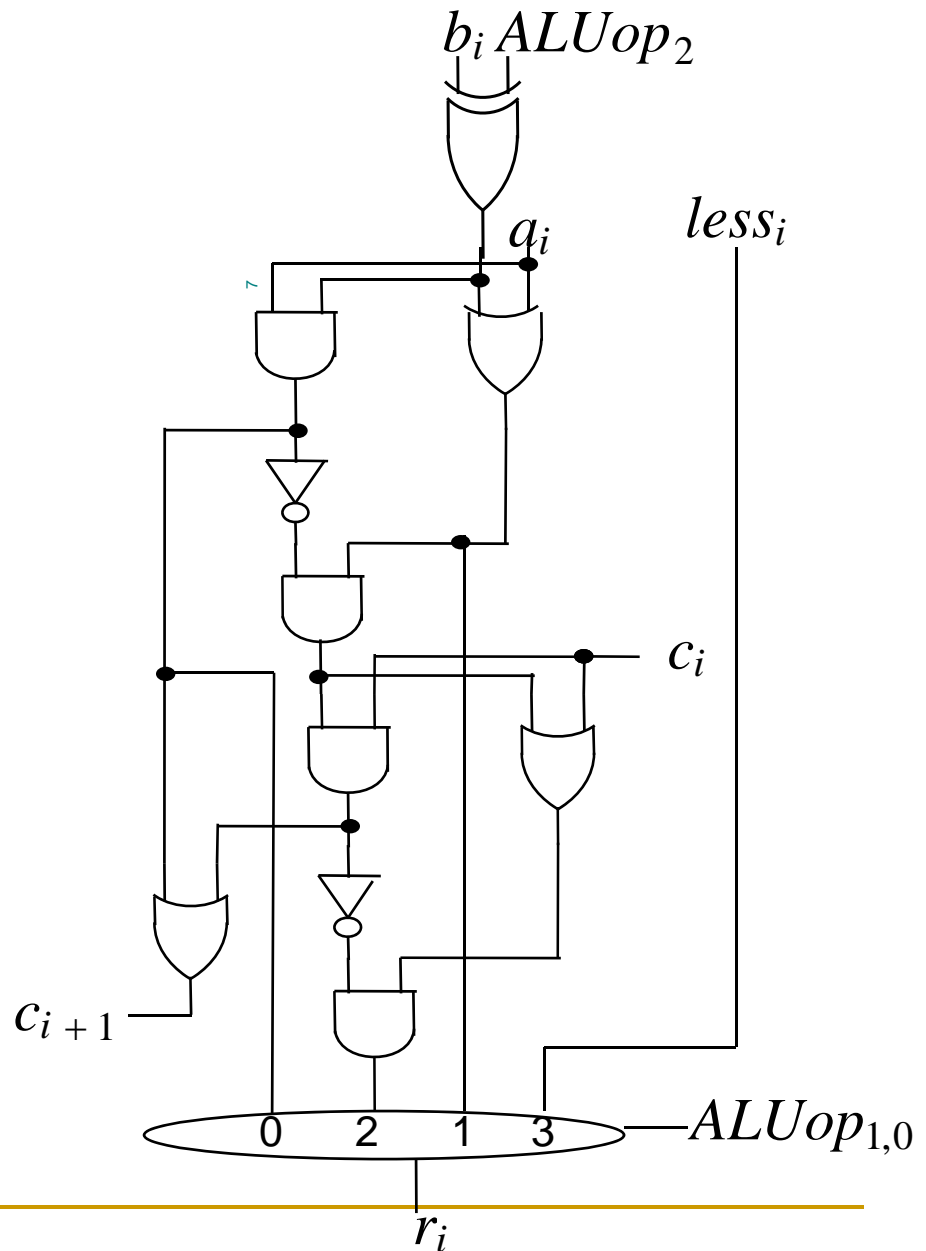
## ■ Additional gates needed to compute V and Z




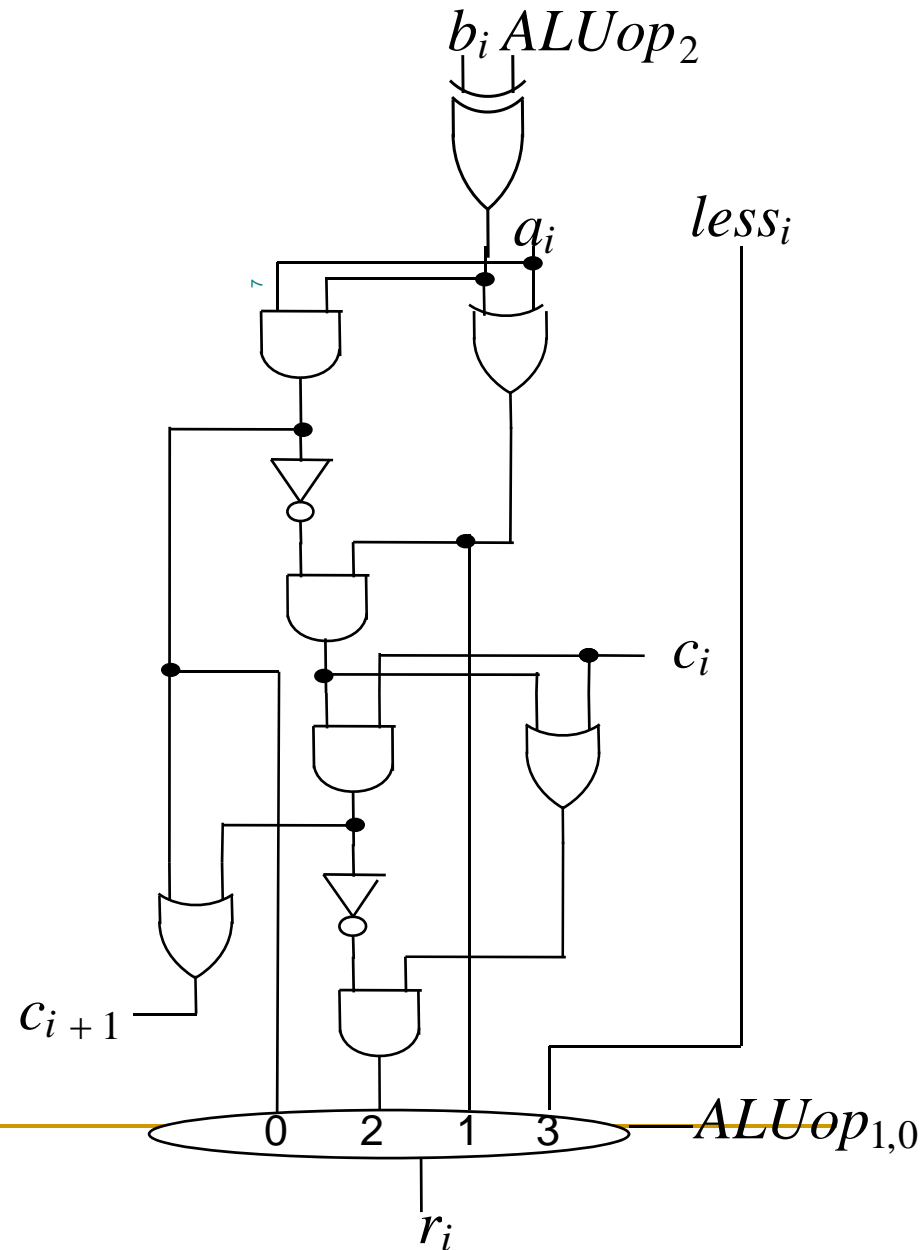
# Gate Counts


- Assume
  - 4-input mux = 5 gates
  - XOR gate = 3 gates
  - AND/OR gate = 1 gate
  - Inverter = 0.5 gates.
- How many gates are required by
  - A 1-bit ALU? 16
  - A 4-bit ALU? 16x4
  - A 32-bit ALU? 16x32
  - An n-bit ALU? 16xn
- (n-1) 2-input OR gates, 1 inverter and 1 XOR gate are needed to compute V and Z for an n-bit ALU




 
# Gate Delays


- Assume delays of
  - 4-input mux =  $2t$
  - XOR gate =  $2t$
  - AND/OR gate =  $1t$
  - Inverter =  $1t$
- What is the delay of
  - A 1-bit ALU?
  - A 4-bit ALU?
  - A 32-bit ALU?
  - An  $n$ -bit ALU?
- Additional delay needed to compute  $Z$




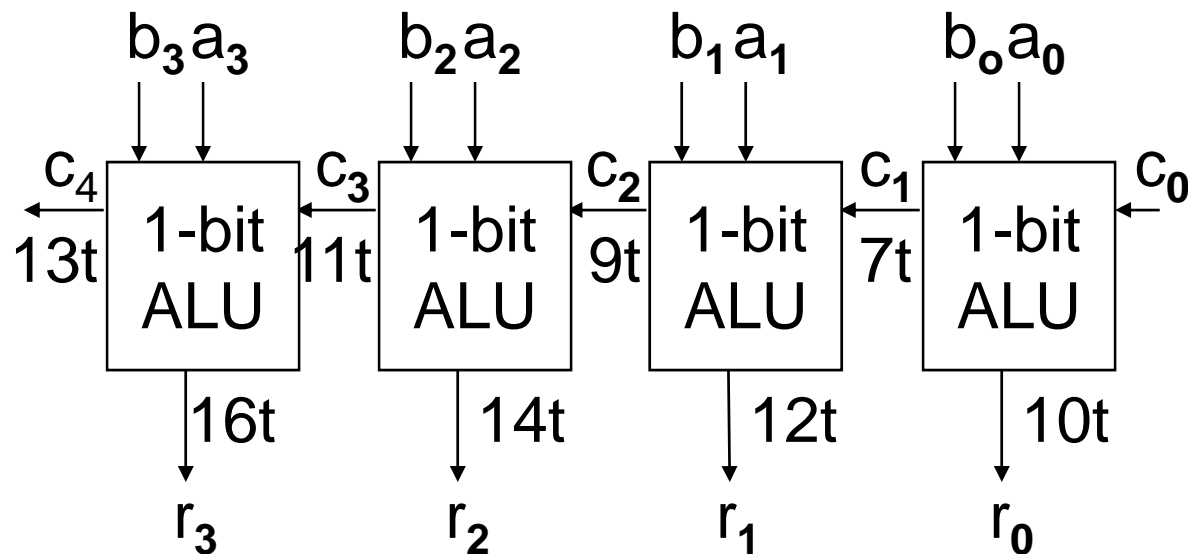
# Ripple Carry Adder (RCA)

- With the previous design the carry “rippled” from one 1-bit ALU to the next.




- These leads to a relatively slow design.
- Z is ready at 19 t


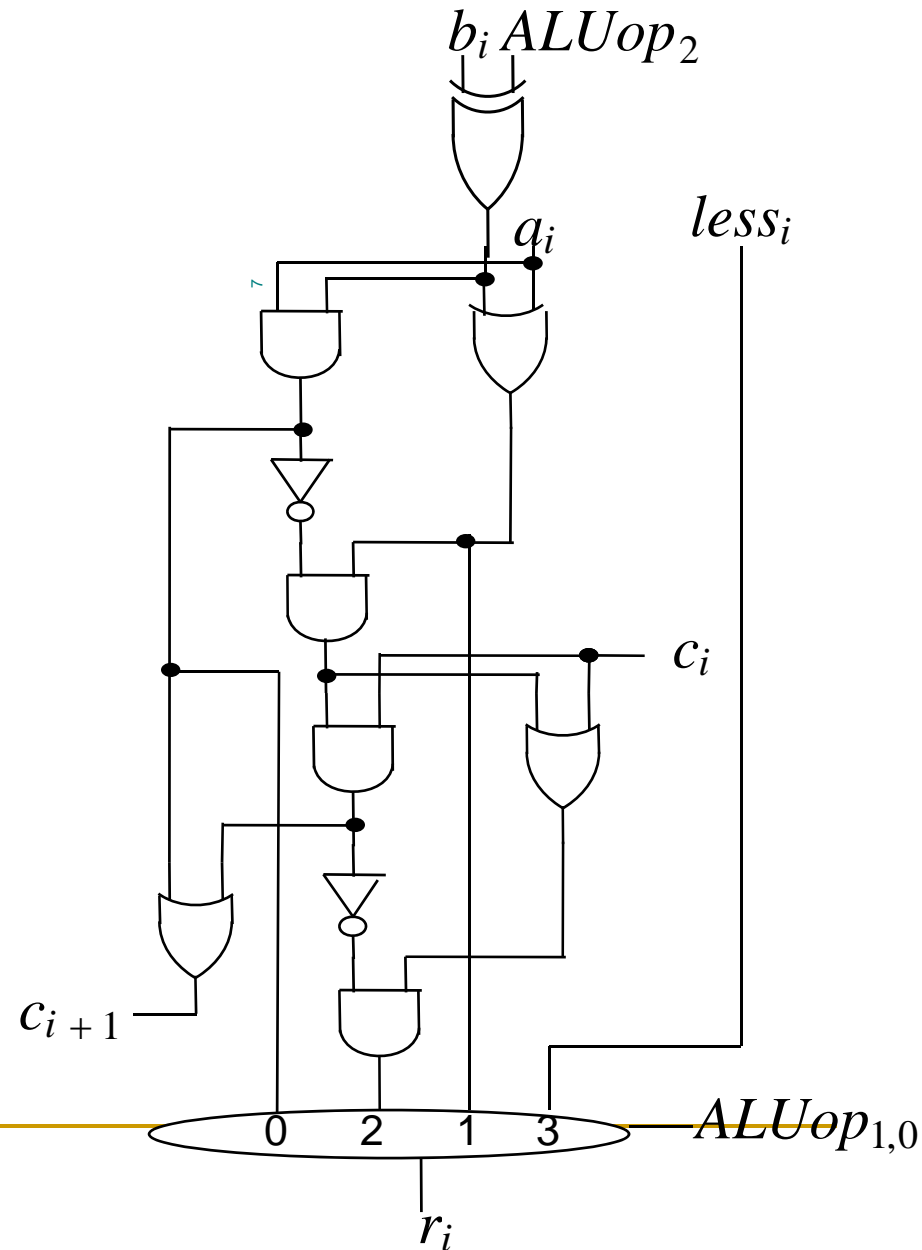
# Gate Delays


- Assume delays of
  - 4-input mux =  $2t$
  - XOR gate =  $2t$
  - AND/OR gate =  $1t$
  - Inverter =  $1t$
- What is the delay of
  - A 1-bit ALU?  $10t$
  - A 4-bit ALU?  $16t$
  - A 32-bit ALU?  $(2 \times 32 + 8)t = 72t$
  - An  $n$ -bit ALU?  $(2n + 8)t$
- $\lceil \log_2(n) \rceil$  levels of 2-input OR gates and 1 inverter are needed to compute  $Z$ .




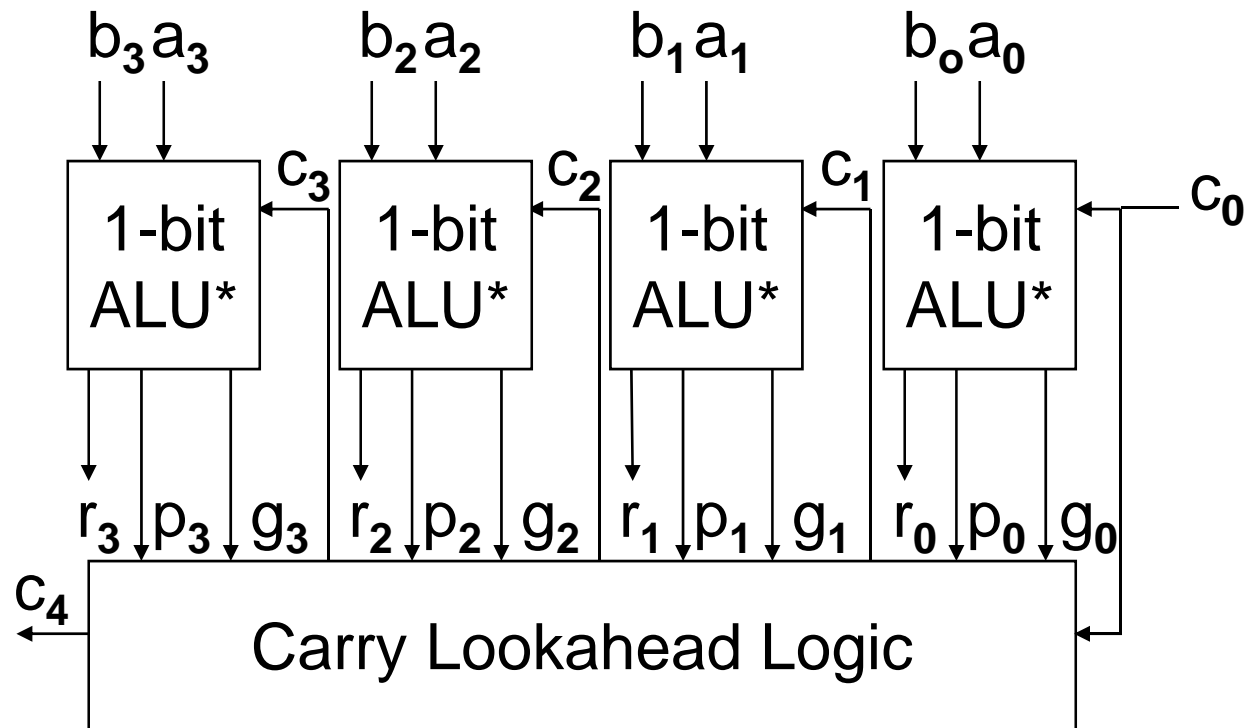
# Carry Lookahead Adder (CLA)

- With a CLA, the carries are computed in parallel using carry lookahead logic (CLL).





# Carry Logic Equation

- The carry logic equation is

$$c_{i+1} = a_i b_i + (a_i + b_i) c_i$$

- We define a propagate signal

$$p_i = a_i + b_i$$

and a generate signal

$$g_i = a_i b_i$$

- This allows the carry logic equation to be rewritten as

$$c_{i+1} = g_i + p_i c_i$$



# Carry Lookahead Logic

- For a 4-bit carry lookahead adder, the carries are computed as

$$c_1 = g_0 + p_0c_0$$

$$c_2 = g_1 + p_1c_1 = g_1 + p_1(g_0 + p_0c_0)$$

$$= g_1 + p_1g_0 + p_1p_0c_0$$

$$c_3 = g_2 + p_2c_2 = g_2 + p_2(g_1 + p_1g_0 + p_1p_0c_0)$$

$$= g_2 + p_2g_1 + p_2p_1g_0 + p_2p_1p_0c_0$$

$$c_4 = g_3 + p_3c_3 = g_3 + p_3(g_2 + p_2g_1 + p_2p_1g_0 + p_2p_1p_0c_0)$$


$$= g_3 + p_3g_2 + p_3p_2g_1 + p_3p_2p_1g_0 + p_3p_2p_1p_0c_0$$

- How many gates does the 4-bit CLL require, if gates can have unlimited fan-in?
- If each logic level has a delay of only  $1t$ , the CLL has a delay of  $2t$ .  $\Rightarrow$  In practice this may not be realistic.


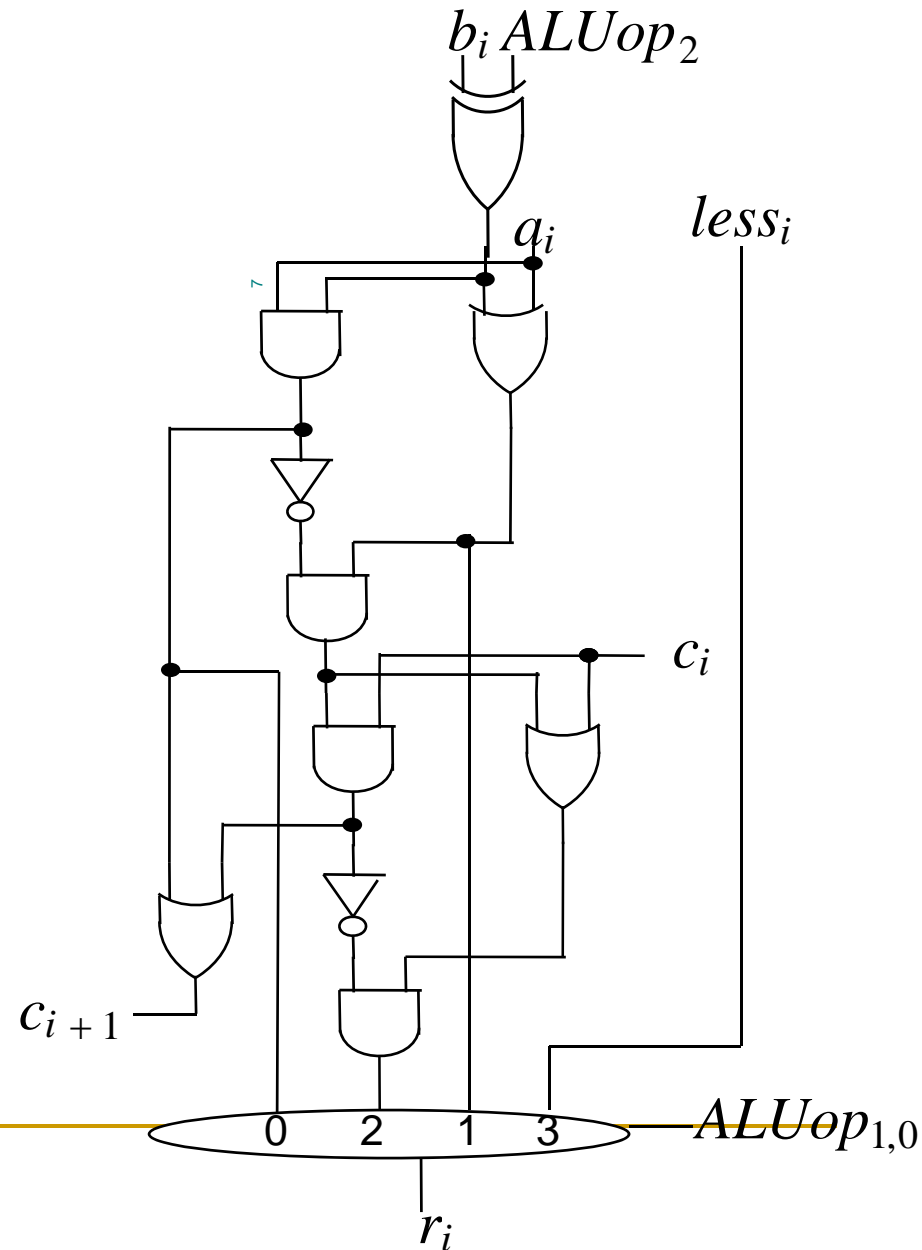
# Modifying the 1-bit ALU


- How would we modify our 1-bit ALU if it is to be used in a CLA?
- How many gates does the modified 1-bit ALU require?
- How many gates does a 4-bit CLA require?
- How many gate delays until  $p_i$  and  $g_i$  are ready?




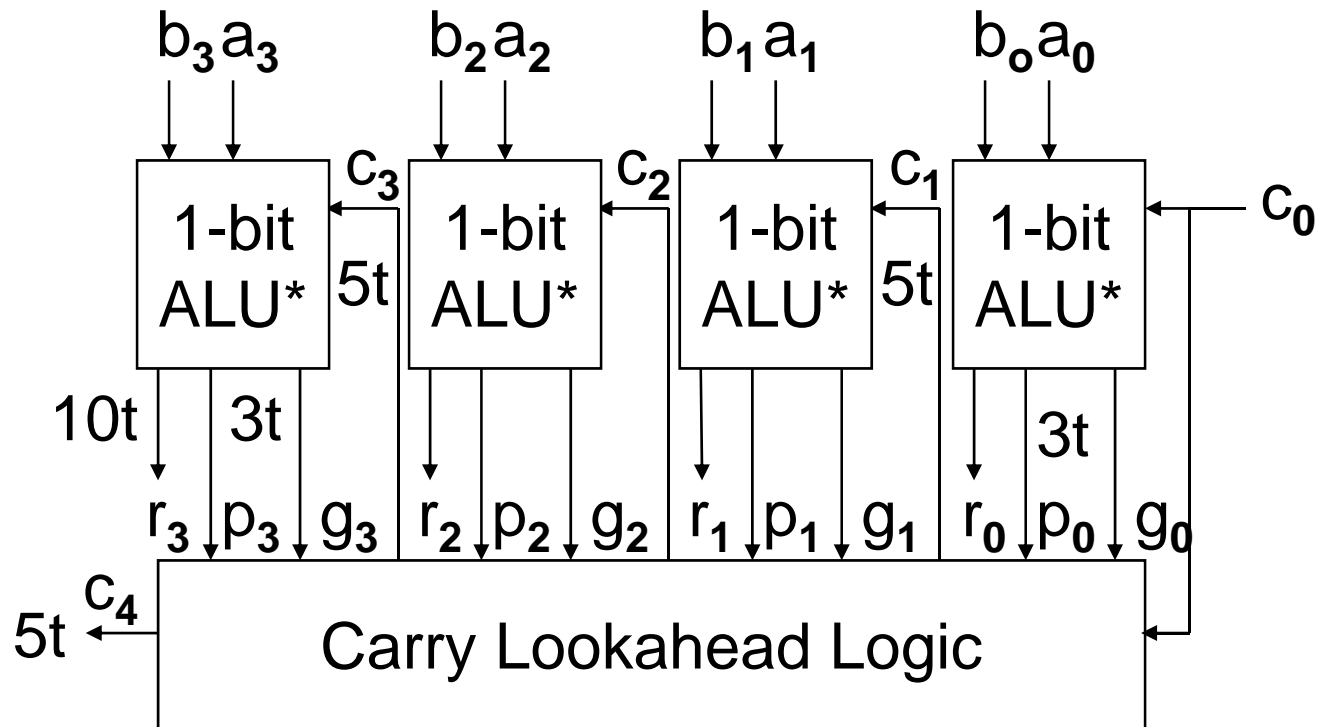
## 4-bit CLA Timing

- With a carry lookahead adder, the carries are computed in parallel using carry lookahead logic.




- This design requires  $15 \times 4 + 14 = 74$  gates, without computing V or Z


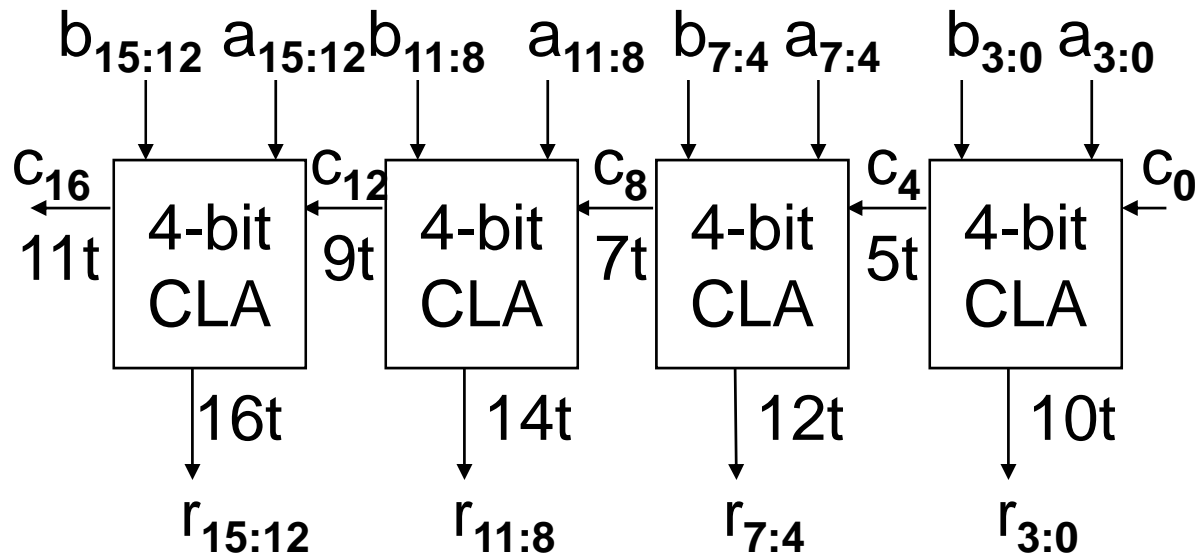
# 16-bit ALU - Version 1

- A 16-bit ALU could be constructed by concatenating four 4-bit CLAs and letting the carry “ripple” between 4-bit “blocks”.




- This design requires  $74 \times 4 = 296$  gates, without computing V or Z.


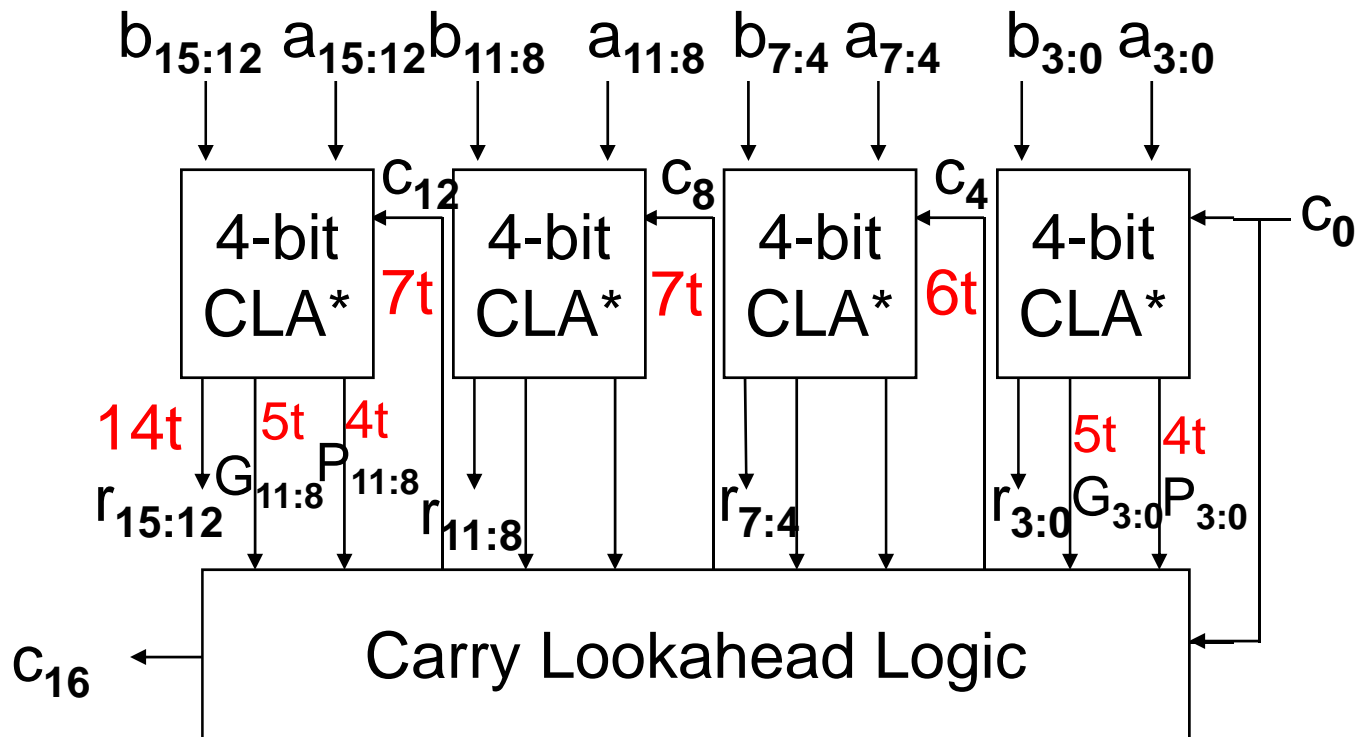
# 16-bit ALU - Version 2

- Another approach is to use a second level of carry lookahead logic.
- This approach is faster, but requires more gates  
 $16 \times 15 + 5 \times 14 = 310$  gates





## 4-bit CLA\*

- The 4-bit CLA\* (Block CLA) is similar to the first 4-bit CLA, except the CLL computes a “block” generate and “block propagate”, instead of a carry out.

- Thus the computation

$$c_4 = g_3 + p_3g_2 + p_3p_2g_1 + p_3p_2p_1g_0 + p_3p_2p_1p_0c_0$$

is replaced by

$$P_{3:0} = p_3p_2p_1p_0$$

$$G_{3:0} = g_3 + p_3g_2 + p_3p_2g_1 + p_3p_2p_1g_0$$

- Note:  $c_4 = G_{3:0} + P_{3:0}c_0$
- This approach limits the maximum fan-in to four, and the carry-lookahead logic still requires 14 gates.



---

# Conclusions

- An  $n$ -bit ALU can be designed by concatenating  $n$  1-bit ALUs.
  - Carry lookahead logic can be used to improve the speed of the computation.
  - A variety of design options exist for implementing the ALU.
  - The best design depends on area, delay, and power requirements, which vary based on the underlying technology.
-



---

# Reading assignment

- Read 3.4, 3.5