


COMP303 - Computer Architecture

Lecture 8

Designing a Single Cycle Datapath

The Big Picture

 
- The Five Classic Components of a Computer



The Big Picture: The Performance Perspective

- Performance of a machine is determined by:

 - ❑ Instruction count
- ❑ Clock cycle time
- ❑ Clock cycles per instruction




- Processor design (datapath and control) will determine:
 - ❑ Clock cycle time
 - ❑ Clock cycles per instruction
- Single cycle processor - one clock cycle per instruction
 - ❑ Advantages: Simple design, low CPI
 - ❑ Disadvantages: Long cycle time, which is limited by the slowest instruction.

How to Design a Processor: step-by-step

- Analyze instruction set => datapath requirements
 - the meaning of each instruction is given by *register transfers*
$$\mathbf{R[rd] \leftarrow R[rs] + R[rt];}$$
 - datapath must include storage element for ISA registers
 - datapath must support each register transfer
- Select set of datapath components and establish clocking methodology
- Design datapath to meet the requirements
- Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
- Design the control logic

Review: MIPS Instruction Formats

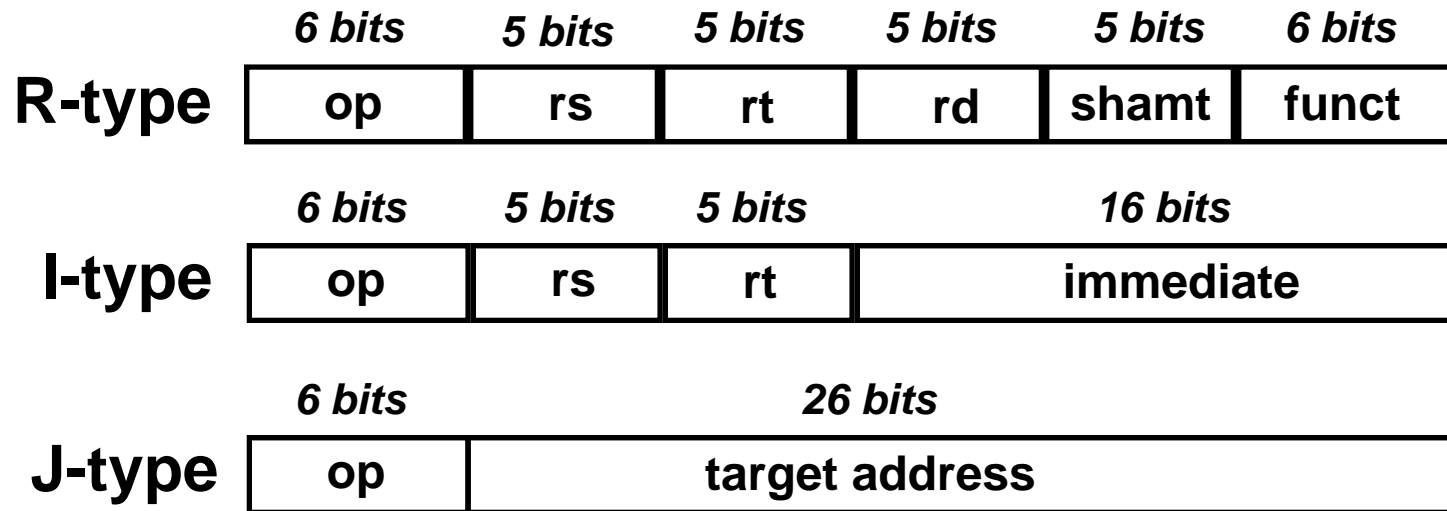- All MIPS instructions are 32 bits long. The three instruction formats are:




The different fields are:

op : basic operation of the instruction (opcode)
rs, rt, rd : source and destination register specifier
shamt : shift amount
funct : selects the variant of the operation in the "op" field
immediate : address offset or immediate value
target address : target address of the jump instruction

Step 1a: The MIPS Subset for Today


■ R-Type:

 - ❑ add rd, rs, rt
- ❑ sub rd, rs, rt
- ❑ and rd, rs, rt
- ❑ or rd, rs, rt
- ❑ slt rd, rs, rt




■ LOAD and STORE:

 - ❑ lw rt, rs, imm16
- ❑ sw rt, rs, imm16



■ BRANCH:

- ❑ beq rs, rt, imm16

 

Register Transfer Logic (RTL)

- RTL gives the meaning of the instructions
- All instructions start by fetching the instruction

op | rs | rt | rd | shamt | funct = MEM[PC]

op | rs | rt | Imm16 = MEM[PC]

inst **Register Transfers**

add $R[rd] \leftarrow R[rs] + R[rt];$ $PC \leftarrow PC + 4$

$$\text{sub} \quad \mathbf{R}[\text{rd}] \leftarrow \mathbf{R}[\text{rs}] - \mathbf{R}[\text{rt}]; \quad \mathbf{PC} \leftarrow \mathbf{PC} + 4$$

```
load    R[rt] ← MEM[ R[rs] + sign_ext(imm16)];      PC ← PC + 4
```

```
store    MEM[ R[rs] + sign_ext(imm16) ] ← R[rt];           PC ← PC + 4
```

```

beq      if ( R[rs] == R[rt] ) then PC ← PC + 4 + sign_ext(imm16) || 00
           else PC ← PC + 4


```

Step 1: Requirements of the Instruction Set


- Memory
 - instruction & data
- Registers (32 x 32)
 - read rs
 - read rt
 - write rt or rd
- PC
- Sign extender
- Add and sub register or extended immediate
- Add 4 and/or shifted extended immediate to PC

Step 2: Components of the Datapath


- Adder

 

- MUX

 

- ALU

 

**Combinational Logic:
Does not use a clock**

Storage Element: Register (Basic Building Blocks)


■ Register

□ Similar to the D Flip Flop except

- N-bit input and output
- Write enable input


□ Write Enable:

 - negated (0): Data Out will not change
- asserted (1): Data Out will become Data In on the falling edge of the clock




Storage Element: Register File


- Register File consists of 32 registers:
 - Two 32-bit output busses: busA and busB
 - One 32-bit input bus: busW
- Register is selected by:
 - RA (number) selects the register to put on busA (data)
 - RB (number) selects the register to put on busB (data)
 - RW (number) selects the register to be written via busW (data) when Write Enable is 1
- Clock input (CLK)
 - The CLK input is a factor ONLY during write operation
 - During read operation, behaves as a combinational logic block:
 - RA or RB valid => busA or busB valid after “access time.”

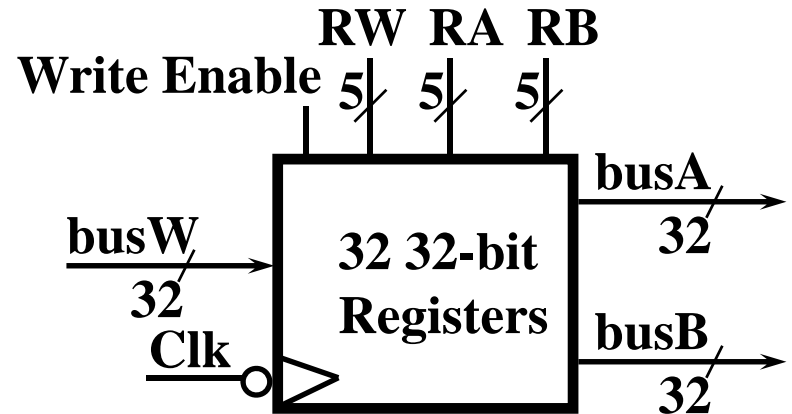

Read from Register File

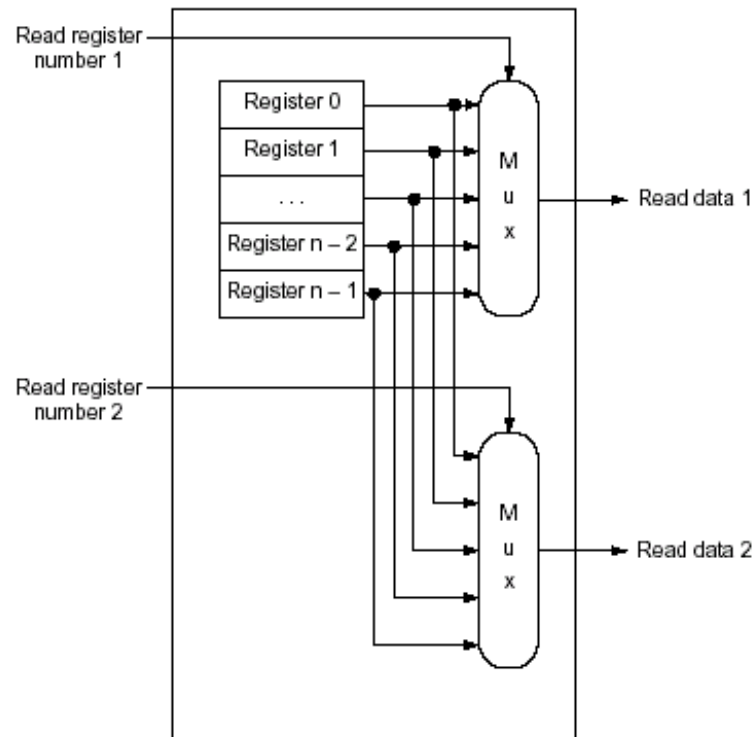

Write to Register File

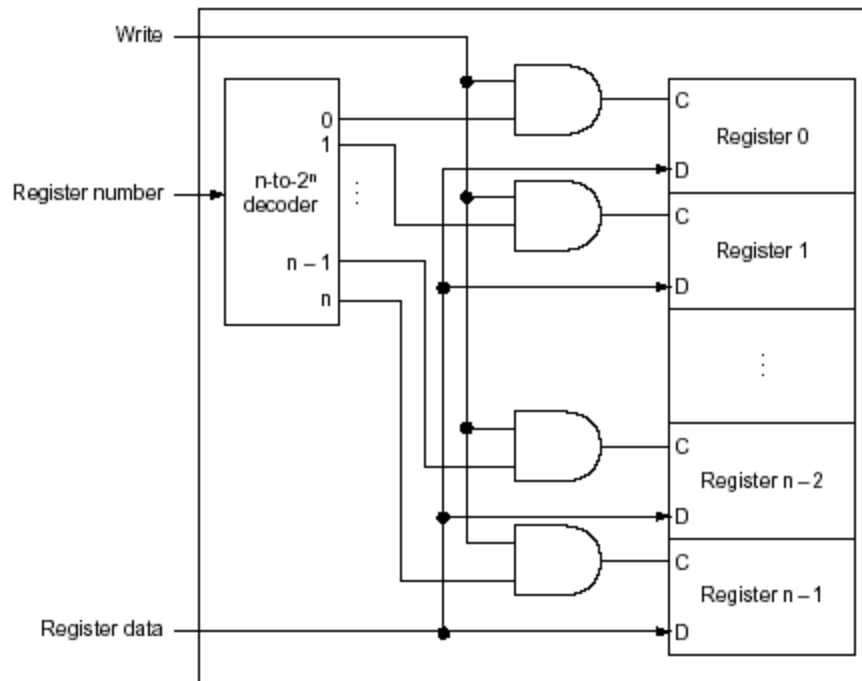

Storage Element: Memory

■ Memory


- ❑ One input bus: Data In
- ❑ One output bus: Data Out

■ Memory word is selected by:

- ❑ Address selects the word to put on Data Out
- ❑ Write Enable = 1: address selects the memory word to be written via the Data In bus

■ Clock input (CLK)

 - ❑ The CLK input is a factor ONLY during write operation
- ❑ During read operation, memory behaves as a combinational logic block:
 - Address valid => Data Out valid after “access time.”




Step 3

- Register Transfer Requirements → Datapath Design
 - Instruction Fetch
 - Decode instructions and Read Operands
 - Execute Operation
 - Write back the result



3a: Overview of the Instruction Fetch Unit

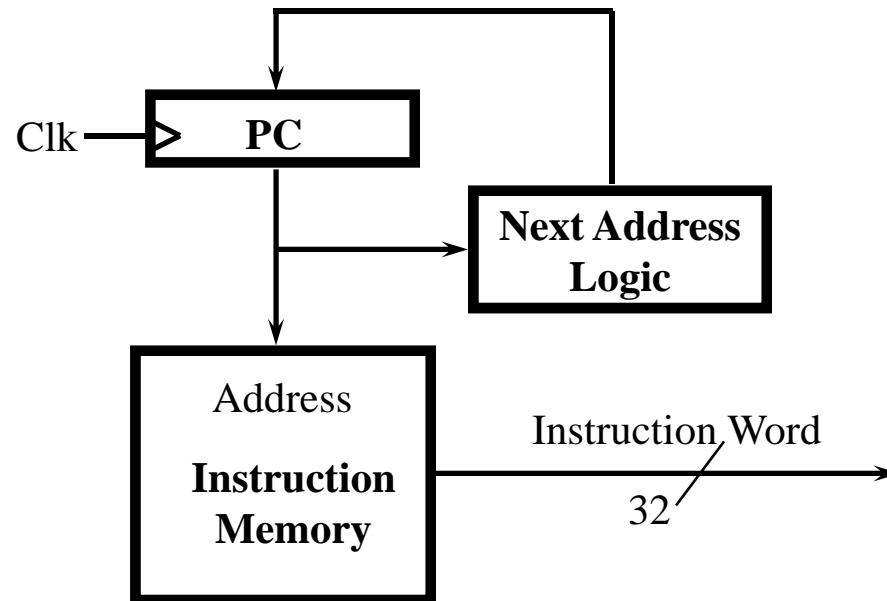- The common RTL operations
 - Fetch the Instruction: $\text{mem}[\text{PC}]$
 - Update the program counter:
 - Sequential Code: $\text{PC} \leftarrow \text{PC} + 4$
 - Branch and Jump: $\text{PC} \leftarrow \text{"something else"}$





3b: R-Type Instructions

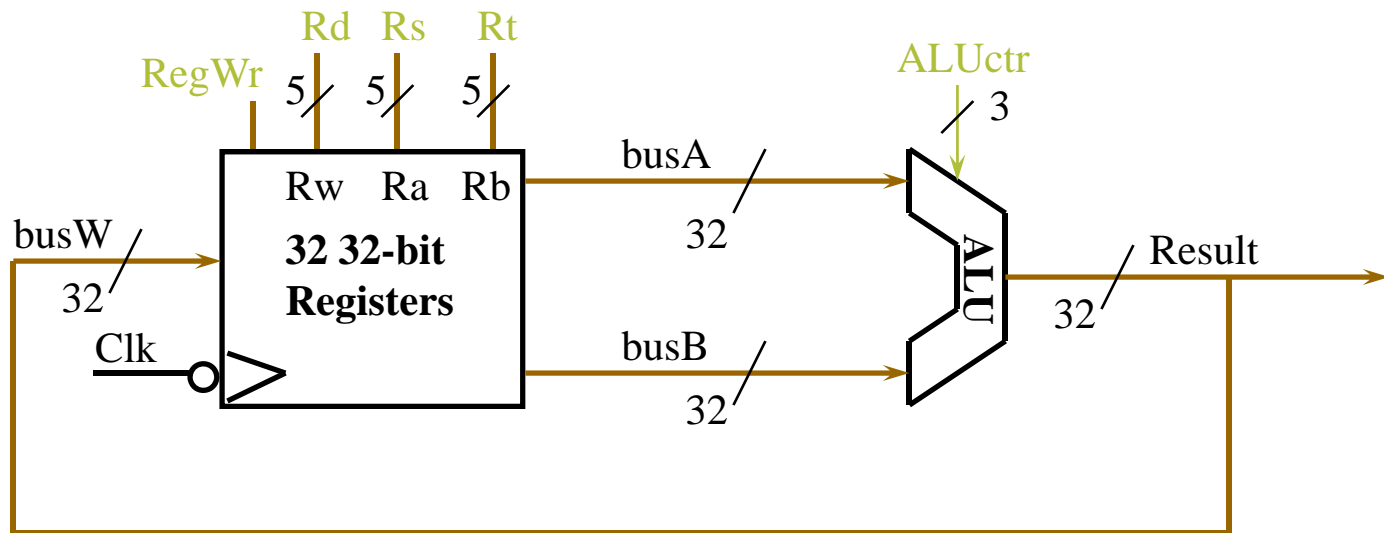 - $R[rd] \leftarrow R[rs] \text{ op } R[rt]$ Example: add rd, rs, rt
 - Ra, Rb, and Rw come from instruction's rs, rt, and rd fields
 - ALUctr and RegWr: control logic after decoding the instruction





3c: Load Operations

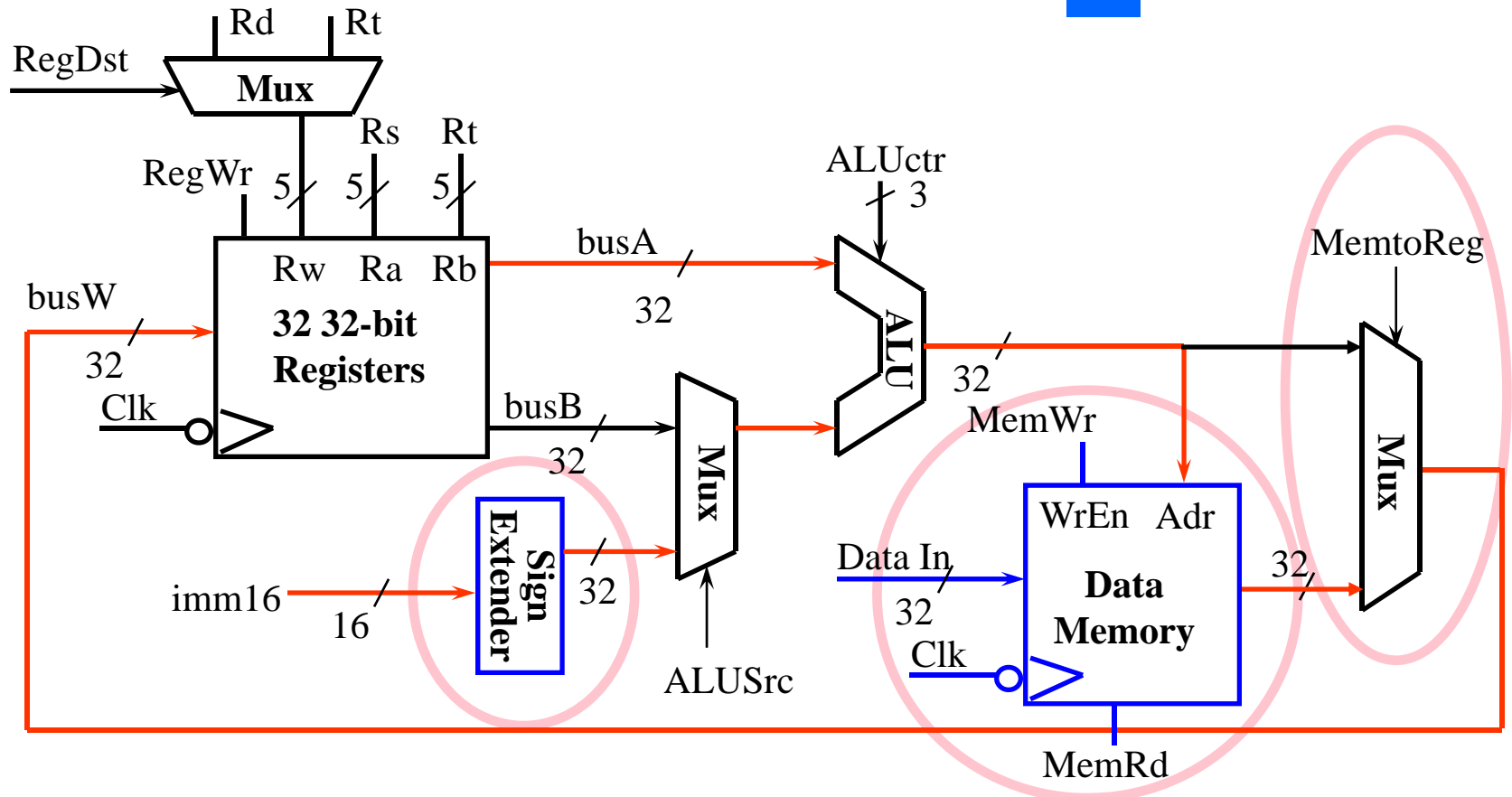 - $R[\underline{rt}] \leftarrow \text{Mem}[R[rs] + \text{SignExt}[\text{imm16}]]$ Example: `lw rt, rs, imm16`




3d: Store Operations

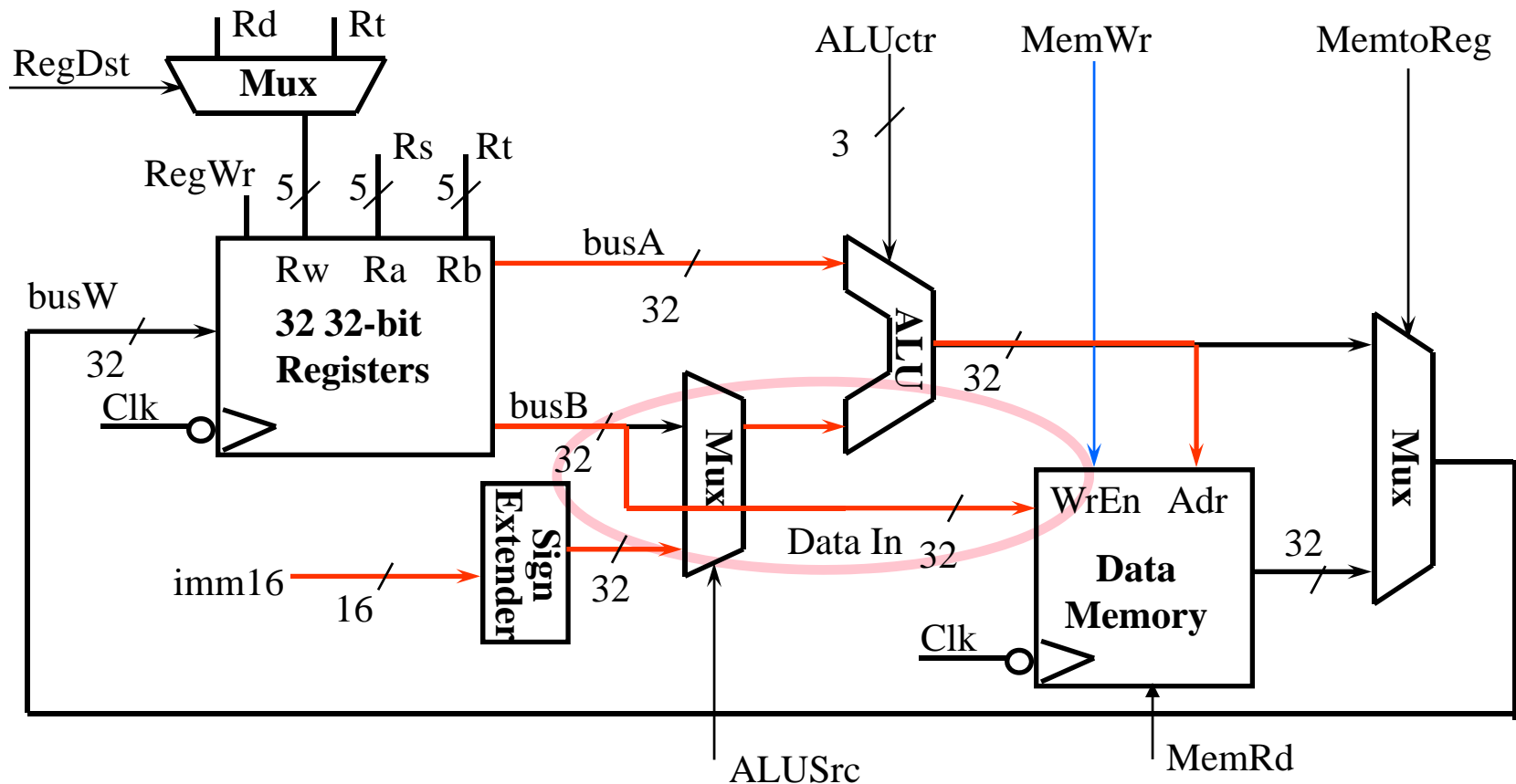 - $\text{Mem}[\text{R}[\text{rs}] + \text{SignExt}[\text{imm16}]] \leftarrow \text{R}[\text{rt}]$ Example: `sw rt, rs, imm16`



3e: The Branch Instruction


 


■ beq rs, rt, imm16


- mem[PC] Fetch the instruction from memory
- $\text{Equal} \leftarrow R[\text{rs}] == R[\text{rt}]$ Calculate the branch condition
- if (Equal && Branch Instr.) Calculate the next instruction's address
 - $\text{PC} \leftarrow \text{PC} + 4 + (\text{SignExt}(\text{imm16}) \times 4)$
- else
 - $\text{PC} \leftarrow \text{PC} + 4$

Datapath for Branch Operations


■ beq rs, rt, imm16

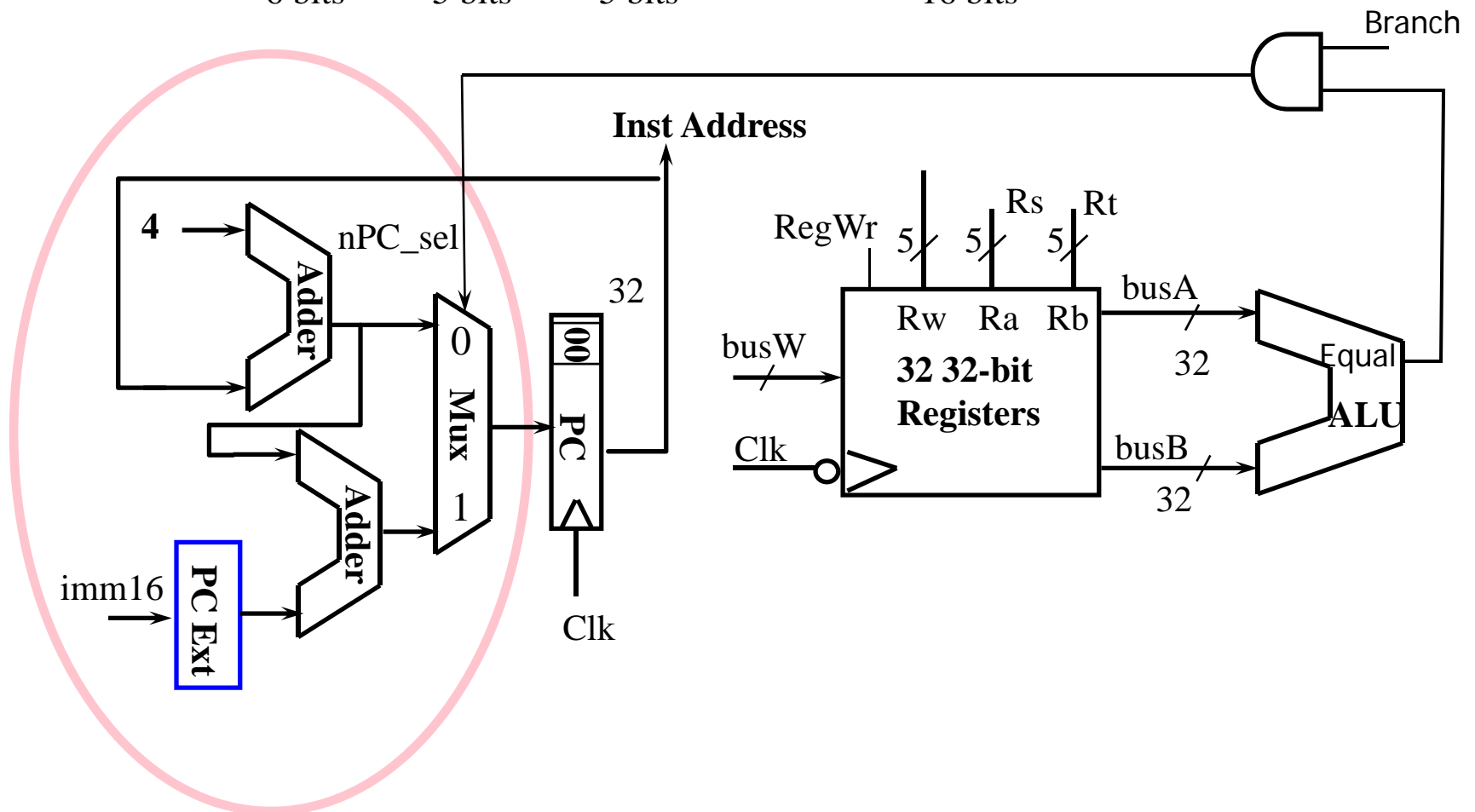 

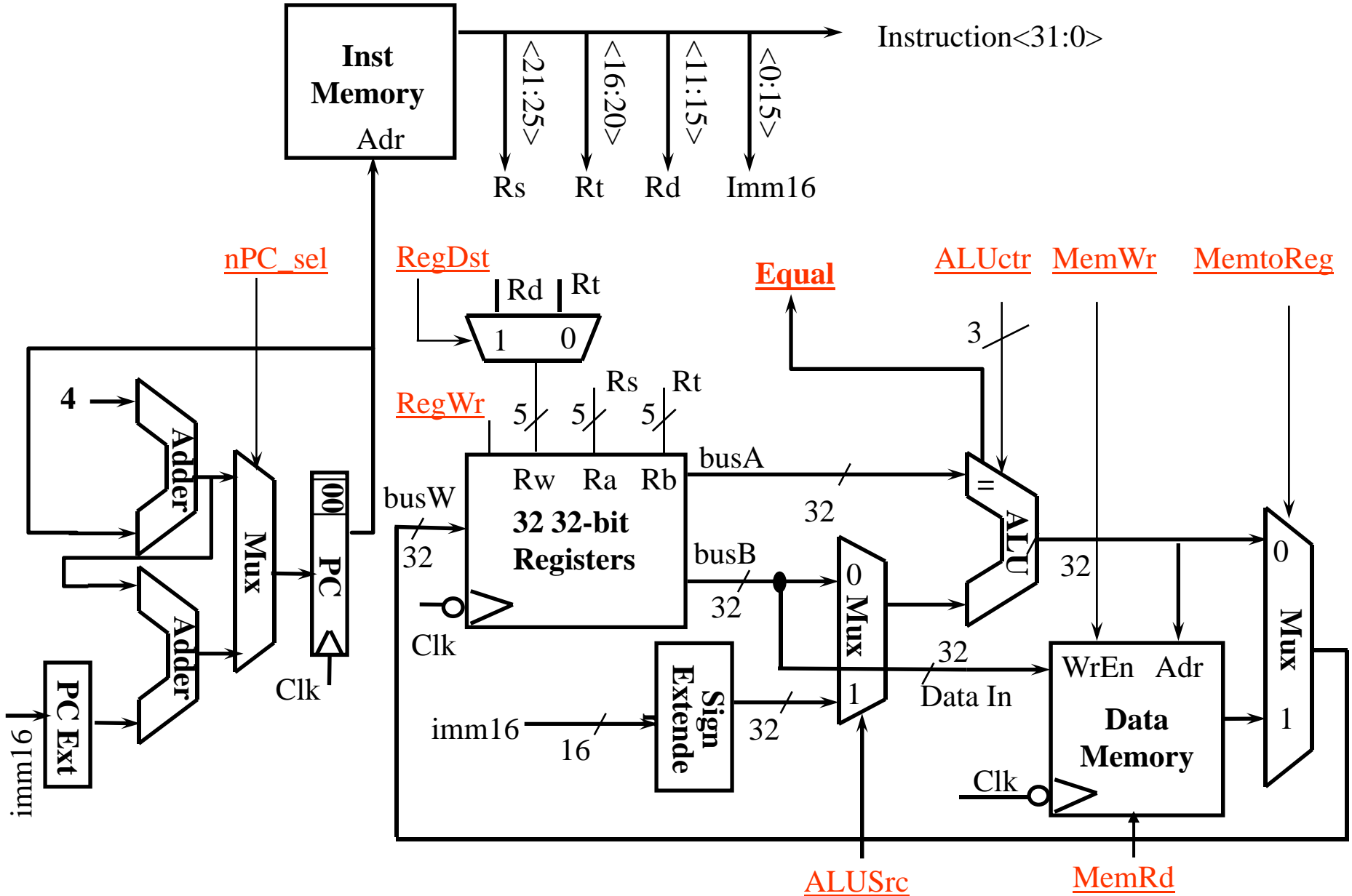
Putting it All Together: A Single Cycle Datapath



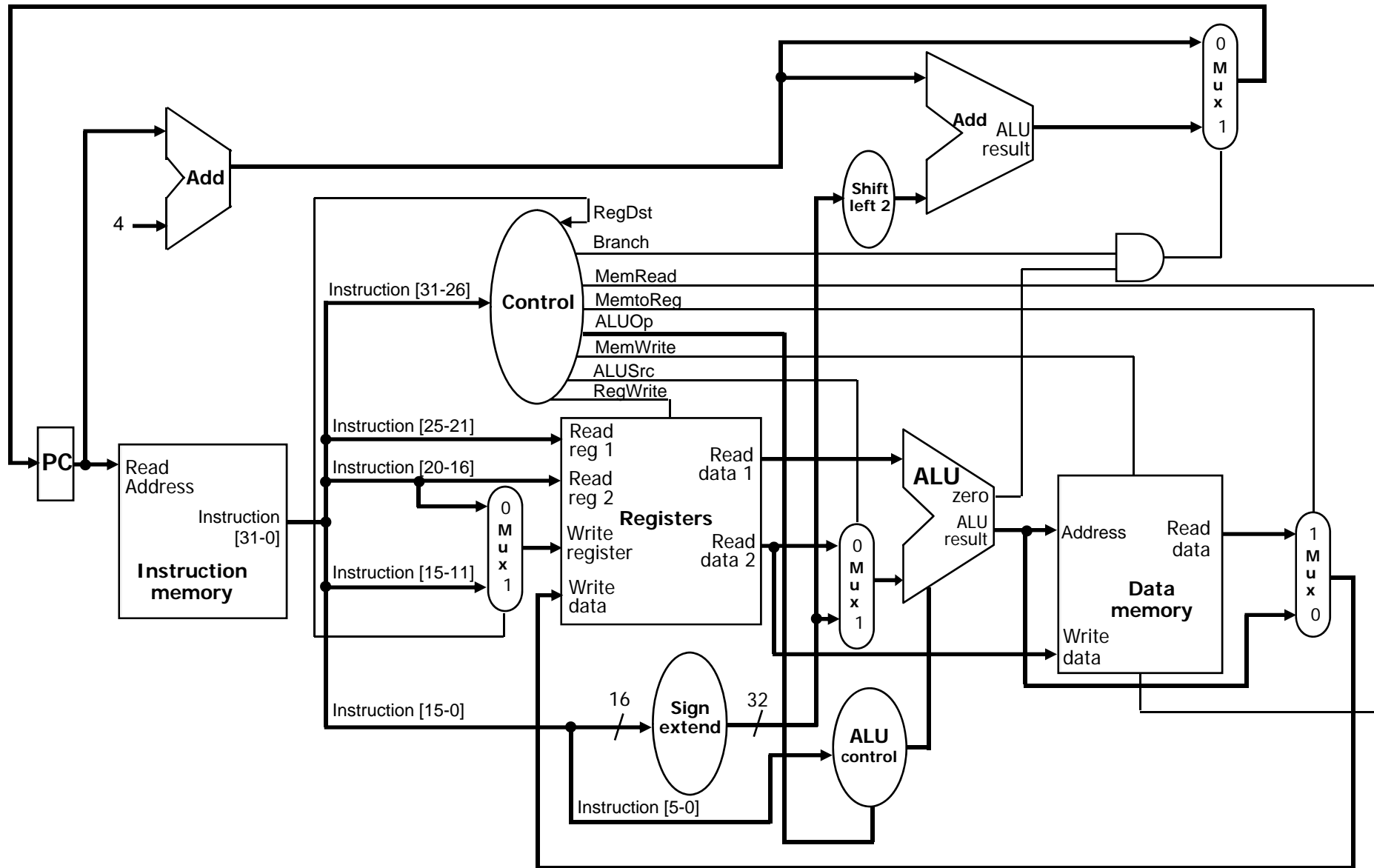Different View of Same Implementation (From Book)




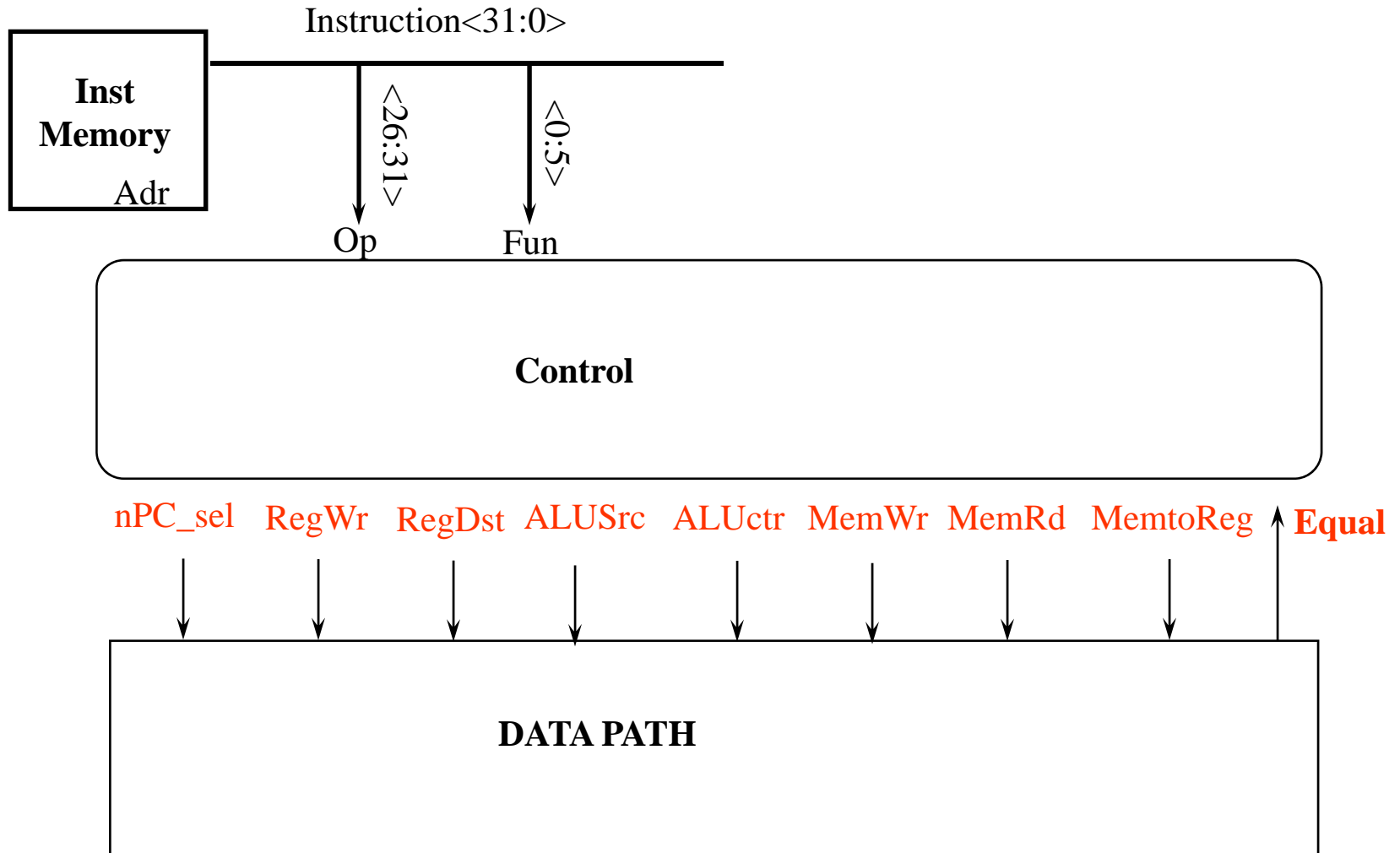Step 4: Given Datapath: RTL \rightarrow Control



Meaning of the Control Signals

 - Rs, Rt, Rd and Imm16 hardwired into datapath
- nPC_sel: $0 \Rightarrow PC \leftarrow PC + 4;$
 $1 \Rightarrow PC \leftarrow PC + 4 + \text{SignExt}(\text{Imm16}) \parallel 00$



Meaning of the Control Signals

■ **ALUSrc:** 0 => regB; 1 => immedi

■ **MemRd:** read memory


■ **MemWr:** write memory

■ **ALUctr:** “add”, “sub”, “and”, “or”, “set less than”


■ **RegWr:** write dest register

■ **MemtoReg:** 0 => ALU; 1 => Mem


■ **RegDst:** 0 => “rt”; 1 => “rd”

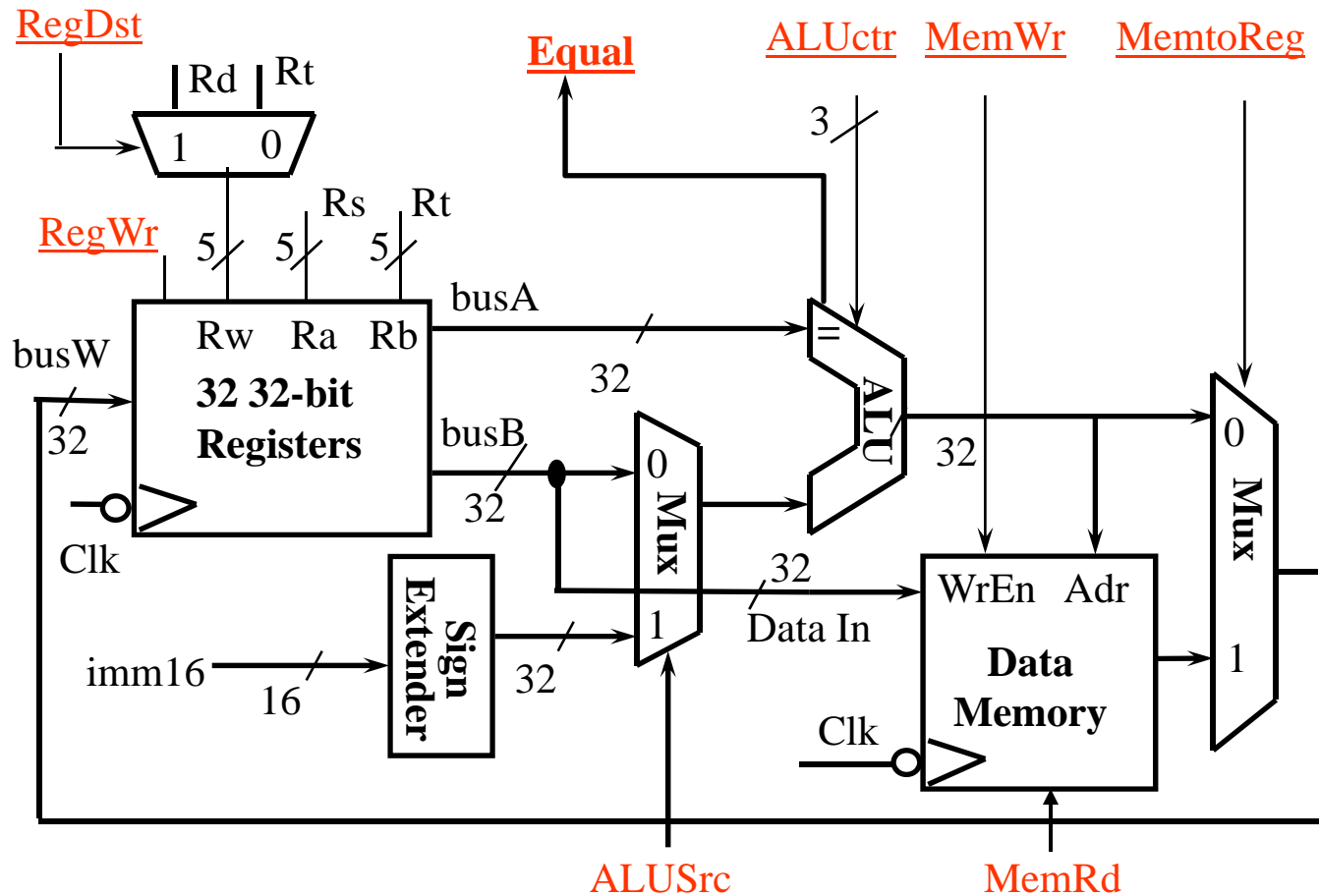

Example: Load Instruction

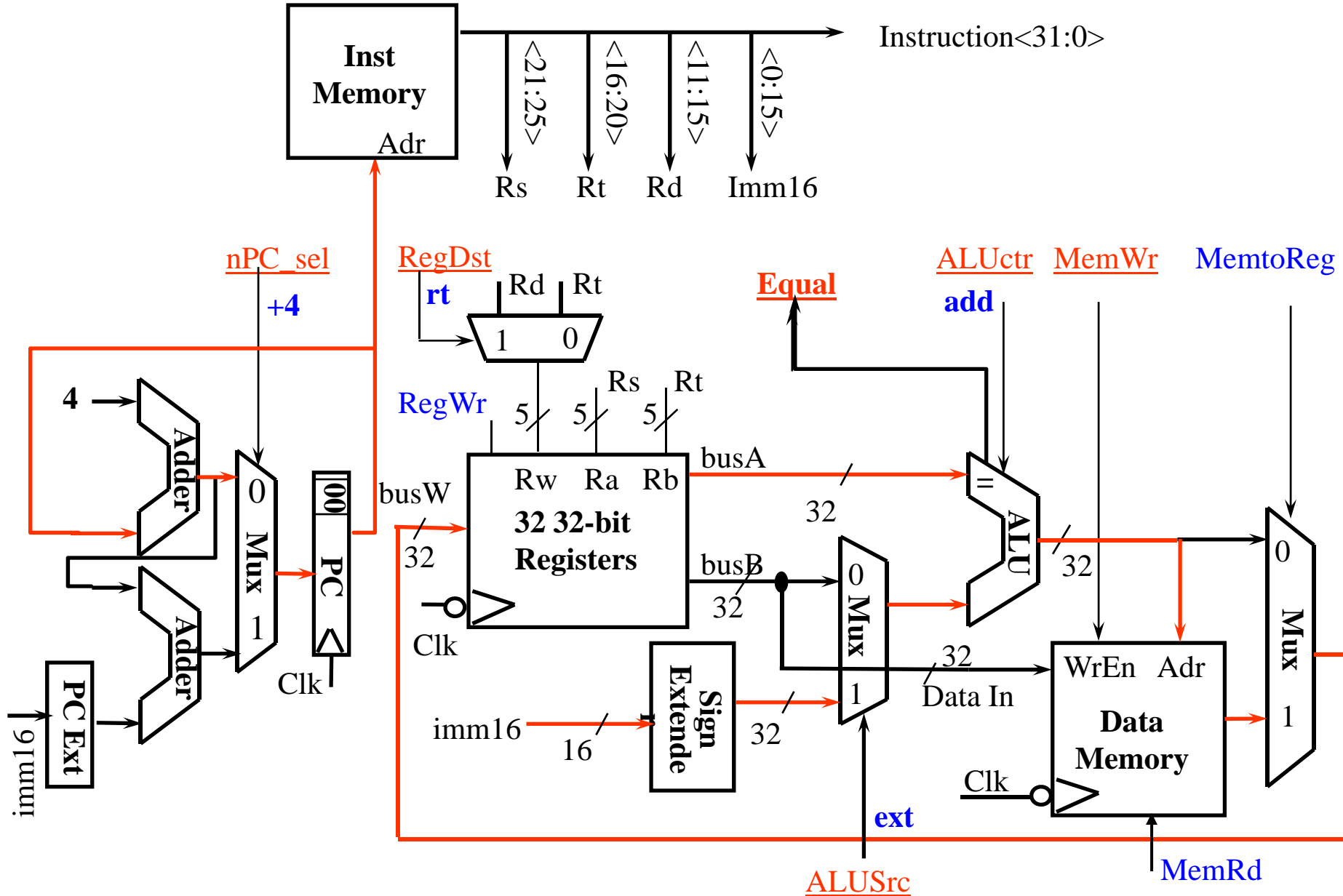

An Abstract View of the Implementation

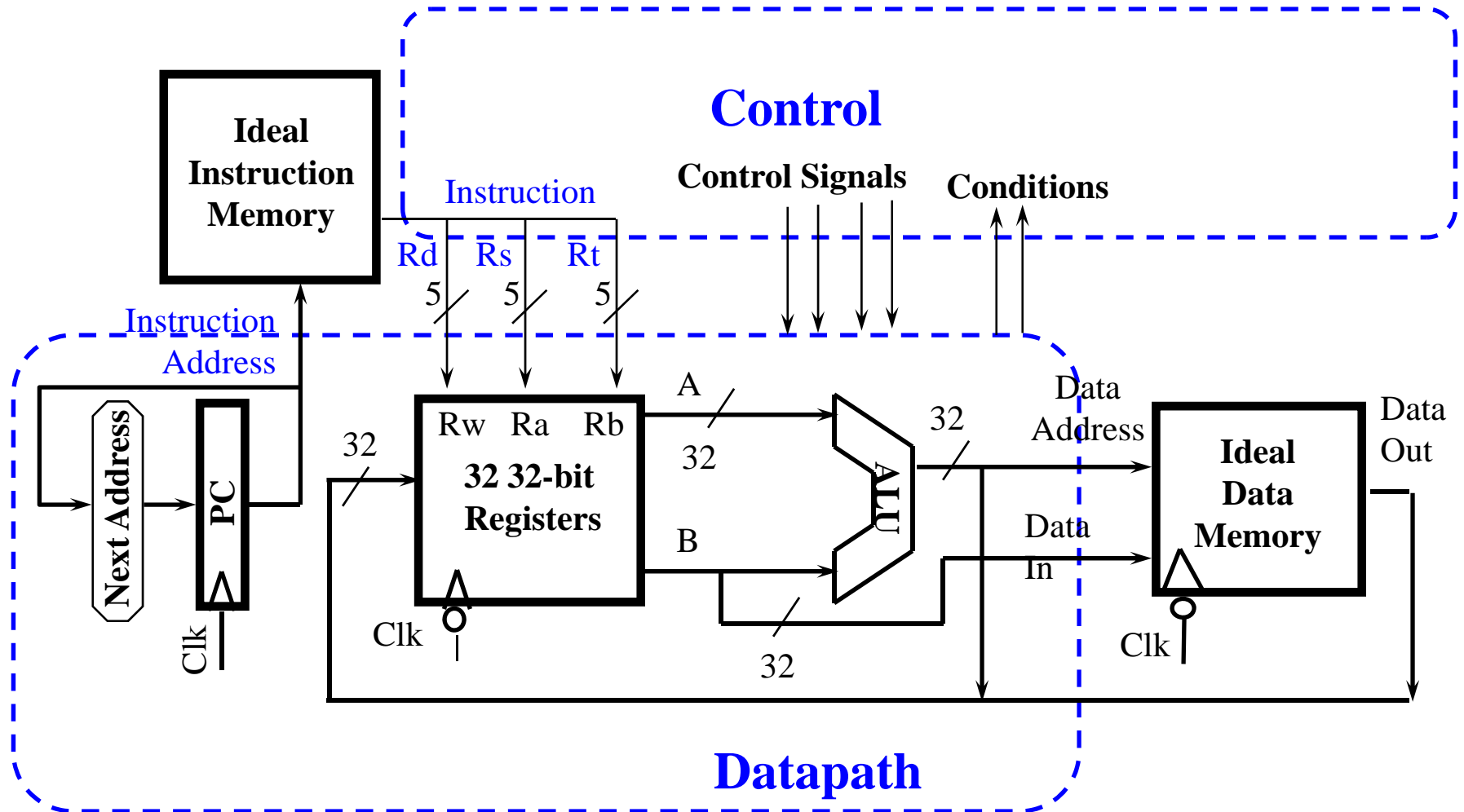

Summary

- 5 steps to design a processor
 - 1. Analyze instruction set => datapath requirements
 - 2. Select set of datapath components & establish clock methodology
 - 3. Design datapath meeting the requirements
 - 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
 - 5. Design the control logic
- MIPS makes it easier
 - Instructions same size
 - Source registers always in same place
 - Immediates same size, location
 - Operations always on registers/immediates
- Single cycle datapath => CPI=1, CCT => long
- Next time: implementing control