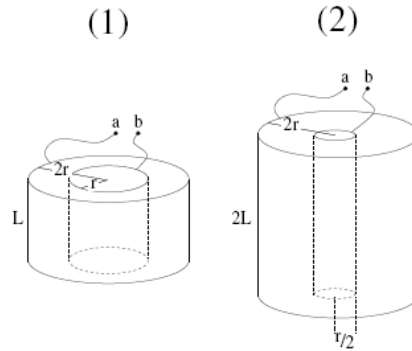


Closed book. No calculators are to be used for this quiz.

Quiz duration: 10 minutes


Name: _____ Student ID: _____ Signature: _____

Q. The inner and outer walls of the hollow cylindrical resistors below are coated with a metallic paint and between the walls is the same uniform material with a constant resistivity. The resistance measured between the terminals a and b in (1) is R , which is a function of L and the ratio of the inner and outer radii. Find the resistance measured between the terminals a and b in (2) by considering it as a collection of resistors connected in series and/or in parallel.



Solution:

Decompose (2) into four resistors:

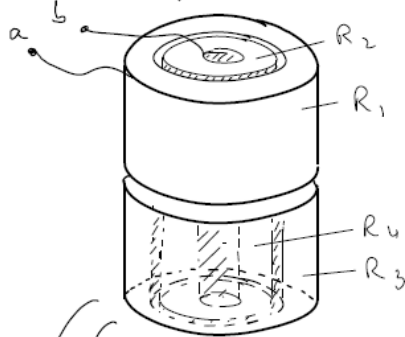

R_1 and R_3 are identical to (1)

$$\text{with } \frac{r_{in}}{r_{out}} = \frac{r}{2r} = \frac{1}{2}$$

R_2 and R_4 have the same length

$$L \text{ and } \frac{r_{in}}{r_{out}} = \frac{r/2}{r} = \frac{1}{2}$$

Therefore, $R_1 = R_2 = R_3 = R_4 = R$.


$$R_{ab} = (R_1 // R_3) + (R_2 // R_4) = \frac{R}{2} + \frac{R}{2} = \boxed{R}$$

Closed book. No calculators are to be used for this quiz.


Quiz duration: 10 minutes

Name: Student ID: Signature:

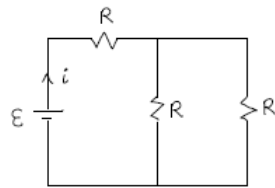Q. The current flowing across the emf source in the resistor circuit in (a) is i . Calculate the currents in the circuit (b) in terms of i only. (Hint: You can consider each emf source separately first and then use the superposition principle to obtain the currents.)




(a)

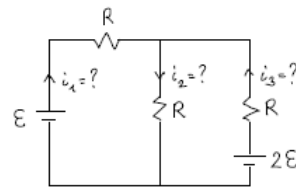


(b)

Solution:

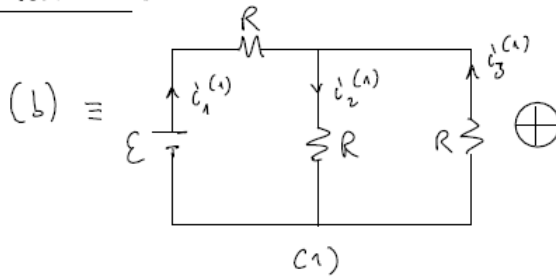

(1)

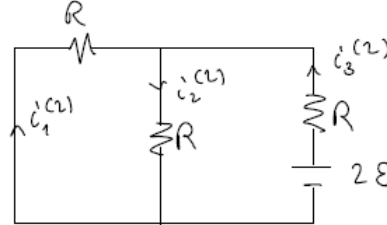

(2)

(1) is the same as (a) \Rightarrow $i_1^{(1)} = i, i_2^{(1)} = i/2, i_3^{(1)} = -i/2$

(2) is the mirror image of (a), except the currents are doubled since $E \rightarrow 2E$. \Rightarrow $i_1^{(2)} = -i, i_2^{(2)} = i, i_3^{(2)} = 2i$

\Rightarrow Currents in (b) follow from superposition:

$$i_1 = i_1^{(1)} + i_1^{(2)} = 0$$

$$i_2 = i_2^{(1)} + i_2^{(2)} = 3i/2$$


$$i_3 = i_3^{(1)} + i_3^{(2)} = 3i/2$$

Closed book. No calculators are to be used for this quiz.

Quiz duration: 10 minutes

Name: _____ Student ID: _____ Signature: _____

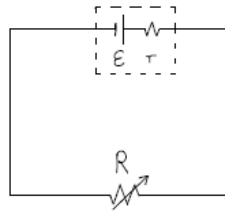Q. The emf source in the circuit below has an internal resistance r as shown and is connected to a variable "load" resistor R . Find the value of R for which the power dissipated on the load has the maximum possible value.



Solution:

$$i = \frac{\mathcal{E}}{r+R} \Rightarrow \text{Power on the load} = i^2 R = \frac{\mathcal{E} R}{(r+R)^2}$$

$$\text{Maximize w.r.t. } R: \frac{d}{dR} \left[\frac{\mathcal{E} R}{(r+R)^2} \right] = 0 \Rightarrow$$

$$(r+R)^2 - 2R(r+R) = 0 \quad \text{or} \quad \boxed{R=r}$$

Make sure that $R=r$ gives a maximum, not a minimum:

$$\begin{aligned} & \left. \frac{d^2}{dR^2} \left[\frac{\mathcal{E} R}{(r+R)^2} \right] \right|_{R=r} \stackrel{?}{<} 0 \\ & = \left. \frac{d}{dR} \left[\frac{r-R}{(r+R)^3} \right] \right|_{R=r} = -\frac{1}{2R^3} < 0 \quad \checkmark \end{aligned}$$

Closed book. No calculators are to be used for this quiz.

Quiz duration: 10 minutes


Name: _____ Student ID: _____ Signature: _____

Q. The capacitor below is initially uncharged. The switch is closed at time $t = 0$. It is opened at a later time t_1 , when the capacitor has a charge $Q_f/2$, half of its maximal value $Q_f = CV$. Find the charge on the capacitor at $t = 2t_1$ in terms of Q_f .

Hint:

Charging: $Q(t) = Q_f(1 - e^{-t/\tau})$

Discharging: $Q(t) = Q_i e^{-t/\tau}$

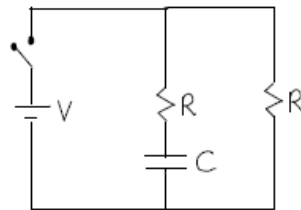

Solution:

The charging circuit is effectively $V \left[\begin{array}{c} R \\ \hline C \end{array} \right] \Rightarrow \tau_1 = RC$

$$\Rightarrow (1 - e^{-t_1/\tau_1}) = 1/2 \Rightarrow t_1 = \tau_1 \cdot \ln 2 = \ln 2 RC$$

After the switch is opened, C discharges over a resistance $2R \Rightarrow \tau_2 = 2RC$

$$\Rightarrow Q(2t_1) = \frac{Q_f}{2} \cdot (1 - e^{-t_1/\tau_2})$$

$$= \frac{Q_f}{2} \cdot (1 - e^{-(\ln 2 RC)/2RC})$$

$$= \frac{Q_f}{2} \left(1 - e^{-\frac{\ln 2}{2}} \right) = \frac{Q_f}{2} \left(1 - \frac{\sqrt{2}}{2} \right) \approx \boxed{\frac{Q_f}{7}}$$

duration of discharge