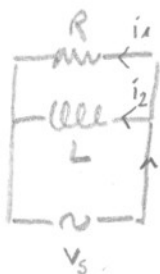


PHYS 102: General Physics KOÇ UNIVERSITY Spring Semester 2010  
 College of Arts and Sciences  
 Quiz 11 May 27, 2010

Closed book. No calculators are to be used for this quiz.  
 Quiz duration: 10 minutes

Name: \_\_\_\_\_ Student ID: \_\_\_\_\_ Signature: \_\_\_\_\_

Q. An AC-voltage source, a resistor  $R$  and an inductor  $L$  are all connected in parallel, so that  $v_s(t) = v_R(t) = v_L(t) = V \cos(\omega t)$ . Draw a single phasor diagram for all the voltages and the currents when  $\omega t = \pi/4$ . Assume  $R > \omega L$ .



$$v_L(t) = L \frac{di_2}{dt} = V \cos \omega t$$

$$\frac{di_2}{dt} = \frac{V}{L} \cos \omega t \Rightarrow i_2 = \frac{V}{\omega L} \sin \omega t = \frac{V}{\omega L} \cos(\omega t - \pi/2) \quad (1)$$

$$v_R(t) = R i_1(t) = V \cos \omega t$$

$$i_1(t) = \frac{V}{R} \cos \omega t \quad (2)$$

$$(1) + (2) \rightarrow i = i_1 + i_2 = V \left( \frac{1}{R} \cos \omega t + \frac{1}{\omega L} \sin \omega t \right)$$

$$\cos(\alpha + \beta) = \cos \alpha \cos \beta - \sin \alpha \sin \beta$$

$$\left. \begin{aligned} \alpha &= \omega t \\ \cos \beta &= 1/R \\ \sin \beta &= -1/\omega L \end{aligned} \right\} \tan \beta = \frac{-1/\omega L}{1/R} = -\frac{R}{\omega L}$$


$$\beta = \tan^{-1}(-R/\omega L)$$

So we can write,

$$i(t) = V \cos(\omega t + \beta)$$
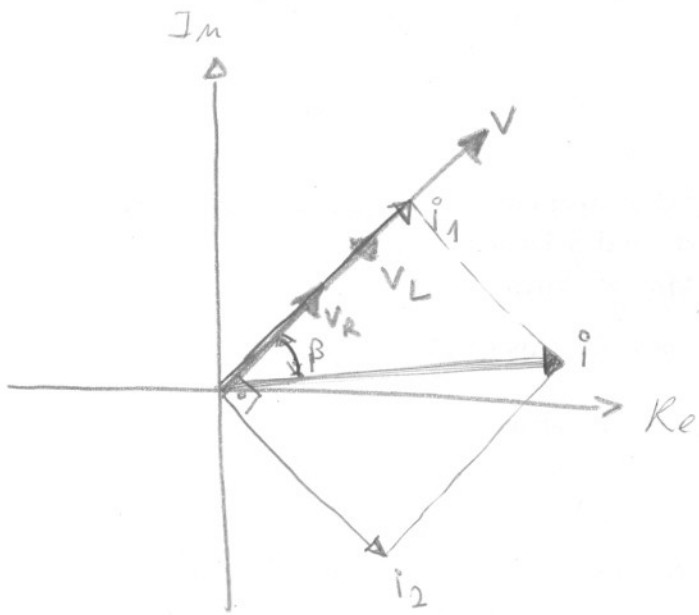
$$\text{where } \beta = \tan^{-1}\left(\frac{-R}{\omega L}\right) \Rightarrow \beta < 0$$






$$\beta = \arctan \left( \frac{-R}{\omega L} \right)$$

Closed book. No calculators are to be used for this quiz.  
 Quiz duration: 10 minutes

Name: \_\_\_\_\_ Student ID: \_\_\_\_\_ Signature: \_\_\_\_\_

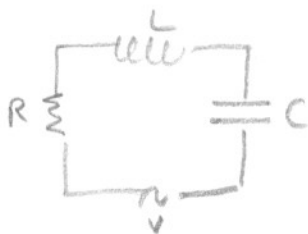Q. An AC-current source, a resistor  $R$ , an inductor  $L$  and a capacitor  $C$  are all connected in series. The current supplied by the source is  $i(t) = I \cos(\omega_0 t)$ , oscillating at the resonant frequency  $\omega_0 = 1/\sqrt{LC}$ . Find the maximum power stored in the inductor.



Since the circuit is in resonance,

$$X_L = X_C \Rightarrow \phi = 0 \quad (\tan \phi = \frac{X_L - X_C}{R})$$

Thus  $v(t) = V \cos(\omega_0 t)$

$$V_L(t) = L \frac{di}{dt} = -IL\omega_0 \sin \omega_0 t$$

$$P(t) = i(t) \cdot V_L(t) = (I \cos \omega_0 t) (-IL\omega_0 \sin \omega_0 t)$$

$$= -\frac{I^2 L \sin(2\omega_0 t)}{2}$$

then power is maximized when,  $-1 \leq \sin \theta \leq 1$

$$\left. \frac{dP}{dt} \right|_{t=t_1} = 0$$

$$|P_{\max}| = \frac{I^2 L}{2}$$

$$\Rightarrow -\frac{I^2 L}{2} 2\omega_0 \cos(2\omega_0 t_1) = 0$$

$$2\omega_0 t_1 = \frac{\pi}{2} \rightarrow t_1 = \frac{1}{\omega_0} \frac{\pi}{4}$$

and its maximum value is,


$$|P(t=t_1)| = \left| -\frac{I^2 L}{2} \sin\left(2\omega_0 \cdot \frac{1}{\omega_0} \frac{\pi}{4}\right) \right| = \frac{I^2 L}{2}$$

Quiz 11 May 27, 2010

Closed book. No calculators are to be used for this quiz.  
Quiz duration: 10 minutes

Name: \_\_\_\_\_ Student ID: \_\_\_\_\_ Signature: \_\_\_\_\_

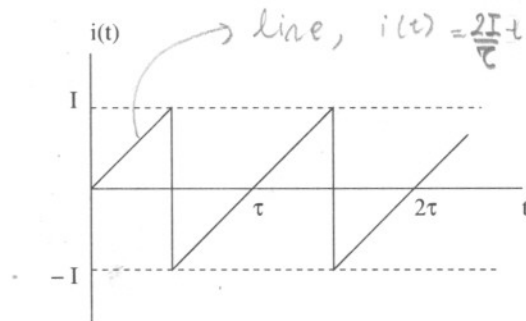Q. The current in a circuit is given in the figure. Find the average current and the rms current.



$$i_{av} = \frac{1}{2} \int_0^{2\tau} i(t) dt = 0$$

$$i_{rms} = \sqrt{\frac{1}{2} \int_0^{2\tau} i^2(t) dt}$$

$$= \sqrt{\frac{1}{2} \cdot \frac{2I}{3}}$$

$$= \sqrt{\frac{I}{3}}$$

$$I = 2 \times \int_0^{\tau/2} \left[ \frac{2I}{\tau} t \right]^2 dt = 2 \cdot \frac{4I}{\tau^2} \cdot \frac{\tau^3}{8} = \frac{I}{3}$$

PHYS 102: General Physics KOÇ UNIVERSITY Spring Semester 2010  
 College of Arts and Sciences  
 Quiz 11 May 27, 2010


Closed book. No calculators are to be used for this quiz.  
 Quiz duration: 10 minutes

Name: \_\_\_\_\_ Student ID: \_\_\_\_\_ Signature: \_\_\_\_\_

Q. You wish to step-down the 220 V rms house voltage for using your water heater (which is effectively a resistor), by placing a transformer between the heater and the wall socket. If the maximum voltage your heater can take is 30 V, what would you use for the winding number ratio  $N_2/N_1$  in your transformer? Recall that the heater is connected to the secondary winding with  $N_2$  turns. ( $\sqrt{2} \approx 1.4$ )

$$V_{\text{rms}} = 220 \text{ V} = \frac{V}{\sqrt{2}} \quad (\text{for a sinusoidal source})$$
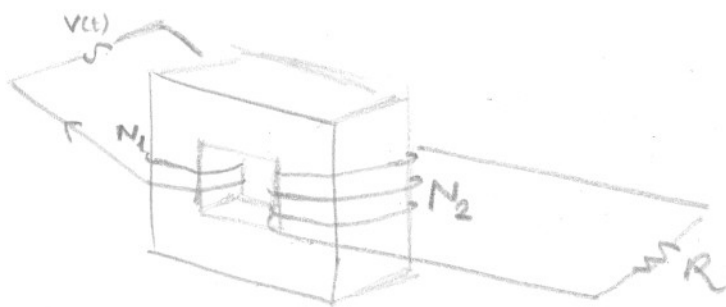
$$V_R = V_R \cdot \cos(\omega t + \phi) \quad \Rightarrow V = \sqrt{2} \times 220 \text{ V} = 308 \text{ V}$$



$$\frac{V_2}{V_1} = \frac{N_2}{N_1}$$


to step-down the voltage we need to choose  $N_2 < N_1$  ( $V_2 < V_1$ ).

$$\frac{30 \text{ V}}{308 \text{ V}} = \frac{N_2}{N_1} \approx 0.1$$

Closed book. No calculators are to be used for this quiz.  
 Quiz duration: 10 minutes

Name: \_\_\_\_\_ Student ID: \_\_\_\_\_ Signature: \_\_\_\_\_

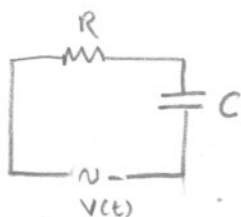Q. You have a  $200\text{-}\Omega$  resistor and a  $6.00\text{-}\mu\text{F}$  capacitor. You construct a series circuit with an AC-voltage source that has voltage amplitude  $V = 30\text{ V}$  and angular frequency of  $250\text{ rad/s}$ . Find the phase angle of the source voltage with respect to the current. Does the source voltage lag or lead the current?




$$V(t) = V \cos(\omega t + \phi) \quad , \quad V = 30\text{ V}, \quad \omega = 250\text{ rad/s}$$

$$i(t) = I \cos \omega t$$

$$V_C = \frac{q(t)}{C} \quad \text{and} \quad i = \frac{dq}{dt} \Rightarrow q = \int i(t) dt = \frac{I}{\omega} \sin \omega t \Rightarrow \boxed{V_C = \frac{I}{\omega C} \sin \omega t}$$

$$V_R = i(t) \cdot R = IR \cos \omega t$$
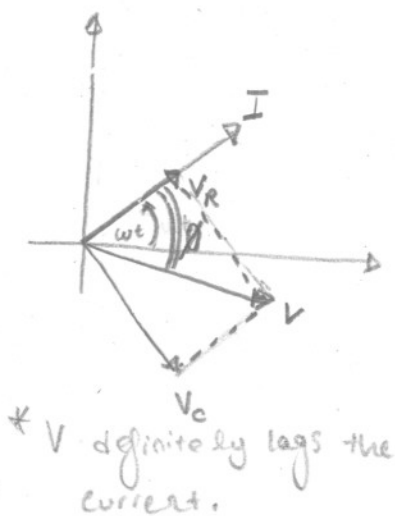
$$\boxed{= \frac{I}{\omega C} \cos(\omega t - \pi/2)}$$



$$\tan \phi = \frac{V_C}{V_R} = \frac{\frac{I}{\omega C}}{IR} = \frac{1}{\omega RC}$$

$$= [250\text{ rad/s} \times 200\ \Omega \times 6 \times 10^{-6}\text{ F}]^{-1}$$

$$= [300000 \times 10^{-6}]^{-1}$$

$$= \frac{10}{3}$$

$$\phi = \arctan\left(\frac{10}{3}\right) \approx 1.28\text{ rad}$$