

Closed book. No calculators are to be used for this quiz.


Quiz duration: 10 minutes

Name:

Student ID:

Signature:

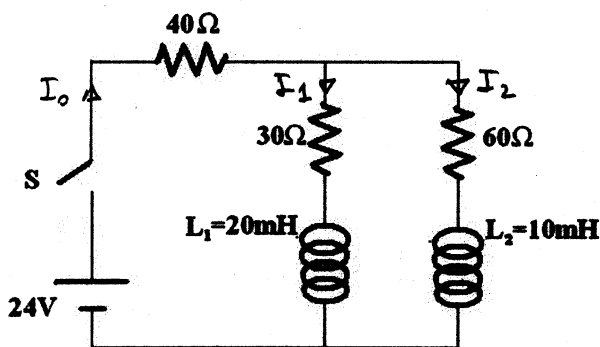In the circuit shown below, the switch S is closed at time $t=0$. Find the total energies stored in the inductors L_1 and L_2 after the switch has been closed a long time.



- Energy stored in an inductor = $U = \frac{1}{2} L I^2$
- after a long time : currents are settled to their steady state values.
- $R_{eq} = 40\Omega + \left(\frac{1}{30\Omega} + \frac{1}{60\Omega} \right)^{-1} = 40\Omega + 20\Omega = 60\Omega$
- I_0, I_1 and I_2 are as shown on the figure.

$$I_0 = \frac{24V}{R_{eq}} = \frac{24V}{60\Omega} = 0,4A \Rightarrow I_1 = \frac{2}{3} \times 0,4A, \quad I_2 = \frac{1}{3} \times 0,4A$$

$$U_1 = \frac{1}{2} 20 \times 10^{-3} H \times \frac{4}{3} \times 0,16 A = 0,711 \text{ mJ}$$

$$U_2 = \frac{1}{2} 10 \times 10^{-3} H \times \frac{1}{3} \times 0,16 A = 0,089 \text{ mJ}$$

Closed book. No calculators are to be used for this quiz.

Quiz duration: 10 minutes

Name:

Student ID:

Signature:

Show that the quantity $\sqrt{\frac{L}{C}}$ has units of resistance (ohms).

- Energy of an inductor: $U = \frac{1}{2} L I^2$

Dimensional analysis of this equation gives:

$$[\text{energy}] = [\text{inductance}] [\text{current}]^2 \rightarrow [\text{inductance}] = \frac{[\text{energy}]}{[\text{current}]^2}$$

- Energy of a capacitor: $U = \frac{1}{2} C V^2$

Dimensional analysis of this equation gives:

$$[\text{energy}] = [\text{capacitance}] [\text{potential}]^2 \rightarrow [\text{capacitance}] = \frac{[\text{energy}]}{[\text{potential}]^2}$$

The quantity $\sqrt{\frac{L}{C}}$ has units of $\sqrt{\frac{[\text{inductance}]}{[\text{capacitance}]}} = \sqrt{\frac{\frac{[\text{energy}]}{[\text{current}]^2}}{\frac{[\text{energy}]}{[\text{potential}]^2}}}$

$$= \sqrt{\frac{[\text{potential}]^2}{[\text{current}]^2}} = [\text{resistance}]$$

$[\text{resistance}] = \Omega$ in the SI system.

Closed book. No calculators are to be used for this quiz.

Quiz duration: 10 minutes

Name:

Student ID:

Signature:

A toroidal solenoid with cross-sectional area A and mean radius r is closely wound with N turns of wire. The toroid is wound on a nonmagnetic core. Determine its self-inductance L . Assume that B is uniform across a cross section.

- Toroidal solenoid
- Cross-sectional area: A
- mean radius: $r \rightarrow \text{length} = 2\pi r$
- N turns
- assume uniform B .

$$L = \frac{N\Phi_B}{i} = \frac{NB \cdot A}{i}$$

B of a solenoid = $\mu_0 n i$, where n is the number of turns per length.
 For the case of a toroidal solenoid length is the circumference of the toroid, and $n = \frac{N}{2\pi r}$. With this n , B of a toroidal solenoid becomes $\mu_0 \frac{N}{2\pi r} i$. Substituting this into L , we obtain:

$$L = \frac{N \cdot A}{i} \cdot \mu_0 \frac{N}{2\pi r} i = \mu_0 \frac{N^2}{2\pi r} A$$

Closed book. No calculators are to be used for this quiz.


Quiz duration: 10 minutes

Name:

Student ID:

Signature:

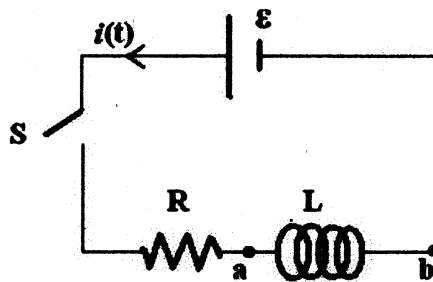In the circuit shown below, the switch S is closed at time $t=0$. a) What is the current i just after S is closed? b) What is the current i long time after S is closed? c) Find an expression for V_{ab} as a function of time since S is closed.



- a) Immediately after S is closed, $i = 0$, because current cannot develop instantaneously.
- b) Long after S is closed, current reaches its steady state value ($\frac{di}{dt} = 0$), and we have $i = \frac{\mathcal{E}}{R}$.
- c) For the transient case we need to solve the following equations:

$$\mathcal{E} - V_R - V_L = 0$$

V_R : voltage drop due to resistor. $V_R = i \cdot R$
 V_L : " " " " inductor. $V_L = L \cdot \frac{di}{dt}$

$$\mathcal{E} - i \cdot R - L \frac{di}{dt} = 0 \quad (i \text{ is a function of time, } i = i(t))$$

$$\mathcal{E} - iR = L \frac{di}{dt} \quad dt = L \frac{di}{\mathcal{E} - iR} \quad \int_0^t dt = \int_0^{i(t)} L \frac{di}{\mathcal{E} - iR}$$

$$t = L \left[-\frac{1}{R} \ln(\mathcal{E} - iR) \right]_0^{i(t)} = -\frac{L}{R} \left[\ln(\mathcal{E} - i(t)R) - \ln \mathcal{E} \right]$$

$$-\frac{R}{L} t = \ln \frac{\mathcal{E} - i(t)R}{\mathcal{E}} \quad 1 - i(t) \frac{R}{\mathcal{E}} = e^{-\frac{R}{L} t}$$

$$1 - e^{-\frac{R}{L} t} = i(t) \frac{R}{\mathcal{E}} \quad \rightarrow \quad i(t) = \frac{\mathcal{E}}{R} \left(1 - e^{-\frac{R}{L} t} \right)$$

$$V_{ab} = L \frac{di}{dt} = L \frac{d}{dt} \left(\frac{\mathcal{E}}{R} - \frac{\mathcal{E}}{R} e^{-\frac{R}{L}t} \right) = L \left(-\frac{\mathcal{E}}{R} \right) \left(-\frac{R}{L} \right) e^{-\frac{R}{L}t}$$

$$= \mathcal{E} e^{-\frac{R}{L}t}$$

==

Closed book. No calculators are to be used for this quiz.

Quiz duration: 10 minutes

Name:

Student ID:

Signature:

A long solenoid with length l and cross-sectional area A is closely wound with N_1 turns of wire. A coil with N_2 turns surrounds it at its center. Find the mutual inductance.

$$\text{Mutual inductance, } M = \frac{N_2 \Phi_{B_2}}{i_1} = \frac{N_1 \Phi_{B_1}}{i_2}$$

$$\Phi_{B_2} = \Phi_{B_1} = B_1 \cdot A \quad (\text{because the outer solenoid surrounds the inner one})$$

$$B \text{ of a solenoid: } \mu_0 n I \rightarrow B_1 = \mu_0 \frac{N_1}{l} i_1$$

$$\Rightarrow M = \frac{N_2 \left(\mu_0 \frac{N_1}{l} i_1 \right) A}{i_1} = \mu_0 \frac{N_1 N_2 A}{l}$$