

Closed book. No calculators are to be used for this quiz.


Quiz duration: 10 minutes

Name:


Student ID:

Signature:

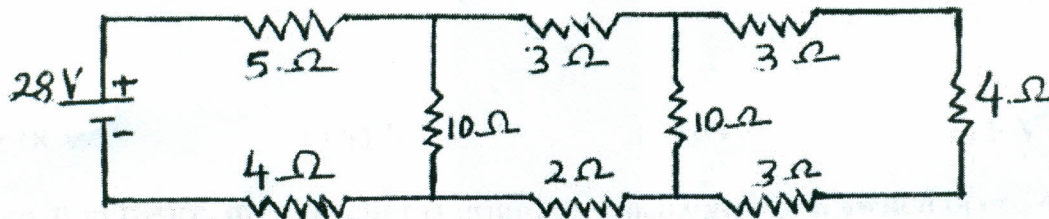Consider the circuit shown in the figure.



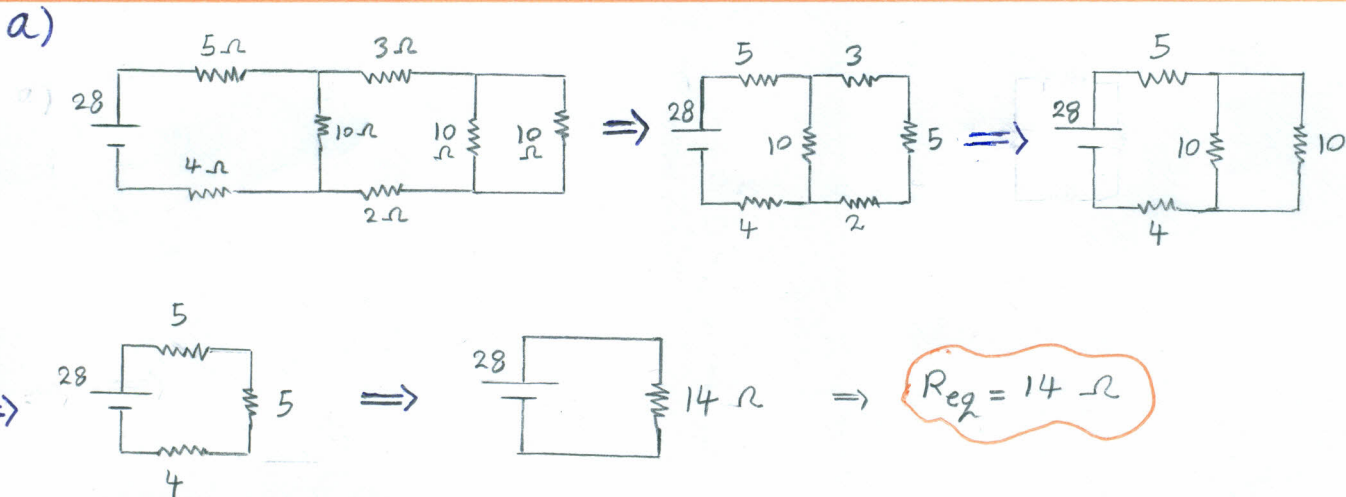- a) Calculate the current in $5\ \Omega$ resistor.
b) What power is dissipated by the entire circuit?



$$I = \frac{V}{R_{eq}} = \frac{28}{14} = 2\text{ A} \Rightarrow \text{the same current passes through } 5\ \Omega \text{ resistor.}$$

b)

$$P = \frac{V^2}{R}$$

$$= \frac{(28)^2}{14}$$

$P = 56\text{ W}$

Closed book. No calculators are to be used for this quiz.


Quiz duration: 10 minutes

Name:

Student ID:

Signature:

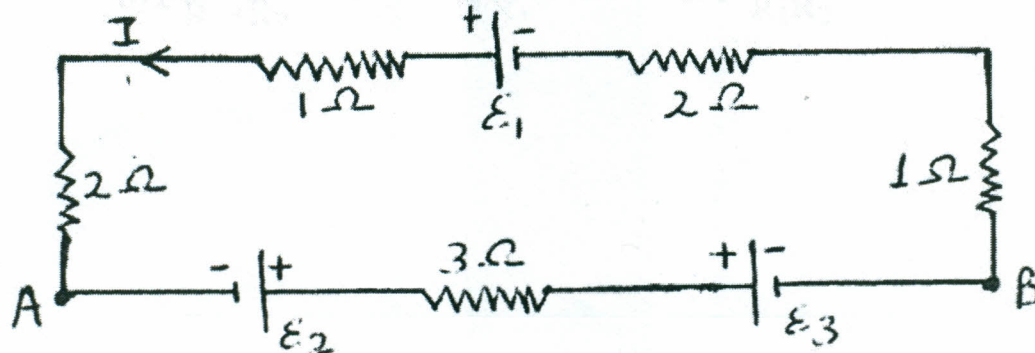Three batteries of emf $\varepsilon_1 = 8V$, $\varepsilon_2 = 12V$, and $\varepsilon_3 = 2V$ are connected with five resistors in a circuit as shown in the figure.



- Find the current I flowing in the circuit.
- Find the potential difference between points A and B, $V_B - V_A$.

a) Start from point A and go around the circuit counterclockwise.

$$V_A + \varepsilon_2 - I \times 3 - \varepsilon_3 - I \times 1 - I \times 2 + \varepsilon_1 - I \times 1 - I \times 2 = V_A$$

$$\Rightarrow 12 - 3I - 2 - I - 2I + 8 - I - 2I = 0$$

$$\Rightarrow 18 - 9I = 0$$

$$\Rightarrow I = \frac{18}{9} = 2 \text{ A} > 0 \Rightarrow \text{The direction of } I \text{ has chosen correctly.}$$

b)

$$V_A + \varepsilon_2 - 3I - \varepsilon_3 = V_B$$

$$\Rightarrow V_B - V_A = 12 - 3 \times 2 - 2$$

$$\Rightarrow V_B - V_A = 4 \text{ V}$$

Closed book. No calculators are to be used for this quiz.

Quiz duration: 10 minutes

Name:

Student ID:

Signature:

A capacitor C that is initially uncharged is connected in series with a resistor R and emf source $\varepsilon = 120\text{V}$. Just after the circuit is completed, the current through the

resistor is $6 \times 10^{-5}\text{A}$. The time constant for the circuit is 10s .

Find the resistance of the resistor and the capacitance of the capacitor.

$$I_0 = 6 \times 10^{-5} \text{ A}$$

at $t=0$ we can ignore capacitor:


$$R = \frac{\varepsilon}{I_0} = \frac{120}{6 \times 10^{-5}}$$

$$\Rightarrow R = 2 \times 10^6 \ \Omega$$

$$\tau = 10 \text{ s}$$

$$\tau = RC \Rightarrow C = \frac{\tau}{R} = \frac{10}{2 \times 10^6}$$
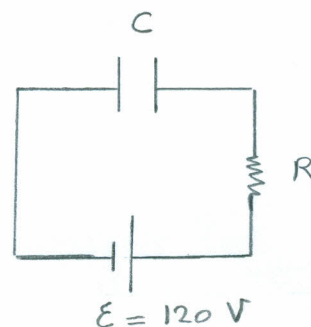
$$\Rightarrow C = 5 \times 10^{-6} \text{ F} = 5 \ \mu\text{F}$$



Closed book. No calculators are to be used for this quiz.


Quiz duration: 10 minutes

Name:

Student ID:

Signature:

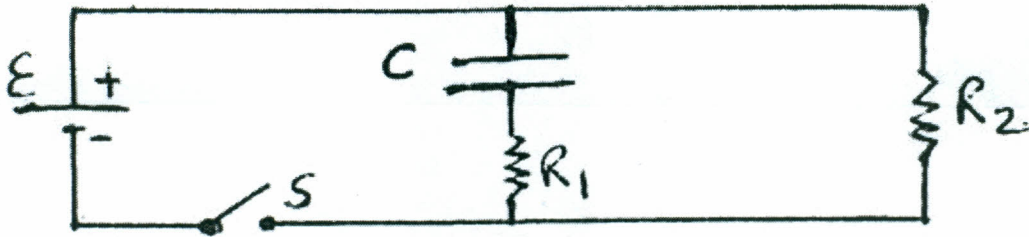In the circuit shown in the figure, the capacitor is originally uncharged with switch open. At $t=0$ the switch is closed.




- What is the current supplied by the emf just after the switch is closed?
- What is the current long time after the switch is closed?

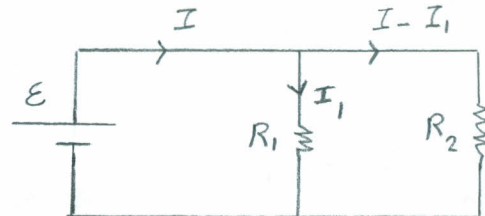a) At $t=0$ we can ignore capacitor and the circuit is like below:


$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$I = \frac{\epsilon}{R_{eq}} = \frac{R_1 + R_2}{R_1 R_2} \epsilon$$



b) As $t \rightarrow \infty$ the capacitor becomes fully charged and $I_1 = 0$, In this case the circuit becomes:

$$I = \frac{\epsilon}{R_2}$$

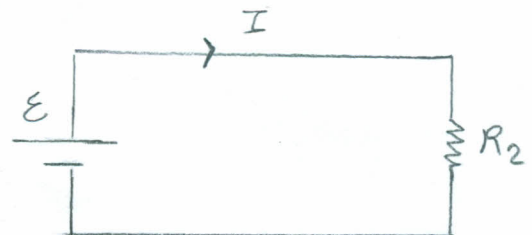

Closed book. No calculators are to be used for this quiz.


Quiz duration: 10 minutes

Name:

Student ID:

Signature:

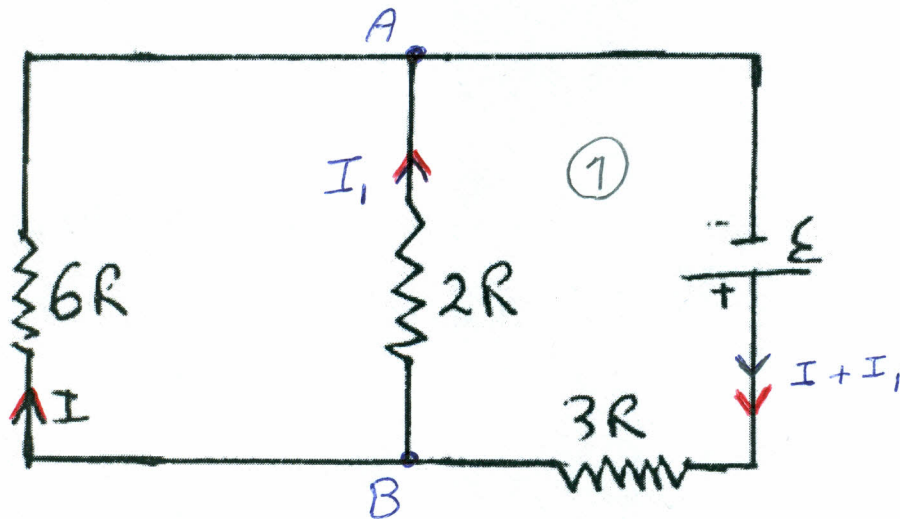In the circuit shown in the figure, if $R=50\Omega$ and $I=20\text{mA}$, determine \mathcal{E} .



Potential difference across resistor $6R$ is:

$$V_{AB} = I(6R) = 20 \times 10^{-3} \times 6 \times 50$$

$$\Rightarrow V_{AB} = 6 \text{ V}$$

$$\Rightarrow I_1 = \frac{V_{AB}}{2R} = \frac{6}{2 \times 50} = 0.06 \text{ A} \Rightarrow I_1 = 60 \text{ mA}$$

$$\Rightarrow I_{\text{total}} = I + I_1 = 80 \text{ mA}$$

$$R_{\text{eq}} = \frac{(6R)(2R)}{6R + 2R} + 3R = \frac{12R}{8} + 3R = \frac{3}{2}R + 3R = 4.5R = 4.5 \times 50$$

$$\Rightarrow R_{\text{eq}} = 225 \Omega$$

$$\mathcal{E} = I_{\text{total}} \cdot R_{\text{eq}} = 80 \times 10^{-3} \times 225 = 18 \text{ V} \Rightarrow \mathcal{E} = 18 \text{ V}$$