

Chapter 26: Direct Current Circuits

Direct current (dc) circuits:


Current, electric potential in the circuit have no time dependence

5V DC Power Supply

3V DC Power Supply


Alternating current (ac) circuits:

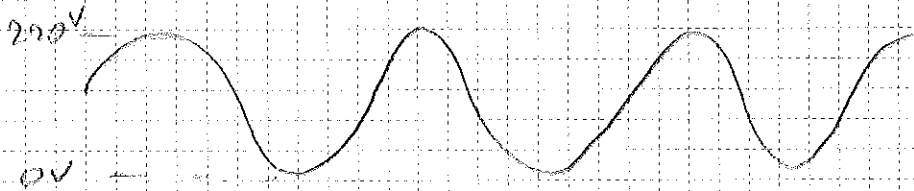Current, electric potential in the circuit oscillates with time.




230V AC Voltage

Resistors In Series and Parallel:

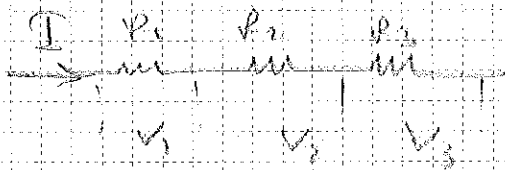

$$\begin{aligned}
 V &= V_1 + V_2 + V_3 \\
 &= I R_1 + I R_2 + I R_3 \\
 &= I (R_1 + R_2 + R_3) \\
 &\quad R_{eq}
 \end{aligned}$$

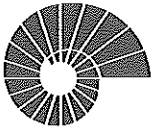$R_{eq} = R_1 + R_2 + R_3 + \dots$
 Equivalent resistance of resistors connected in series



$I = I_1 + I_2 + I_3$ ← conservation of charge flow!

$V_1 = V_2 = V_3 = V$


$I = I_1 + I_2 + I_3$

$= \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) = \frac{V}{R_{eq}}$

$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$

Equivalent resistance of resistors connected in parallel.

26.2 Kirchoff's Rules:

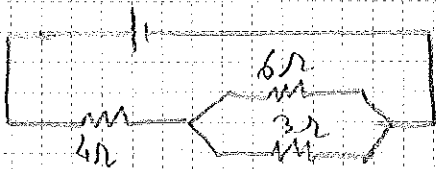

Many practical resistor networks cannot be solved using the simple series-parallel resistor reduction techniques.


Kirchoff's Rules help analyzing complicated circuits.

Kirchoff's Rules:

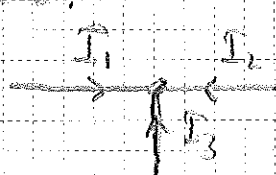(i) The algebraic sum of the currents into any junction is equal to zero.


$\sum I = 0$, junction rule.

Junction: A point in the circuit where three or more conductors meet.




$I_1 + I_2 + I_3 = 0$ or $I_3 = -(I_1 + I_2)$


flows in the opposite direction

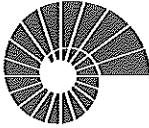

Prob 26.92

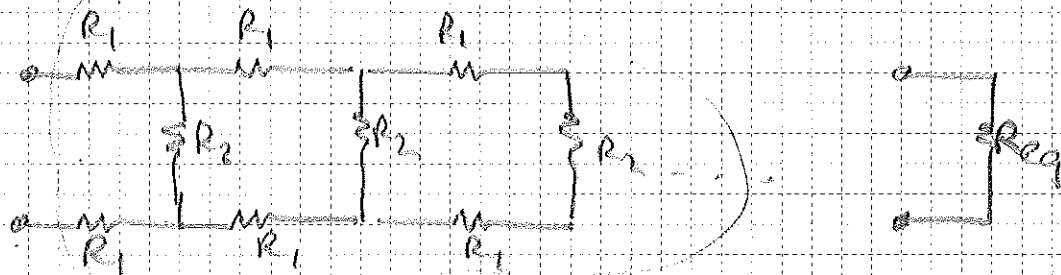

Equivalent resistance?

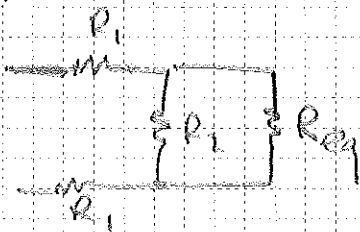

$$\frac{1}{R_1} + \frac{1}{R_{eq}} = \frac{R_2 + R_{eq}}{R_{eq} R_2}$$

$$\Rightarrow R_{eq} = 2R_1 + \frac{R_1 R_{eq}}{R_{eq} + R_2}$$

$$\Rightarrow (R_{eq} - 2R_1)(R_{eq} + R_2) = R_{eq} R_2$$

$$\Rightarrow R_{eq}^2 + R_{eq}(R_2 - 2R_1 - R_2) - 2R_1 R_2 = 0$$

$$R_{eq}^2 - 2R_1 R_{eq} - 2R_1 R_2 = 0$$


$$\Rightarrow R_{eq} = \frac{2R_1 \pm \sqrt{4R_1^2 + 8R_1 R_2}}{2} = R_1 \pm \sqrt{R_1^2 + 2R_1 R_2}$$

$> R_1$

$$\Rightarrow \text{Solution is } R_{eq} = R_1 + \sqrt{R_1^2 + 2R_1 R_2}$$

$$R_{eq} / R_1 = \sqrt{R_1^2 + 2R_1 R_2} \quad \checkmark$$

is not
a physical
solution

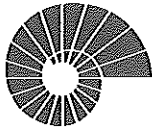


(1) The algebraic sum of the potential differences in any loop (associated with emfs, and resistive elements) must equal zero.

$$\sum V = 0, \text{ Kirchhoff's Loop Rule}$$

Loop: Any closed conducting path in the circuit.

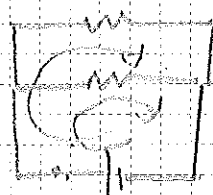
This is clear because electrostatic force is conservative.



$$W_{\text{anc}} = -\Delta U = U_f - U_i = 0$$

How to solve circuits using Kirchhoff's laws:

Given a circuit:

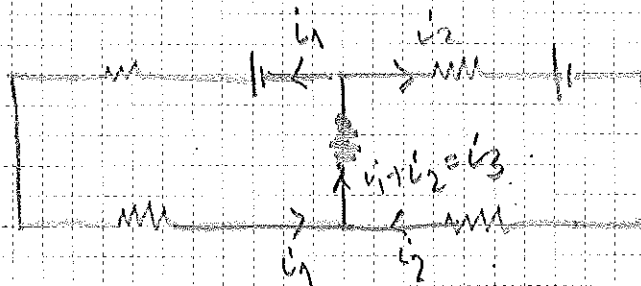


- Label currents with their directions. The directions need not be the correct directions.


Write the Kirchhoff's Junction Law in the junctions:

$$i_1 + i_2 = i_3$$

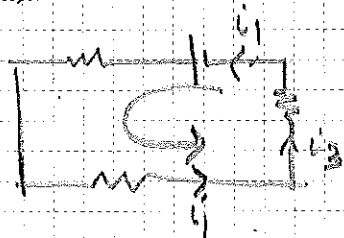Choose any closed loop in the circuit, designate a direction of travel.




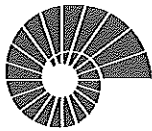Travel around the loop adding potential differences due to different elements.




Potential differences due to different elements:

emf

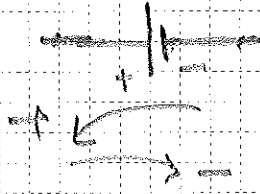

emf is counted + if you traverse from - to +.
emf is counted - if you traverse from + to -.

Resistance

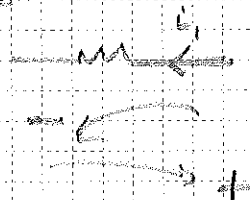

Resistance is - if you traverse in the same direction as current, but Resistance is + if you traverse in the direction opposite to current.




$$\sum V_a + E_1 - i_2 R_1 - i_3 R_3 = \sum V_a$$

$$E_1 - i_2 R_1 - i_3 R_3 = 0$$

Write as many linearly independent equations as the number of currents to solve for the circuit.

Ex 26.4; Consider the circuit:

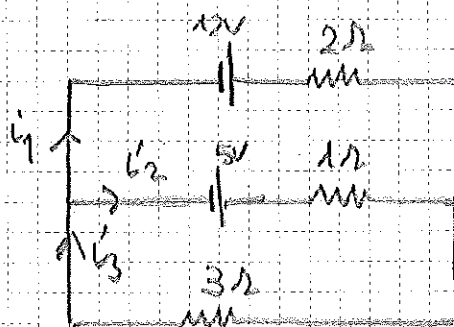


What are the currents?


(i) Label currents with directions

(ii) Apply Kirchhoff's Junction Law

$$i_1 + i_2 = i_3$$

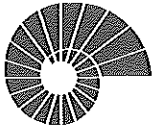


Apply Kirchoff's Loop Law:

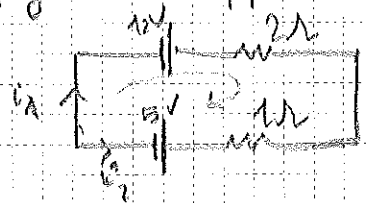


$$12 - 2i_1 + i_2 - 5 = 0$$

$$7 - 2i_1 + i_2 = 0$$

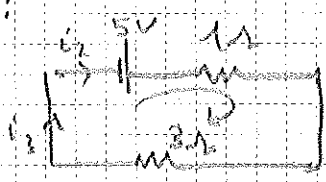

$$5 - i_2 - 3i_3 = 0$$

$$5 - i_2 - 3i_3 = 0$$

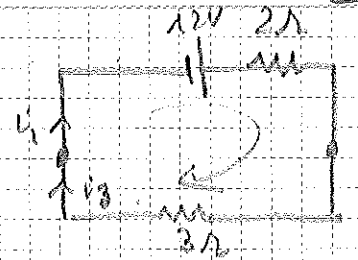

$$12 - 2i_1 - 3i_3 = 0$$

$$12 - 2i_1 - 3i_3 = 0$$

2 linearly independent equations,

Add the first 2:

$$7 - 2i_1 + i_2 = 0$$

$$5 - i_2 - 3i_3 = 0$$

$$12 - 2i_1 - 3i_3 = 0$$

3. Use the equations:

$$i_1 + i_2 = i_3$$

$$7 - 2i_1 + i_2 = 0$$


$$5 - i_2 - 3i_3 = 0 \Rightarrow 5 - i_2 - 3i_1 + 3i_2 = 5 - 3i_1 - 4i_2 = 0$$

$$\Rightarrow i_2 = \frac{5}{4} - \frac{3}{4}i_1$$

$$\Rightarrow 7 - 2i_1 + \frac{5}{4} - \frac{3}{4}i_1 = \frac{33}{4} - \frac{11}{4}i_1 = 0 \Rightarrow i_1 = 3A$$



$$i_2 = \frac{5}{4} - \frac{3}{4}i_1 = \frac{5}{4} - \frac{9}{4} = -1A$$

$$i_3 = 2A$$

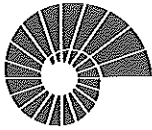

Prob 26.72

Show that $X = \frac{MP}{N}$

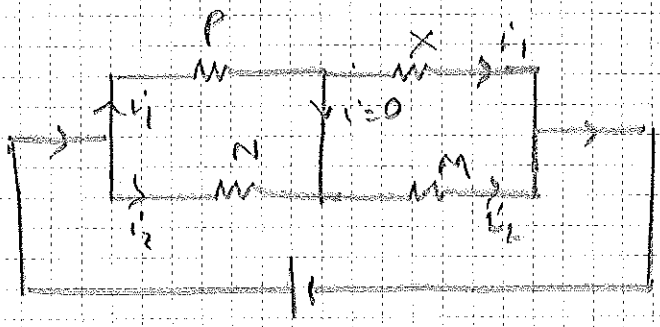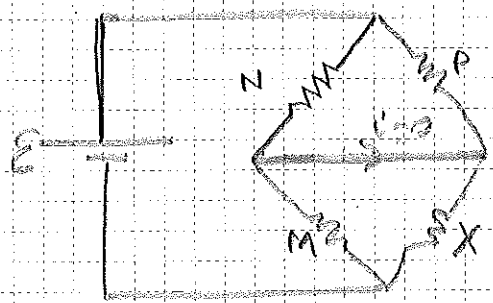

$$i_1 P = i_2 N \Rightarrow \frac{i_1}{i_2} = \frac{N}{P}$$

$$i_1 X = i_2 M \Rightarrow \frac{i_1}{i_2} = \frac{M}{X}$$

$$\frac{M}{X} = \frac{N}{P} \Rightarrow \boxed{X = \frac{MP}{N}}$$

Wheatstone Bridge

Ex 26.63


Find the current in each resistor.



3 Unknowns $i_1, i_2, i_3 \Rightarrow$ write 3 equations using Kirchhoff's Loop Law:



$$-i_2 + i_3 + i_1 = 0$$

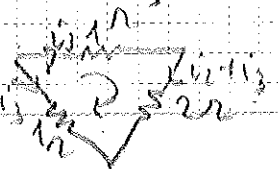

$$-2(i_2 + i_3) + i_1 + i_3 - i_3 = 0$$



$$-i_2 - 2(i_2 + i_3) + 13 = 0$$

$$\Rightarrow i_1 - i_2 + i_3 = 0$$

$$i_1 - 2i_2 - 4i_3 = 0$$

$$-3i_2 - 2i_3 = -13$$

$$2i_1 - i_3 = 13 \Rightarrow i_3 = 2i_1 - 13$$


$$\Rightarrow i_1 - i_2 + 2i_1 - 13 = 0 \Rightarrow 3i_1 - i_2 = 13$$

$$i_1 - 2i_2 - 4(2i_1 - 13) = 0 \Rightarrow -7i_1 - 2i_2 = -52$$

$$= 13i_1 = -52 - 2i_2 = 78 \Rightarrow i_1 = 6A$$


$$i_2 = 3i_1 - 13 = 18 - 13 = 5A //$$

$$i_3 = 2i_1 - 13 = 12 - 13 = -1A //$$

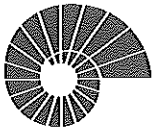

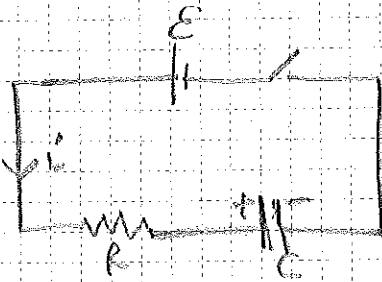2.6.4 R-C Circuits

Circuits that involve charging or discharging of capacitors.



Charging a Capacitor:

Consider the capacitor being initially uncharged.

Then at time $t=0$ the switch is closed.

Capacitor then starts being charged.

$$C = \frac{Q}{V} \Rightarrow Q = CV \Rightarrow \frac{dQ}{dt} = C \frac{dV}{dt} = i$$

$$E - iR - V = 0 \Rightarrow E - R \frac{dV}{dt} - V = 0$$



$$RC \frac{dV}{dt} + V = E \Rightarrow \int_0^V \frac{dV}{E-V} = \int_0^t \frac{dt}{RC}$$



$$\Rightarrow -\ln(E-V) \Big|_0^V = + \frac{t}{RC} \Rightarrow -\ln(E-V) - \ln(E) = -\frac{t}{RC}$$

$$\Rightarrow -\ln\left(\frac{E-V}{E}\right) = \frac{t}{RC} \Rightarrow \frac{E-V}{E} = e^{-t/RC} \Rightarrow \boxed{V = E - Ee^{-t/RC}}$$

$$Q = CV \Rightarrow Q(t) = CE(1 - e^{-t/RC}) //$$

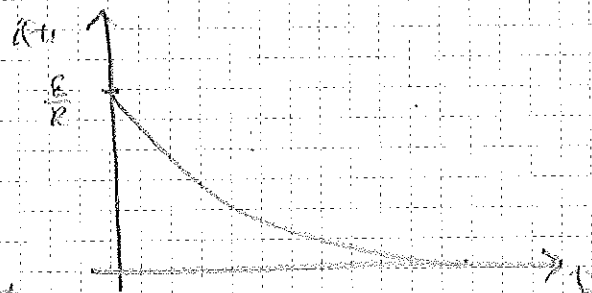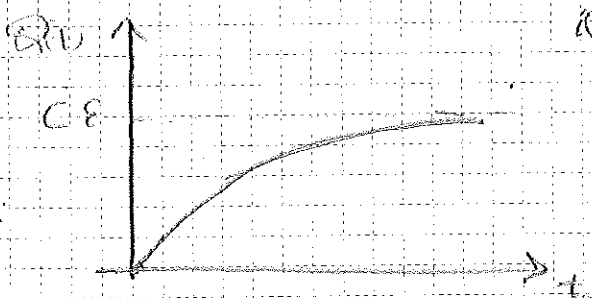
$$i = \frac{dQ}{dt} = CE \left(\frac{1}{RC} e^{-t/RC} \right) = \frac{E}{R} e^{-t/RC} //$$



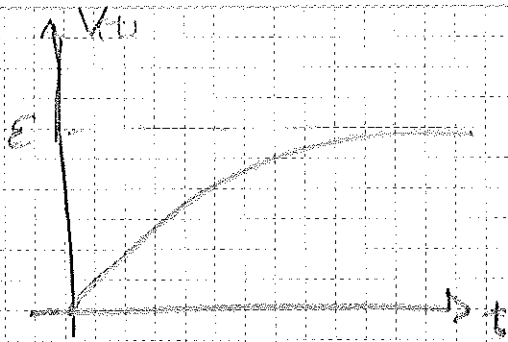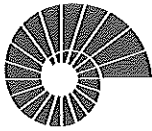

At time $t = RC$, current drops to $\frac{1}{e}$ of its initial value
 $\tau = RC$ is called the time constant of the RC circuit.

Discharging a Capacitor:

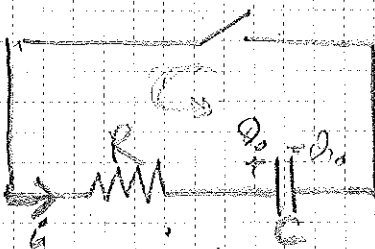

Consider an initially charged capacitor.
 At time $t=0$ the switch is closed.

$$C = \frac{Q(t)}{V(t)}$$



$$V(t) + i(t)R = 0 \Rightarrow \frac{Q(t)}{C} + \frac{dQ(t)}{dt}R = 0$$

$$\Rightarrow \frac{dQ(t)}{dt} = -\frac{Q(t)}{RC} \Rightarrow \ln Q \Big|_{Q_0}^Q = -\frac{t}{RC} \Big|_0^t$$

$$\Rightarrow \ln \left(\frac{Q}{Q_0} \right) = -\frac{t}{RC} \Rightarrow \boxed{Q = Q_0 e^{-t/RC}}$$

$$V(t) = \frac{Q(t)}{C} = \frac{Q_0}{C} e^{-t/RC}$$
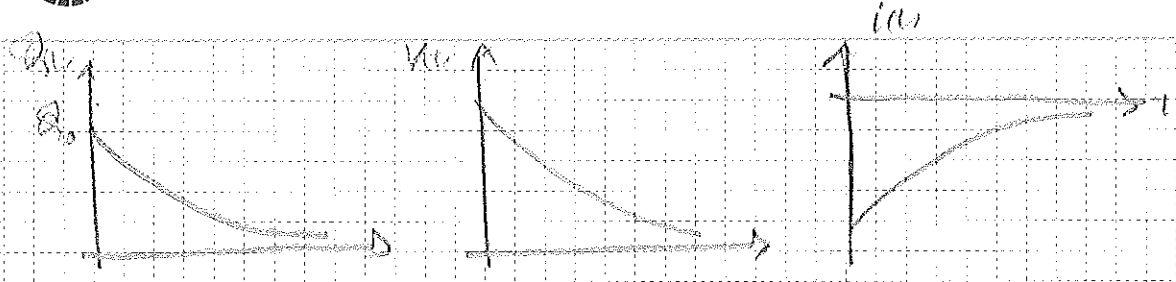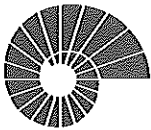
$$i(t) = -\frac{dQ(t)}{dt} = \frac{Q_0}{RC} e^{-t/RC}$$




Time constant: $\tau = RC$

time at which the stored charge drops to $\frac{1}{e}$ of its initial value.

Energy Considerations

In charging of a capacitor:

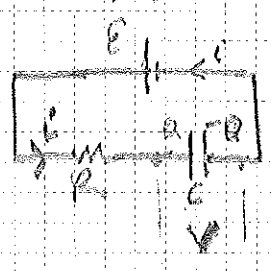

Ei , rate at which the battery delivers energy to the circuit.

$$Ei = i^2 R + V \frac{dQ}{dt} = i^2 R + \frac{Q}{C} i$$

Total energy supplied by the battery during charging of the capacitor:

$$\int R i^2 dt = \int E \frac{dQ}{dt} dt = \int E dQ = E Q_0$$

Final charge of the capacitor


Total energy stored in the capacitor

$$U = \frac{1}{2} Q_0 V = \frac{1}{2} Q_0 E$$


Half of the energy is stored in the capacitor
Half is dissipated in the resistor.

$$U = \int \frac{Q}{C} i dt = \int \frac{Q}{C} \frac{dQ}{dt} dt = \int \frac{Q}{C} dQ = \frac{1}{2C} Q^2 = \frac{1}{2} \frac{Q_0^2}{C}$$

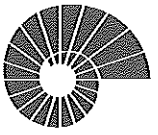\therefore This does not depend on the values of R , E and C .



Discharging of a Capacitor

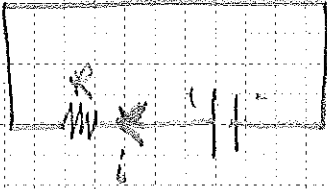

Power dissipated by the capacitor:

$$i \frac{dQ}{dt} = i^2 R$$




$$\int i \frac{dQ}{dt} dt = \int - \frac{dQ}{C} = - \frac{1}{2C} Q^2 \Big|_{Q_0}^0 = + \frac{1}{2C} Q_0^2 \leftarrow \text{Total energy}$$

Capacitor delivers to the circuit.

$$\int i^2 R dt = \int \frac{Q_0^2}{RC^2} e^{-2t/RC} R dt = \frac{Q_0^2}{RC^2} \int e^{-2t/RC} dt$$


$$= \frac{Q_0^2}{RC^2} \left[-\frac{RC}{2} e^{-2t/RC} \right]_0^\infty = \frac{Q_0^2}{C} \left(\frac{-1}{2} \right) (0 - 1) = \frac{Q_0^2}{2C}$$

Energy dissipated in the resistor

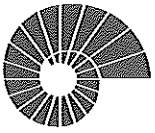

RC - Circuits:

Charging a capacitor

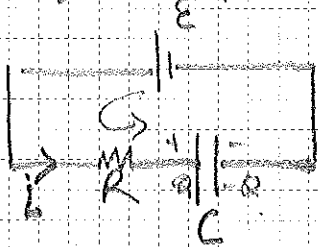


$\frac{dQ}{dt} = i$ direction is important

$$\varepsilon - iR = \frac{Q}{C} = 0 \Rightarrow \varepsilon = \frac{dQ}{dt} R + \frac{Q}{C}$$

$$\Rightarrow Q = C\varepsilon (1 - e^{-t/RC})$$

$$i = \frac{dQ}{dt} = \frac{\varepsilon}{R} e^{-t/RC}$$

Discharging a capacitor:

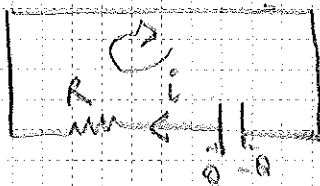

$$i = \frac{dQ}{dt}$$

$$\Rightarrow -iR + \frac{Q}{C} = 0$$


$$\Rightarrow -\frac{dQ}{dt} R = -\frac{Q}{C} \Rightarrow Q = Q_0 e^{-t/RC}$$

$$V = \frac{Q}{C} = \frac{Q_0}{C} e^{-t/RC}$$

$$i(t) = \frac{V_0}{R} = \frac{Q_0}{RC} e^{-t/RC}$$

RC - time constant

Energy Considerations:

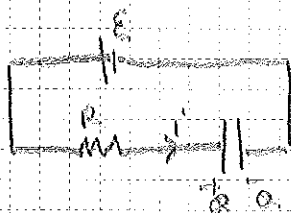

rate of energy dissipated is: $i^2 R + Vi$

rate of energy delivered is: εi

stored in the capacitor: $U = \int V dq = \int \frac{Q}{C} dq = \frac{1}{C} \frac{Q^2}{2}$

$$= \frac{1}{2} Q_0 V_0 = \frac{1}{2} Q_0 \varepsilon$$

delivered by ε : $\int \varepsilon dq = \int \varepsilon dq = \varepsilon Q_0$