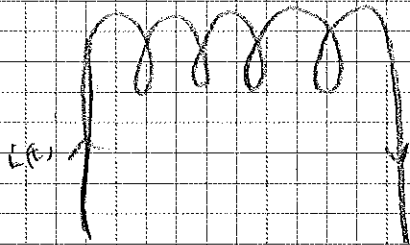


## Chapter 30: Inductance

Consider a copper wire wrapped to form a coil



Changing current in the coil will induce an emf in the coil itself.

Such a coil is called an inductor and the relationship between the current and emf reveals the inductance,

$$\Rightarrow E = -N \frac{d\Phi_B}{dt}$$


Total induced emf  
Faraday's Law

$$i(t) = \frac{N}{L} \Phi_B \Rightarrow \frac{d\Phi_B}{dt} = \frac{L}{N} \frac{di}{dt}$$

we define  $L = \frac{N \Phi_B}{i}$  as self-inductance


with this definition, Faraday's law can be written as

$$E = -L \frac{di}{dt}$$

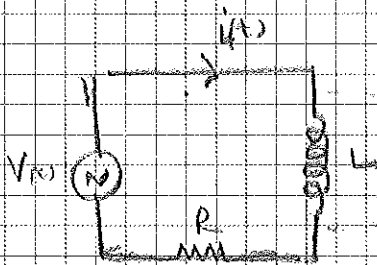


$$V_{ab} = L \frac{di}{dt}$$

Inductor opposes to the variations in the current flowing through the circuit.

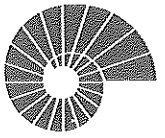

Ex. 30.3:

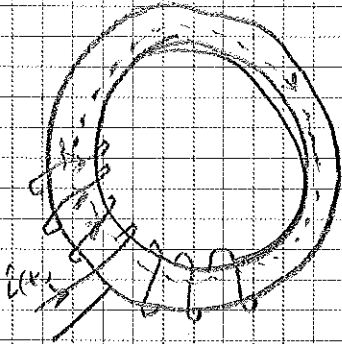

A toroidal solenoid with cross-sectional area  $A$  and mean radius  $r$  is closely wound with  $N$  turns.  
What is  $L$ ?

Use  $L = \frac{N\Phi_B}{i}$

$\vec{B}$  is along the tangential direction with constant magnitude.

Remember:  $\oint \vec{B} \cdot d\vec{\ell} = B(2\pi r) = \mu_0 Ni \Rightarrow B(2\pi r) = \frac{\mu_0 Ni}{2\pi r}$

$\Rightarrow \Phi_B = \int \vec{B}(r) \cdot d\vec{A} \approx A \frac{\mu_0 Ni}{2\pi r}$  — mean radius


flux through one winding

$\Rightarrow L = \frac{N\Phi_B}{i} = \frac{N}{i} \frac{A \mu_0 Ni}{2\pi r} = \frac{\mu_0 N^2 A}{2\pi r} //$


Mutual Inductance:

A changing current in one coil can also induce an emf in another coil.

Consider two coils:

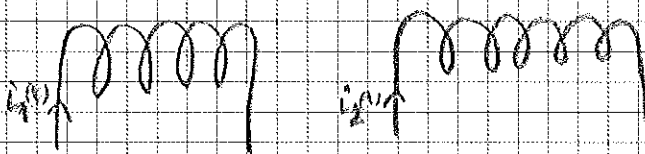

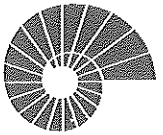$\mathcal{E}_2(t) = -N_2 \frac{d\Phi_{21}}{dt}$



We define the mutual inductance:


$$M_{21} = \frac{N_2 \Phi_{21}}{I_1}, \text{ mutual inductance}$$

compare with  $(L = \frac{N^2 \Phi}{I})$

$$\Rightarrow \boxed{E_2(t) = -M_{21} \frac{dI_1}{dt}}$$

induced emf in coil 2 due to changing current in coil 1.

Ex 32.1:

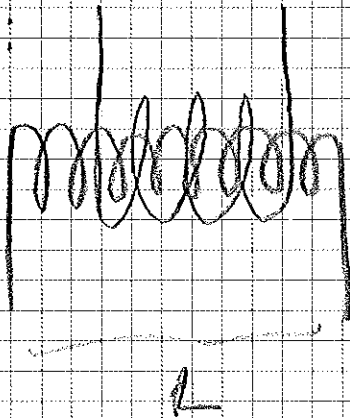

A long solenoid with length  $L$  and cross-sectional area  $A$  is closely wound with  $N_1$  turns.


A coil with  $N_2$  turns surrounds the first coil.

What is the mutual inductance?

$$M_{21} = \frac{N_2 \Phi_{21}}{I_1}$$


$$\begin{aligned} \Phi_{21} &= BA, & B &= \mu_0 \mu_r \frac{N_1}{L} I_1 \\ &= \mu_0 \mu_r \frac{N_1}{L} I_1 A \end{aligned}$$
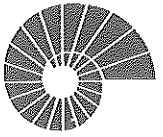
$$\Rightarrow \boxed{M_{21} = \mu_0 \frac{N_1 N_2}{L} A}$$



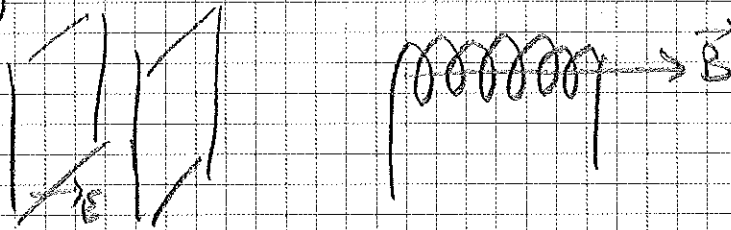
### 30.3 Magnetic Field Energy:

An inductor carrying current has energy stored in it.  
In a capacitor an electric field is built up due to the stored energy.



In an inductor magnetic field is built up due to the stored energy.

Consider an inductor in a circuit:

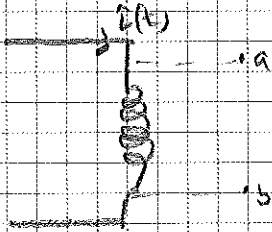

$$V_{ab} = L \frac{di}{dt}$$

Power stored in the inductor

$$\hookrightarrow P = V_{ab} i = L i \frac{di}{dt} = \frac{dU}{dt}$$

$$\Rightarrow \int_0^U dU = \int_0^L L i di$$


$$\Rightarrow \boxed{U = \frac{1}{2} Li^2}$$

Energy stored in an inductor.

→ When current increases from 0 to  $I$  energy is stored in the inductor.

When current decreases from  $I$  to 0 inductor acts as a source supplying total energy of  $\frac{1}{2} Li^2$ .

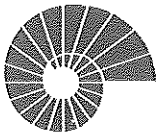When a steady current flows through an inductor, no energy flows into or out from the inductor.



Energy stored in the inductor can be viewed as stored in the magnetic field.

⇒ Consider the ideal toroidal solenoid

$$L = \frac{\mu_0 N^2 A}{2\pi r}$$

$$\Rightarrow U = \frac{1}{2} L i^2 = \frac{1}{2} \frac{\mu_0 N^2 A}{2\pi r} i^2$$

This energy is localized in a volume of  $2\pi r A$

$$\Rightarrow \text{energy density } u = \frac{U}{2\pi r A} = \frac{1}{2} \mu_0 \frac{N^2 i^2}{(2\pi r)^2}$$


$$B = \frac{\mu_0 N i}{2\pi r} \text{ inside the toroid } \Rightarrow \frac{N^2 i^2}{(2\pi r)^2} = \frac{B^2}{\mu_0^2}$$

$$\Rightarrow \boxed{u = \frac{B^2}{2\mu_0}}$$

Magnetic energy density in vacuum


This is in general true. For a material with magnetic permeability  $\mu$ , the energy density is:

$$u = \frac{B^2}{2\mu}$$

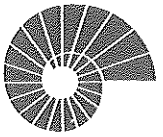
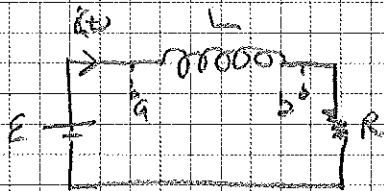
### 30.4 RL Circuit:

A circuit that includes a resistor and an inductor.



What is  $i(t)$ ?

$$E = V_{ab} + V_{bc} \quad \text{"Kirchoff's Loop Rule"}$$

$$E = L \frac{di}{dt} + iR \quad \text{First order DE.}$$


$$\Rightarrow \frac{E}{L} - i \frac{R}{L} = \frac{di}{dt}$$

$$\Rightarrow \int \frac{di}{E - iR} = \int \frac{dt}{L} \Rightarrow -\frac{1}{R} \ln(E - iR) \Big|_0^{i(t)} = \frac{t}{L}$$

$$\Rightarrow \ln\left(\frac{E - i(t)R}{E}\right) = -\frac{R}{L}t$$


$$\Rightarrow 1 - i(t) \frac{R}{E} = e^{-\frac{R}{L}t}$$
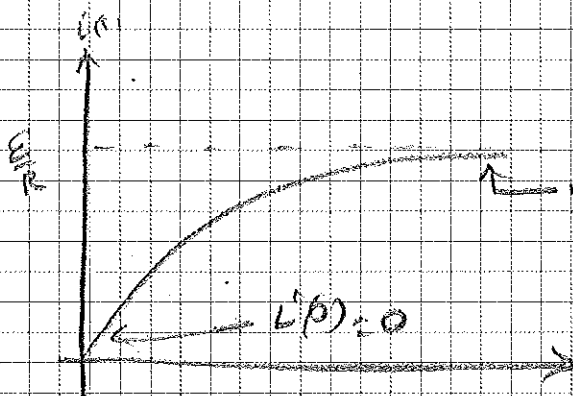
$$\boxed{i(t) = \frac{E}{R} \left(1 - e^{-\frac{R}{L}t}\right)}$$




inductor behaves like a short circuit

The time constant is  $\left| \tau = \frac{L}{R} \right|$

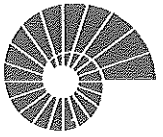


Energy wise:

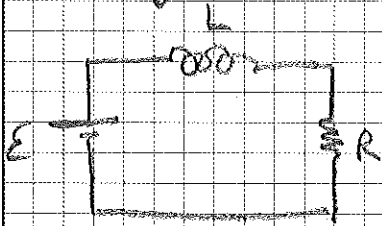


$$\begin{aligned}
 i^2 R + L i \frac{di}{dt} &= \\
 &= \frac{E^2}{R^2} R \left(1 - e^{-\frac{R}{L}t}\right)^2 + \cancel{L} \frac{E}{R} \left(1 - e^{-\frac{R}{L}t}\right) \frac{E}{R} \frac{R}{L} e^{-\frac{R}{L}t} \\
 &= \frac{E^2}{R} \left\{ 1 - 2e^{-\frac{R}{L}t} + e^{-\frac{2R}{L}t} + e^{-\frac{R}{L}t} \right\} \\
 &= \frac{E^2}{R} \left(1 - e^{-\frac{R}{L}t}\right) = \underline{\underline{E i}}
 \end{aligned}$$

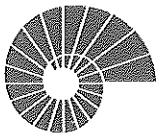$\Rightarrow E i = \underbrace{i^2 R}_{\substack{\text{power supplied} \\ \text{by the battery}}} + \underbrace{L i \frac{di}{dt}}_{\substack{\text{power} \\ \text{dissipated} \\ \text{in } R}} = \underbrace{E i}_{\text{power stored in } L}$


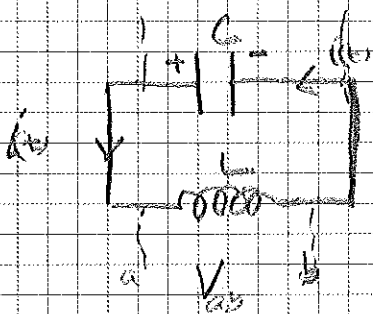
### 30.5 L-C Circuit:

A circuit containing an <sup>ideal</sup> inductor and capacitor.



There is no energy dissipating component in the circuit so the energy will be oscillating between the capacitor and inductor.

$$V_C = V_L \Rightarrow \frac{Q}{C} = L \frac{di}{dt}$$

$$L \frac{di}{dt} = - \frac{dQ}{dt} \Rightarrow \frac{Q}{C} = -L \frac{d^2Q}{dt^2} \Rightarrow \boxed{\frac{d^2Q}{dt^2} = -\frac{1}{LC} Q}$$

solutions:  $Q(t) = A \cos\left(\frac{1}{\sqrt{LC}} t\right) + B \sin\left(\frac{1}{\sqrt{LC}} t\right)$

A, B are constants which depend on the initial conditions.

For example if the initial conditions are:  $Q(0) = Q_0$ ,  $i(0) = 0$

$$\Rightarrow Q(0) = A = Q_0$$

$$i(0) = - \frac{dQ}{dt} \Big|_{t=0} = - \left\{ \frac{1}{\sqrt{LC}} B \right\} = 0 \Rightarrow B = 0$$

$$\Rightarrow \boxed{Q(t) = Q_0 \cos\left(\frac{1}{\sqrt{LC}} t\right)}$$


$\omega = \frac{1}{\sqrt{LC}}$ , angular frequency of oscillations

Power stored in L:  $\frac{1}{2} L i^2 = \frac{1}{2} L \frac{Q_0^2}{LC} \sin^2\left(\frac{1}{\sqrt{LC}} t\right) = \frac{1}{2} \frac{Q_0^2}{C} \sin^2\left(\frac{1}{\sqrt{LC}} t\right)$

Power stored in C:  $\frac{1}{2} C Q^2 = \frac{1}{2} \frac{Q_0^2}{C} \cos^2\left(\frac{1}{\sqrt{LC}} t\right)$
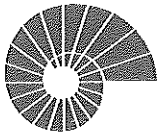
$$\Rightarrow \boxed{P_L + P_C = \frac{1}{2} \frac{Q_0^2}{C} = \text{constant}}$$





Ex 30.9: A 300V dc power is used to charge a  $27\mu\text{F}$  capacitor. After the capacitor is fully charged, it is disconnected from the power supply, and connected across a  $10\text{mH}$  inductor.

- a) Frequency and period of oscillations?
- b) Capacitor charge and the circuit current  $1.2\text{ms}$  after the inductor and capacitor are connected?

$$a) \omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10 \times 10^{-3} \times 27 \times 10^{-6}}} = 2.0 \times 10^3 \text{ rad/s}$$


$$\Rightarrow f = \frac{\omega}{2\pi} = 320 \text{ Hz}$$

$$T = \frac{1}{f} = 3.1 \text{ ms}$$

$$b) Q_0 = CV = 27 \times 10^{-6} \times 300 = 8.1 \times 10^{-4} \text{ C}$$

$$\begin{aligned} \Rightarrow Q(t) &= Q_0 \cos(\omega t) \Rightarrow Q(1.2 \text{ ms}) = 8.1 \times 10^{-4} \cos(2.0 \times 10^3 \times 1.2 \times 10^{-3}) \\ &= 8.1 \times 10^{-4} \cos(2.4) \\ &= -5.5 \times 10^{-4} \text{ C} \end{aligned}$$
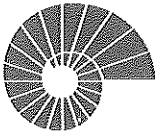
$$\begin{aligned} i(t) &= -\frac{dQ}{dt} = Q_0 \omega \sin \omega t \Rightarrow i(1.2 \text{ ms}) = 8.1 \times 10^{-4} \times 2 \times 10^3 \sin(2.4) \\ &= 10 \text{ A} \end{aligned}$$



$$Q(t) = e^{-\frac{R}{2L}t} \left\{ A e^{\frac{1}{2}\sqrt{\frac{R^2}{L^2} - \frac{4}{LC}}t} + B e^{-\frac{1}{2}\sqrt{\frac{R^2}{L^2} - \frac{4}{LC}}t} \right\}$$

There are 3 regimes of operation depending on the values of  $R, L, C$ .

(i)  $\frac{R^2}{L^2} = \frac{4}{LC} \Rightarrow Q(t) = A e^{-\frac{R}{2L}t}$ , critically damped case


(ii)  $\frac{R^2}{L^2} > \frac{4}{LC} \Rightarrow$  overdamped case


(iii)  $\frac{R^2}{L^2} < \frac{4}{LC} \Rightarrow$  under damped case

$$Q(t) = e^{-\frac{R}{2L}t} \left\{ A e^{\frac{1}{2}\sqrt{\frac{4}{LC} - \frac{R^2}{L^2}}t} + B e^{-\frac{1}{2}\sqrt{\frac{4}{LC} - \frac{R^2}{L^2}}t} \right\}$$


oscillations
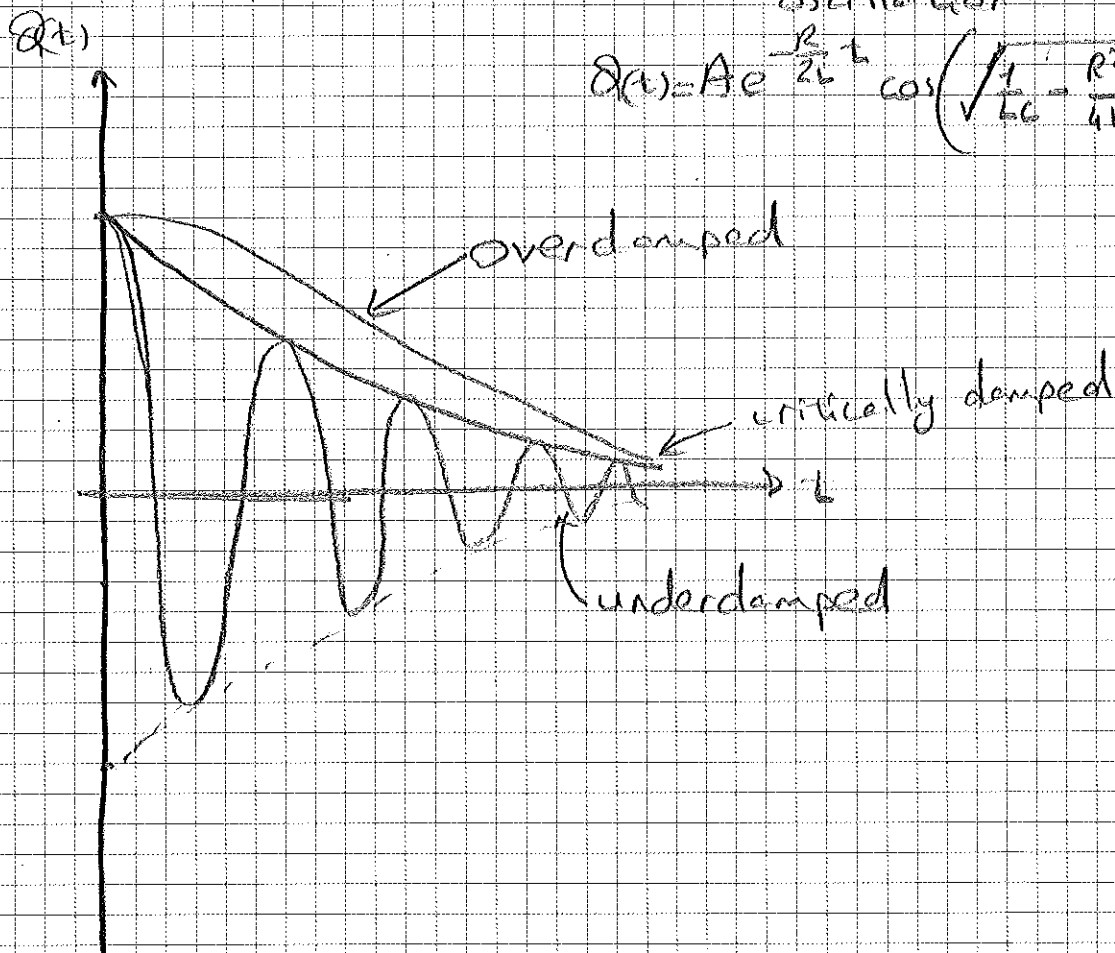
$$Q(t) = A e^{-\frac{R}{2L}t} \cos\left(\sqrt{\frac{4}{LC} - \frac{R^2}{L^2}}t + \phi\right)$$



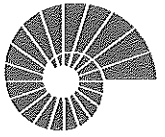

30.6. R-L-C Circuit

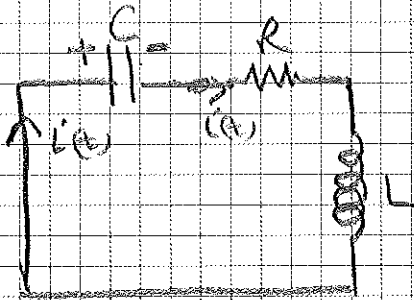

This time there is an energy dissipating term in the circuit. So, the initial energy stored in the C (or L) will reach to 0 at large times.

$$V_C + iR = -V_L \Rightarrow \frac{Q}{C} + iR = -L \frac{di}{dt}$$

$$i = \frac{dQ}{dt} \Rightarrow L \frac{d^2Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = 0$$

$$\Rightarrow \frac{d^2Q}{dt^2} + \frac{R}{L} \frac{dQ}{dt} + \frac{Q}{LC} = 0, \text{ 2nd order differential equation}$$


We try solutions of the form:

$$Q(t) = Ae^{kt} \Rightarrow k^2 + \frac{R}{L}k + \frac{1}{LC} = 0 \quad k_1, k_2$$


$$\Rightarrow k = \frac{-\frac{R}{L} \pm \sqrt{\frac{R^2}{L^2} - \frac{4}{LC}}}{2} = -\frac{R}{2L} \pm \frac{1}{2} \sqrt{\frac{R^2}{L^2} - \frac{4}{LC}}$$

General solution:  $Q(t) = Ae^{k_1 t} + Be^{k_2 t}$
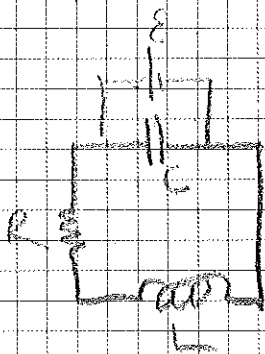
$$Q(t) = e^{-\frac{R}{2L}t} \left\{ A e^{\frac{1}{2} \sqrt{\frac{R^2}{L^2} - \frac{4}{LC}} t} + B e^{-\frac{1}{2} \sqrt{\frac{R^2}{L^2} - \frac{4}{LC}} t} \right\}$$



In the circuit we first charge the capacitor using a battery. Then we disconnect the battery from the circuit.

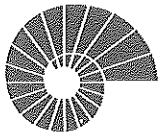

Ex 30.11: What is the R value required to give an R-L-C circuit of frequency that is  $\frac{1}{2}$  of the undamped freq.?

Underdamped frequency

$$\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$


Undamped frequency, R=0

$$\sqrt{\frac{1}{LC}}$$

$$\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} = \frac{1}{2} \sqrt{\frac{1}{LC}} \Rightarrow \frac{1}{LC} - \frac{R^2}{4L^2} = \frac{1}{4} \frac{1}{LC}$$

$$\Rightarrow \frac{R^2}{4L^2} = \frac{3}{4} \frac{1}{LC} \Rightarrow R^2 = 3 \frac{L}{C} \Rightarrow R = \sqrt{\frac{3L}{C}}$$

Prob. 30.73:

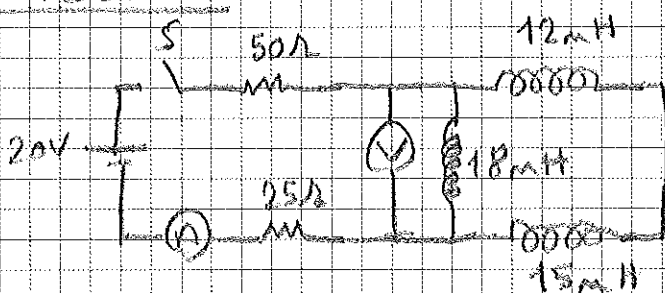

S has been open for a long time. S is suddenly closed.


- What are the readings in A and V just after the switch is closed?
  - What " " " " after a long time?
  - " " " " at  $t = 0.115 \text{ ms}$ ?
- b) As  $t \rightarrow \infty$  all inductors behave like short circuits.

$$\rightarrow V = 0, \quad A = \frac{20V}{75\Omega}$$


$$c) \text{ At } t=0 \quad A=0, \quad V=20V$$

$$e) \quad \frac{L_1}{100\Omega} \quad \frac{L_2}{100\Omega} \quad \equiv \quad \frac{L_1 + L_2}{100\Omega}$$

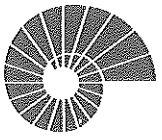
$$V = L_1 \frac{di_1}{dt} = L_2 \frac{di_2}{dt} = L_{eq} \frac{d(i_1 + i_2)}{dt}$$



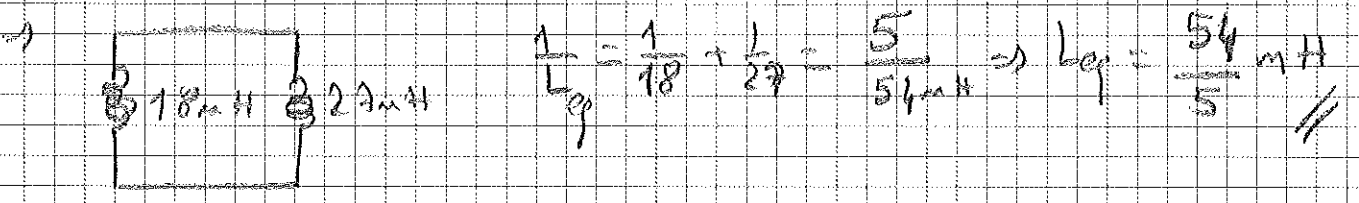
$$\Rightarrow L_{eq} \left( \frac{V}{L_1} + \frac{V}{L_2} \right) = V \Rightarrow \frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} //$$




$\rightarrow$  R-L circuit

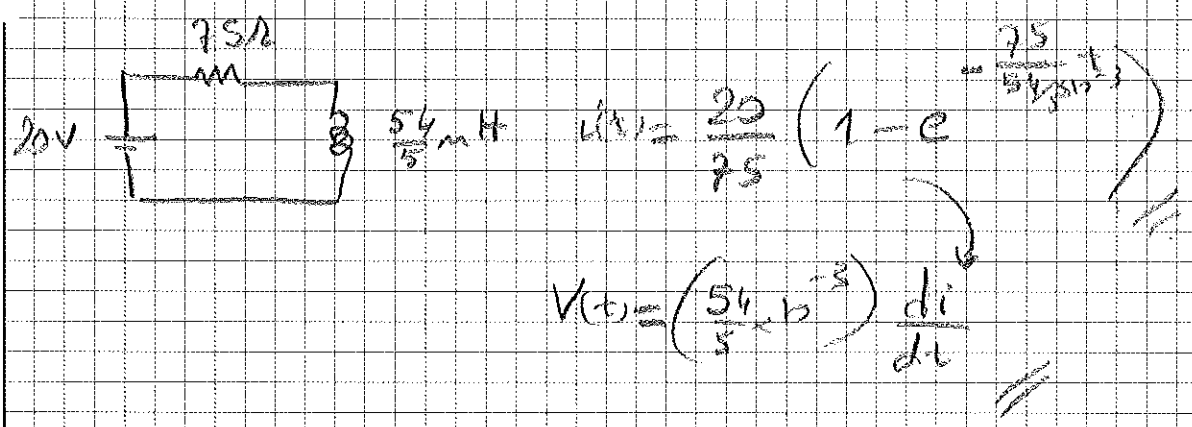

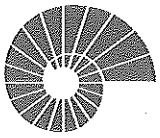

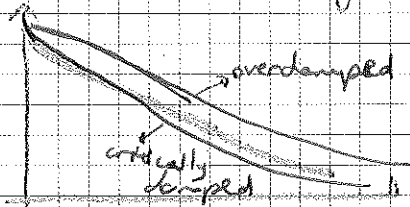When  $R^2 = \frac{4L}{C}$ , the system no longer oscillates.  
↳ critically damped case.



When  $R^2 > \frac{4L}{C}$ , overdamped. Capacitor charge approaches zero even more slowly.

Ex: What resistance R is required to give an L-R-C circuit an oscillation frequency that is 1/2 the undamped frequency.

undamped frequency:  $\sqrt{\frac{1}{LC}}$

$$\frac{1}{2} \sqrt{\frac{1}{LC}} = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} \Rightarrow R = \frac{3L}{C}$$

### Chap 31: Alternating Current


Circuits in which voltages and currents vary sinusoidally are called alternating current circuits.

#### Phasors and Alternating Currents


A sinusoidal voltage is described as:  
 $v = V \cos \omega t$

"Most present day household and industrial power-distribution systems operate with alt. current."  
"in Turkey 1.500V"

A sinusoidal current is described as:

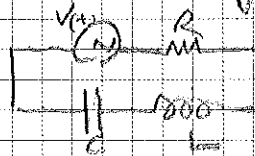

i = I cos ωt

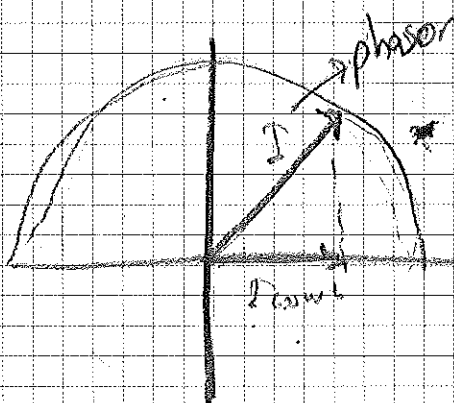

We use phasor diagrams to represent sinusoidally varying voltages and currents.

The instantaneous value of a quantity that varies sinusoidally with time is represented by the projection onto a horizontal axis of a vector with length I.

"Phasor is the vector in 2D whose projection to the horizontal axis gives the instantaneous value of the variable."