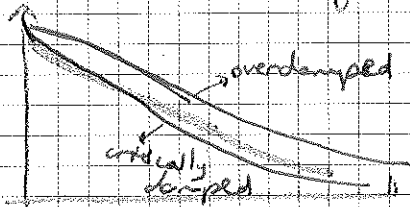


When $R^2 = \frac{4L}{C}$, the system no longer oscillates.
↳ critically damped case.



When $R^2 > \frac{4L}{C}$, overdamped. Capacitor charge approaches zero even more slowly.

Ex: What resistance R is required to give an L-R-C circuit an oscillation frequency that is $\frac{3}{2}$ the undamped frequency.

undamped frequency: $\sqrt{\frac{1}{LC}}$

$$\frac{1}{2} \sqrt{\frac{1}{LC}} = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} \rightarrow R = \frac{3L}{C}$$

Chap 31: Alternating Current


Circuits in which voltages and currents vary sinusoidally are called as alternating current circuits.

Phasors and Alternating Currents


A sinusoidal voltage is described as $v = V \cos \omega t$

"Most present day household and industrial power-distribution systems operate with alt. current."
↳ Turkey f. 50Hz

A sinusoidal current is described as

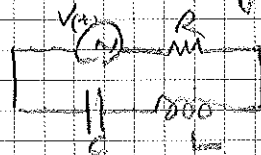


$i = I \cos \omega t$

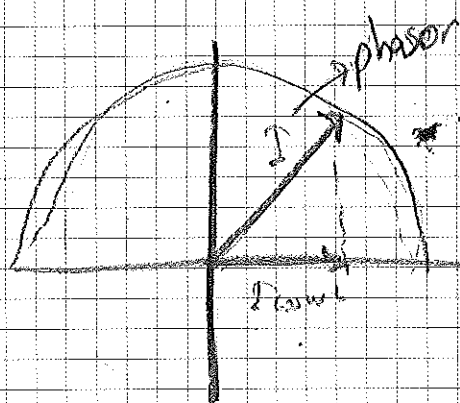


We use phasor diagrams to represent sinusoidally varying voltages and currents. The instantaneous value of a quantity that varies sinusoidally with time is represented by the projection onto a horizontal axis of a vector with a length I .

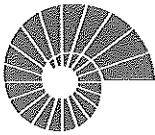
"Phasor is the vector in 2D whose projection to the horizontal axis gives the instantaneous value of the variable."



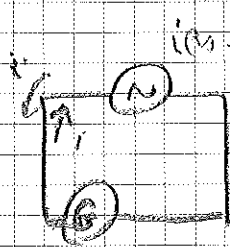"The vector which rotates ^{in the} counter clockwise direction with angular speed ω is called a phasor."





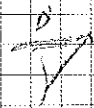AC can be both positive and negative.
 \Rightarrow If we place a galvanometer (for current measurement) into an AC circuit it will not show a value, unless the oscillations are really slow.



\Rightarrow So, we have to find other ways to describe and measure AC.

Full-wave rectifier circuit.

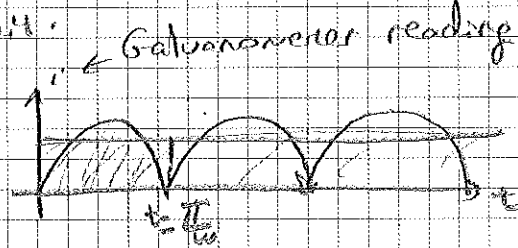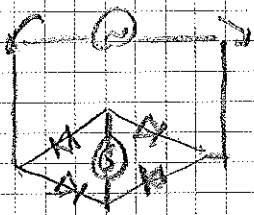


It is consisted of 4 diodes \Rightarrow these are elements which have 0 resistance in the forward and infinite resistance in the backward direction.

Galvanometer will display an average value:

$$\int_0^{T/\omega} I_m \sin \omega t \, dt = I_m \left[-\frac{\cos \omega t}{\omega} \right]_0^{T/\omega} = -\frac{I_m}{\omega} (-1 - 1) = \frac{2I_m}{\omega}$$

$$\frac{2I_m}{\omega} = I_{rav} \cdot \frac{\pi}{\omega} \Rightarrow \left[I_{rav} = \frac{2}{\pi} I_m \right]$$

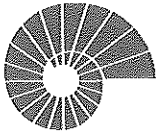rectified average value of a sinusoidal current.



AC is also described by the root mean square value:

$I_{rms} = \sqrt{\overline{i^2}}$, square-root of the time average of current squared.

$$i(t) = I \cos \omega t$$

$$\Rightarrow i^2(t) = I^2 \cos^2 \omega t = I^2 \left(\frac{1 + \cos 2\omega t}{2} \right) = \frac{I^2}{2} + \frac{I^2}{2} \cos 2\omega t$$

$$\overline{i^2(t)} = \overline{\left(\frac{I^2}{2} \right)} + \underbrace{\overline{\frac{I^2}{2} \cos 2\omega t}}_{=0} = \frac{I^2}{2} \quad \Rightarrow \quad \overline{i^2(t)} = \frac{I^2}{2}$$

$\Rightarrow \boxed{I_{rms} = \frac{I}{\sqrt{2}}}$ root-mean-square value of a sinusoidal current


similarly $\boxed{V_{rms} = \frac{V}{\sqrt{2}}}$

31.2 Resistance and Reactance

We will determine how to represent resistors, inductors and capacitors in ac circuits.

⇒ Find the relationships between phasors!


Resistor in an AC circuit

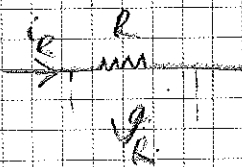


$$i_R = I \cos \omega t$$


$$\Rightarrow v_R = I R \cos \omega t = V_R \cos \omega t$$

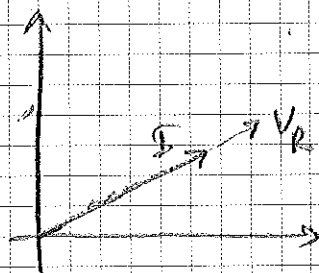$\Rightarrow \boxed{V_R = I R}$ phasor relationship



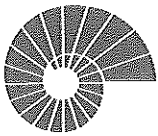

Inductor in an AC circuit

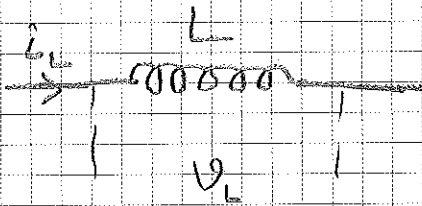


$i_L = I \cos \omega t$

$E = -V_L = L \frac{di_L}{dt} = -L I \omega \sin \omega t$

$V_L = -I \omega L \sin \omega t$

$V_L = \underbrace{I \omega L}_{V_L} \cos(\omega t + 90^\circ)$

$\rightarrow V_L = I X_L \Rightarrow \boxed{X_L = \omega L}$ inductive reactance
 ↑
 amplitude of voltage across an inductor

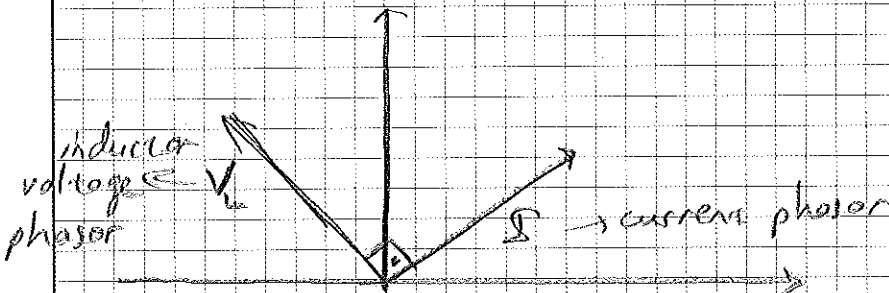

Ex 31.2: You want the current amplitude in a pure inductor to be $250 \mu A$, when voltage amplitude is $3.6 V$ at $f = 1679 Hz$


a) $X_L = ? \quad X_L = \omega L = \frac{V_L}{I} = \frac{3.6 V}{250 \times 10^{-6} A} = 14.4 k\Omega$

$L = ?$


$L = \frac{14.4 \times 10^3 \Omega}{2\pi \times 1679 Hz} = 1.43 mH //$

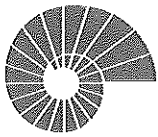b) at $f = 1679 Hz \quad I = ?$ if V_L is the same

$X_L = 2\pi f L = \frac{V_L}{I} \Rightarrow I = \frac{V_L}{2\pi f L} \Rightarrow \boxed{I = 25 \mu A}$



Capacitor in an AC circuit

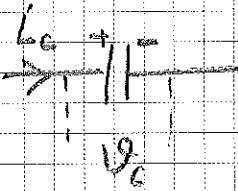

Choose the positive direction of current to be towards the + plate of the capacitor.
 \Rightarrow Capacitor is charging.

$$i_c = \frac{dq}{dt} > 0$$

$$i_c = I \cos \omega t = \frac{dq}{dt}$$

for,


$$q(t) = \frac{I}{\omega} \sin \omega t, \quad q_0 = 0$$

$$q(t) = \frac{I}{\omega} \cos(\omega t - 90^\circ)$$


$$\Rightarrow v_c = \frac{q}{C} = \left(\frac{I}{\omega C}\right) \cos(\omega t - 90^\circ)$$

$$V_c = \frac{I}{\omega C} = I X_C \Rightarrow \boxed{X_C = \frac{1}{\omega C}}$$

capacitive reactance

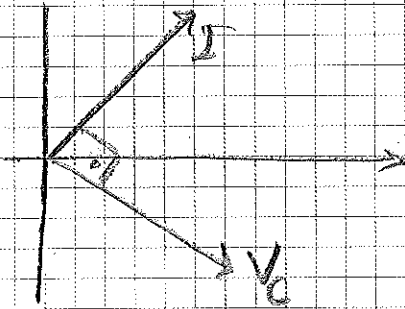

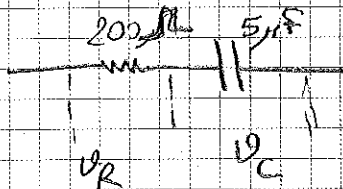Ex 31.3: Resistor and capacitor in an AC circuit.




$$v_R = 1.2 \text{ V} \cos(2500 \text{ rad/s } t)$$


a) $i = ?$ $i = \frac{v_R}{R} = \frac{1.2 \text{ V} \cos(2500 \text{ rad/s } t)}{200 \Omega} = 6 \text{ mA} \cos(2500 \text{ rad/s } t)$

b) $X_C = ?$ $X_C = \frac{1}{\omega C} = \frac{1}{2500 \text{ rad/s} \cdot 5 \times 10^{-6} \text{ F}} = 80 \Omega$

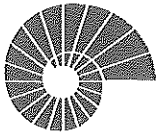c) $v_c = ?$ $v_c = X_C I \sin \omega t = 80 \Omega \cdot 6 \times 10^{-3} \text{ A} \sin(2500 \text{ rad/s } t) = 0.48 \text{ V} \sin(2500 \text{ rad/s } t)$



Phasor Analysis:

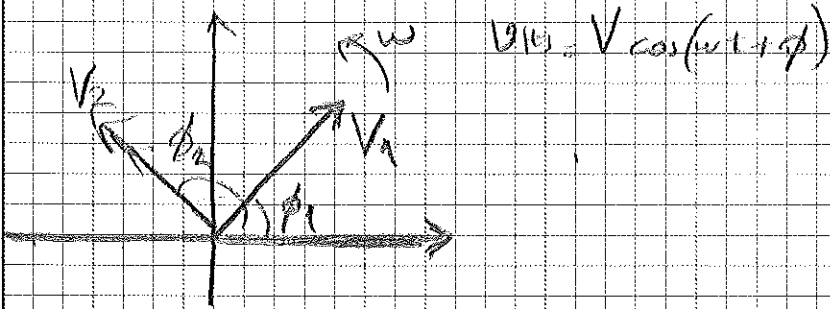

$$v_1(t) = V_1 \cos(\omega t + \phi_1) \quad , \quad v_2(t) = V_2 \cos(\omega t + \phi_2)$$

Projection of \vec{V}_1 to the horizontal axis

$$\vec{V}_1 = V_{1x} \hat{i} + V_{1y} \hat{j}$$

$$\vec{V}_2 = V_{2x} \hat{i} + V_{2y} \hat{j}$$


$$\rightarrow v(t) = v_1(t) + v_2(t)$$

$$\vec{V}_1 + \vec{V}_2 = \underbrace{(V_{1x} + V_{2x})}_{V_{x(t)} = v_x(t)} \hat{i} + \underbrace{(V_{1y} + V_{2y})}_{V_{y(t)} = v_y(t)} \hat{j}$$

Summation of the projections of V_1 and V_2 to the horizontal axis is the projection of the vectorial sum of V_1 and V_2 to the horizontal axis.


\Rightarrow The phasor of $v_1(t) + v_2(t)$

is $\vec{V}_1 + \vec{V}_2$

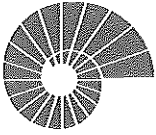


31.3 L-R-C Series Circuit

Consider the circuit:

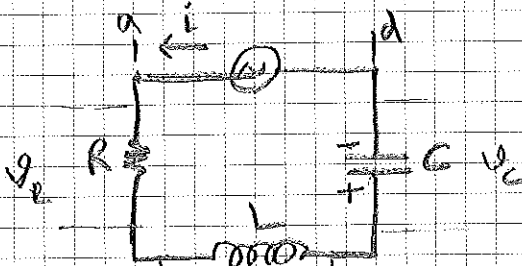

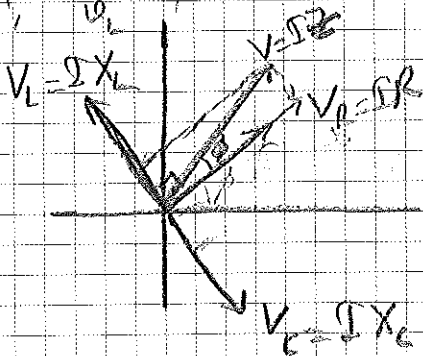We will use a phasor diagram in order to solve for the circuit.



$$v_{ad} = V \cos(\omega t + \phi)$$

$$\vec{V} = \vec{V}_R + \vec{V}_L + \vec{V}_C$$

$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$V = \sqrt{I^2 R^2 + I^2 (X_L - X_C)^2}$$


$$V = I \sqrt{R^2 + (X_L - X_C)^2}$$

We define the impedance Z of an AC circuit as:

$$V = I Z \Rightarrow Z = \sqrt{R^2 + (X_L - X_C)^2}$$

impedance of an L-R-C series circuit

Band pass filter

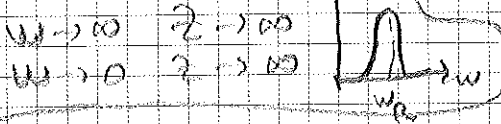

$$Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$\omega_r = \frac{1}{\sqrt{LC}}$$


\therefore For a given amplitude V of the source voltage, the amplitude

$I = \frac{V}{Z}$ will be different at different frequencies.

The angle ϕ between the voltage and current phasors is given by:


$$\tan \phi = \frac{V_L - V_C}{V_R} = \frac{I(X_L - X_C)}{I R} = \frac{\omega L - \frac{1}{\omega C}}{R}$$
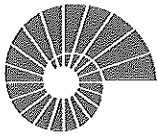
$$\therefore \text{If the current is } i = I \cos \omega t, \quad v = V \cos(\omega t + \phi) = I Z \cos(\omega t + \phi)$$



rms values are related as; $V_{rms} = \frac{V}{\sqrt{2}}$, $I_{rms} = \frac{I}{\sqrt{2}}$

$$V_{rms} = I_{rms} Z$$

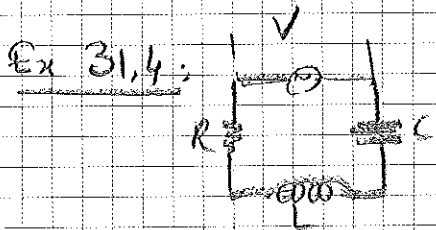

$R = 300\Omega$, $L = 60\text{mH}$, $C = 0.5\mu\text{F}$, $V = 50\text{V}$, $\omega = 1000\text{rad/s}$
 $\rightarrow X_L, X_C, Z, I, \phi, V_R, V_L, V_C = ?$

$$X_L = \omega L = 1000\text{rad/s} \cdot 60 \cdot 10^{-3}\text{H} = 600\Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{1000\text{rad/s} \cdot 0.5 \cdot 10^{-6}\text{F}} = 200\Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(300\Omega)^2 + (400\Omega)^2} = 500\Omega$$

$$I = \frac{V}{Z} = \frac{50\text{V}}{500\Omega} = 0.1\text{A}$$

$$\phi = \arctan\left(\frac{X_L - X_C}{R}\right) = \arctan\left(\frac{400}{300}\right) = 53^\circ$$


$$V_R = IR = 0.1\text{A} \cdot 300\Omega = 30\text{V}$$

$$V_L = IX_L = 0.1\text{A} \cdot 600\Omega = 60\text{V}$$

$$V_C = IX_C = 0.1\text{A} \cdot 200\Omega = 20\text{V}$$

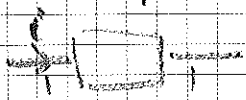31.4 Power in Alternating-Current Circuits


Instantaneous power delivered to a circuit element:




$$p = v i$$



For a pure resistor

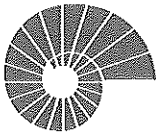

Pure inductor

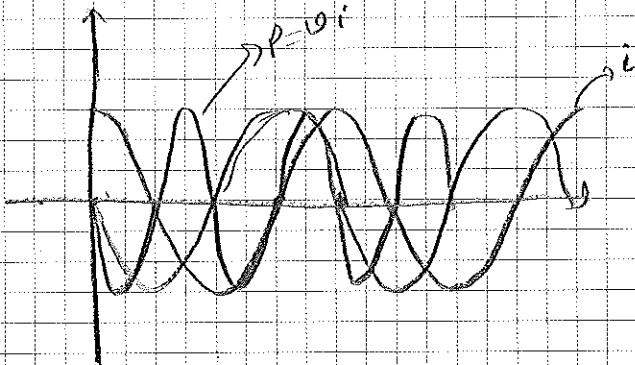

For a pure resistor; $p = vi = VI \cos^2 \omega t$

$$\begin{aligned} \Rightarrow P_{av} &= VI \overline{\cos^2 \omega t} = VI \left(\frac{1}{2} + \frac{\cos 2\omega t}{2} \right) \\ &= \frac{VI}{2} \end{aligned}$$

$$\Rightarrow \boxed{P_{av} = V_{rms} I_{rms}}$$

For an arbitrary circuit element;

$$\begin{aligned} p = vi &= V \cos(\omega t + \phi) I \cos \omega t = VI \cos(\omega t + \phi) \cos \omega t \\ &= VI \left\{ \frac{1}{2} \left[\cos(2\omega t + \phi) + \cos(\phi) \right] \right\} \end{aligned}$$

$$\Rightarrow P_{av} = \frac{VI}{2} \left\{ \underbrace{\cos(2\omega t + \phi)}_0 + \cos(\phi) \right\} = \frac{VI}{2} \cos \phi = \boxed{V_{rms} I_{rms} \cos \phi}$$


The factor $\cos \phi$ is called the power factor.

For a pure resistance $\phi = 0 \Rightarrow P_{av} = V_{rms} I_{rms}$

" " inductor $\phi = 90^\circ \Rightarrow P_{av} = 0$

capacitor $\phi = -90^\circ \Rightarrow P_{av} = 0$

} no average
power delivered
to an inductor
or a capacitor

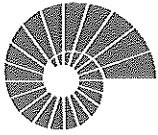

Ex 31.6: Power in a hair dryer

average power

rms voltage


An electric hair dryer is rated 1500 W at 120 V

a) $R = ?$ $P_{av} = V_{rms} I_{rms} = \frac{V_{rms}^2}{R} \Rightarrow R = \frac{(120V)^2}{1500W} = 9.6 \Omega$


b) rms current $I_{rms} = \frac{V_{rms}}{R} = \frac{120V}{9.6 \Omega} = 12.5A$

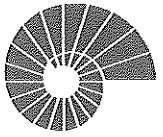c) Maximum instant power

$P_{max} = V I = 2 V_{rms} I_{rms} = 3000W //$




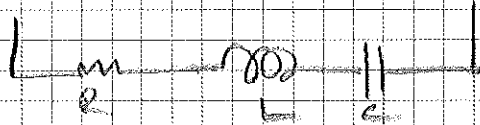
31.5 Resonance in Alternating Current Circuits



$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$


tan $\phi = \frac{X_L - X_C}{R} = \frac{\omega L - \frac{1}{\omega C}}{R}$, angle ϕ between V and I .

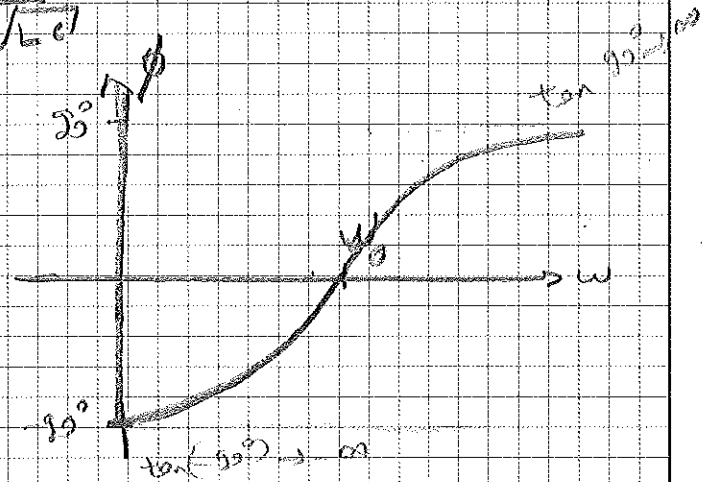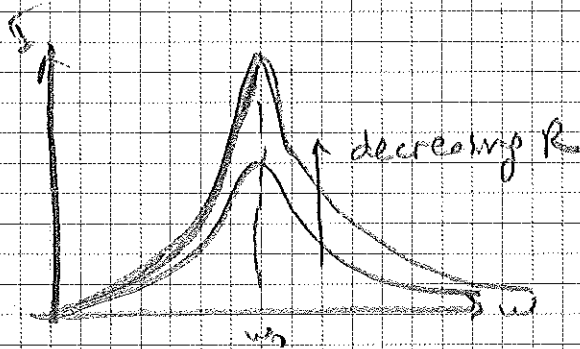Z reaches its minimum at $\omega_0 = \frac{1}{\sqrt{LC}}$




"Resonance"
Tuning is possible
by changing L or C.

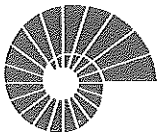"Anteny Radio and Television receiving circuits"



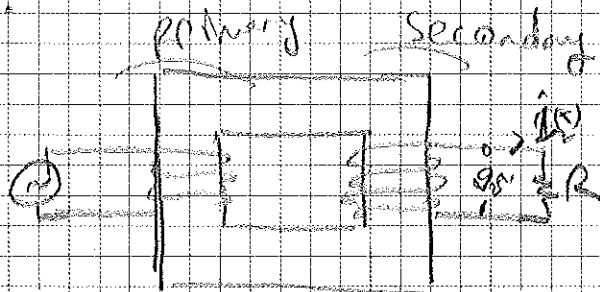31.6 Transformers

It is much easier to change voltage levels in AC as compared to DC.



Two coils of different windings.

Core made of a magnetic material so that the magnetic field lines remain in the core.

When we assume that all the magnetic field lines are confined to the iron core, Φ is the same in both coils,

$$E_1 = -N_1 \frac{d\Phi}{dt}, \quad E_2 = -N_2 \frac{d\Phi}{dt}$$

$$\Rightarrow \frac{E_1}{N_1} = \frac{E_2}{N_2} \Rightarrow \boxed{\frac{E_2}{E_1} = \frac{N_2}{N_1}}$$

Exercise: Power delivered from the primary

$$P_1 = \cancel{V_1 I_1} = (V_2 I_2), \text{ there is no resistance in windings.}$$

$$V_2 = V_1 \frac{N_2}{N_1} = I_2 R$$

$$\cancel{\frac{V_1^2}{R}} = \cancel{\frac{V_1^2}{R}} \frac{N_2}{N_1} \frac{V_1}{N_1} \frac{N_2}{N_1} \frac{V_1}{R} \Rightarrow \boxed{\frac{V_1^2}{R} \left(\frac{N_2}{N_1}\right)^2}$$

Transformer transforms the resistance

$$\frac{V_1^2}{R} \left(\frac{N_2}{N_1}\right)^2 \Rightarrow P = V_1 \frac{V_1}{R} = \frac{V_1^2}{R} \Rightarrow \boxed{R_{eq} = \frac{R}{(N_2/N_1)^2}}$$