

Soln


Closed book. No calculators are to be used for this quiz.  
Quiz duration: 10 minutes

Name:

Student ID:

Signature:

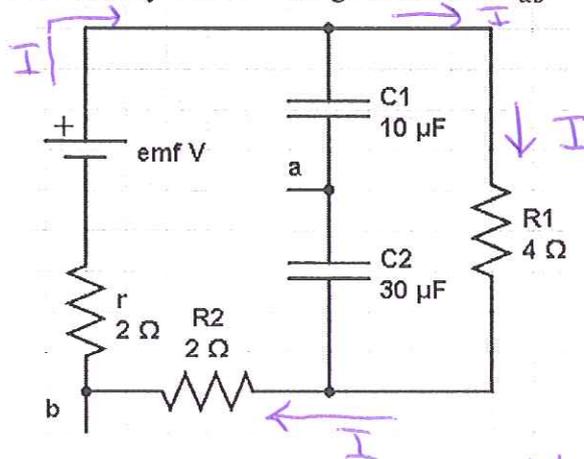In the following circuit the capacitors are fully charged and the charge of the C1 is  $30\mu\text{C}$ . Determine the e.m.f of the battery and the voltage difference  $V_{ab}$ .



connected in series

$$\left. \begin{array}{l} C_1 = 10 \mu\text{F} \\ C_2 = 30 \mu\text{F} \end{array} \right\} \begin{array}{l} Q_1 = 30 \mu\text{C} \Rightarrow V_{C1} = \frac{Q_1}{C_1} = 3\text{V} \\ Q_2 = 30 \mu\text{C} \Rightarrow V_{C2} = \frac{Q_2}{C_2} = 1\text{V} \end{array}$$

Since capacitors are fully charged we assume that there is no current flows through the capacitors. So,

$$V_{\text{emf}} = I(r + R_1 + R_2)$$

Also we know,  $V_{C1} + V_{C2} = V_{R1} = IR_1$

$$\Rightarrow 4\text{V} = I(4\Omega) \Rightarrow I = 1\text{A}$$

$$\rightarrow V_{\text{emf}} = (1\text{A})(2\Omega + 2\Omega + 4\Omega) = 8\text{V}$$

$$V_{ab} = V_{C2} + V_{R2} = 1\text{V} + (1\text{A})(2\Omega) = 3\text{V}$$

$\parallel$   
 $I R_2$


Closed book. No calculators are to be used for this quiz.  
Quiz duration: 10 minutes

Name:

Student ID:

Signature:

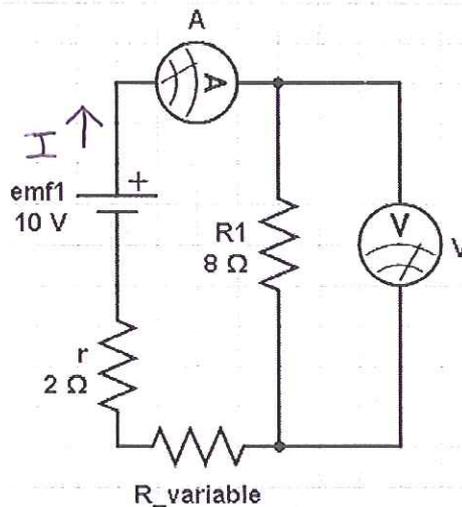In the following circuit, the battery has an internal resistance  $2\Omega$ . The resistor  $R$  is variable such that its resistance can range from  $0$  to  $\infty$ . Determine the maximum and minimum readings that the amperemeter and the voltmeter show as  $R$  changes in the full range. Plot the reading of the voltmeter as a function of  $R$  values qualitatively.



$$10V - I(r + R_1 + R) = 0$$

$$10V = I(10\Omega + R)$$

(A) reads  $\Rightarrow I(R) = \frac{10V}{(10\Omega + R)}$   
function of  $R$


$$I_{\text{max}} = 1A$$

$$I_{\text{min}} = 0A$$

(V) reads  $\Rightarrow V_{R_1} = I(R) R_1$   
 $= \frac{80V\Omega}{(10\Omega + R)}$

$$V_{\text{max}} = 8V$$

$$V_{\text{min}} = 0V$$

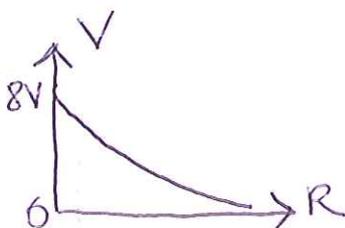

Soln -

PHYS 102: General Physics 2 KOÇ UNIVERSITY  
College of Arts and Sciences

Spring Semester 2013

Section 3

Quiz 5

14 March 2013


Closed book. No calculators are to be used for this quiz.  
Quiz duration: 10 minutes

Name:

Student ID:

Signature:

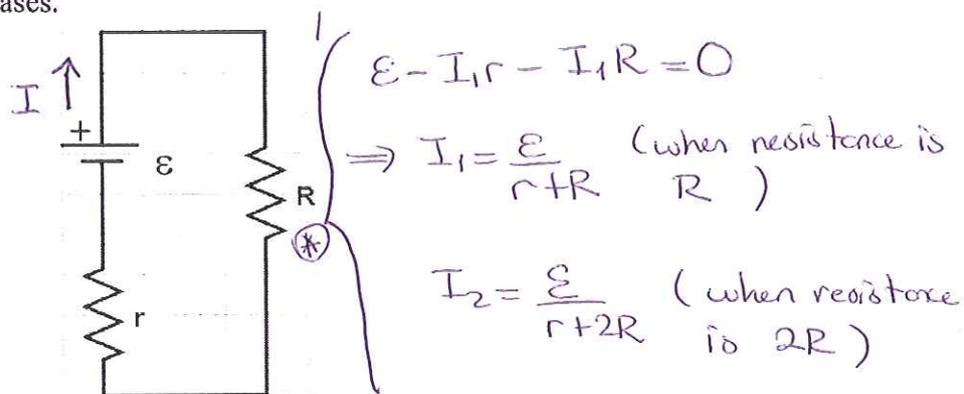Given the following circuit where the internal resistance of the battery is smaller than the resistor in the circuit ( $r < R$ ). Show that when the value of  $R$  is doubled, the power dissipated in the battery decreases.



When resistance =  $R$ , power dissipated by battery:

$$P_1 = I_1^2 r$$

When resistance =  $2R$ , power " " " "

$$P_2 = I_2^2 r$$

Since  $I_2 < I_1$  by \*

$$P_2 < P_1$$



Closed book. No calculators are to be used for this quiz.  
Quiz duration: 10 minutes

Name:

Student ID:

Signature:

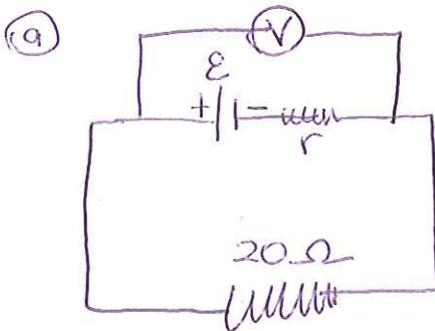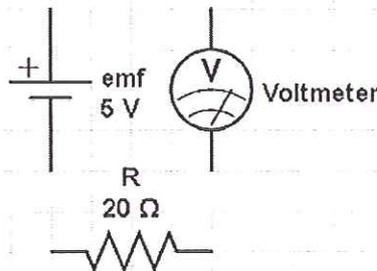You are given the following circuit elements and instruments. The battery has an unknown internal resistance. The voltmeter is ideal. (a) Design a circuit to determine the internal resistance of the battery. (b) Calculate the power output of the battery if the voltmeter in your circuit measures 4 V potential difference.



(b)

$$4V = \epsilon - Ir$$

$$= (20\Omega)(I)$$

$$\Rightarrow I = \frac{4}{20} = 0.2A$$

$$4V = 5V - (0.2)r$$

$$r = 5\Omega$$

$$P_{\epsilon} = \epsilon I = (5V)(0.2A) = 1W$$

$$P_r = I^2 r = 0.2 \cdot 5$$

$$= (0.2A)^2 \cdot 5\Omega$$

$$P_{out} = P_{\epsilon} - P_r = 0.8W$$



Closed book. No calculators are to be used for this quiz.  
Quiz duration: 10 minutes

Name:

Student ID:

Signature:

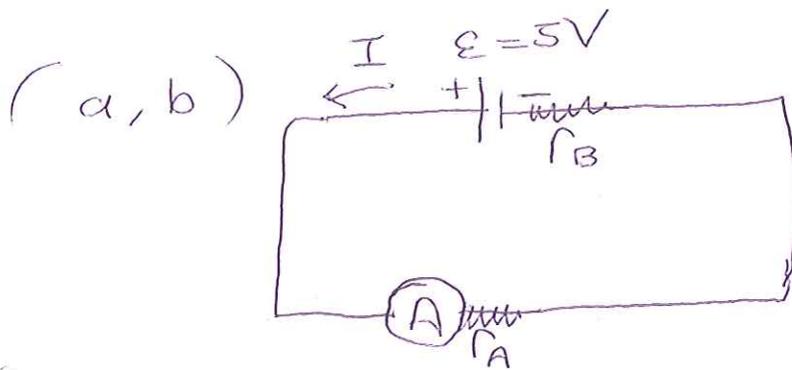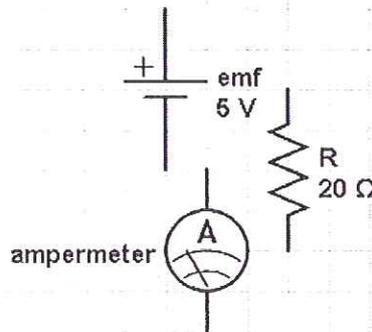You are given the following circuit elements and instruments. The battery has an unknown internal resistance. The internal resistance of the amperemeter is  $0.1\Omega$ . (a) Design a circuit to determine the internal resistance of the battery. (b) Calculate the power output of the battery if the amperemeter indicates a current of  $0.2A$  in your circuit.



$r_A = 0.1\Omega$  (internal resistance of (A))  
 $r_B = \text{unknown}$  (internal resistance of battery)

$$R = 20\Omega$$

$$E = 5V$$

Note that  $P_E - P_{r_B} = P_R + P_{r_A}$  also!

$$(b) \quad I = 0.2 A$$

$$P_E = (5V)(0.2A) = 1W$$

$$P_{r_B} = I^2 r_B = (0.2A)^2 (4.8\Omega) \approx 0.196 W$$

$$P_{\text{output}} = P_E - P_{r_B} \approx 0.8W$$


Closed book. No calculators are to be used for this quiz.  
Quiz duration: 10 minutes

Name:

Student ID:

Signature:

In the circuit shown in the figure,  $r_1$  and  $r_2$  are the internal resistance of the batteries with  $\text{emf}_1$  and  $\text{emf}_2$ , respectively.  $R$  is a resistor connected to the circuit. (a) calculate the power input to the battery being charged, (b) plot the change of electric potential in a loop starting from point P as the zero level of potential and moving clockwise in the circuit.

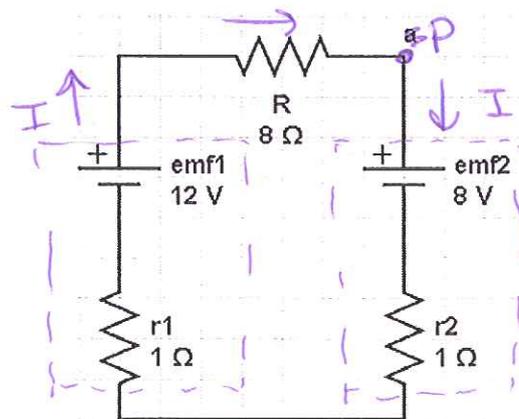

(a) First, we find  $I$

$$-8V - I r_2 - I r_1 + 12V - I R = 0$$

$$4V = (10\Omega) I \Rightarrow I = 0.4A$$

$$P_{\text{input}} = P_{\mathcal{E}_2} + P_{r_2} = \mathcal{E}_2 I + I^2 r_2$$

$$= (8V)(0.4A) + (0.4A)^2 \cdot 1\Omega$$

$$= 3.2W + 0.16W$$

$$= 3.36W$$

