

Section 1

Quiz 6

21 March 2013


Closed book. No calculators are to be used for this quiz.**Quiz duration: 10 minutes**

Name:

Student ID:

Signature:

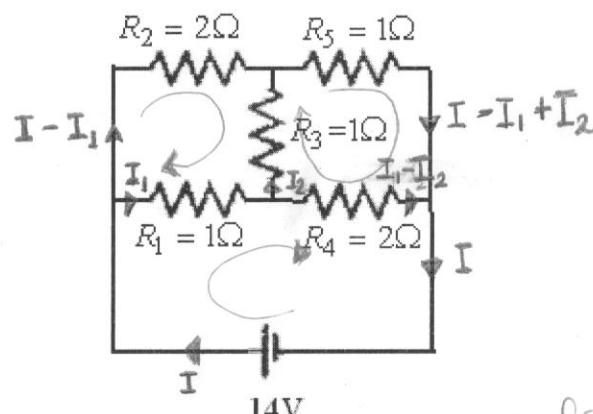Find the current through each resistor in the circuit.



bottom loop:

$$14V - I_1 \cdot 1\Omega - (I_1 - I_2) \cdot 2\Omega = 0$$

$$3I_1 + 2I_2 = 14 \quad (1)$$

top left loop:

$$-(I - I_1) \cdot 2\Omega + I_2 \cdot 1\Omega + I_1 \cdot 1\Omega = 0$$

$$-2I + 3I_1 + I_2 = 0 \quad (2)$$

top right loop:

$$-(I - I_1 + I_2) \cdot 1\Omega + (I_1 - I_2) \cdot 2\Omega + I_2 \cdot 1\Omega = 0$$

$$-I_1 + 3I_1 - 4I_2 = 0 \quad (3)$$

Thus,

$$I_{R_1} = I_1 = 6A$$

$$I_{R_2} = I - I_1 = 10A - 6A = 4A$$

$$I_{R_3} = I_2 = 2A$$

$$I_6 = I_1 - I_2 = 2A$$

★ Current in
the loops are
determined via
junction rule

from (1) - (2) we get:

$$2I - 3I_2 = 14 \quad (4)$$

from (3) - (2) we get

$$I - 5I_2 = 0$$

$$\Rightarrow I = 5I_2 \quad (5)$$

Substitute (5) into (4):

$$7I_2 = 14A \Rightarrow I_2 = 2A$$

$$\Rightarrow I = 5I_2 = 10A$$

Solving (1) for I_1 , we find:

$$I_1 = \frac{14A + 2I_2}{3} = 6A$$

Closed book. No calculators are to be used for this quiz.


Quiz duration: 10 minutes

Name:

Student ID:

Signature:

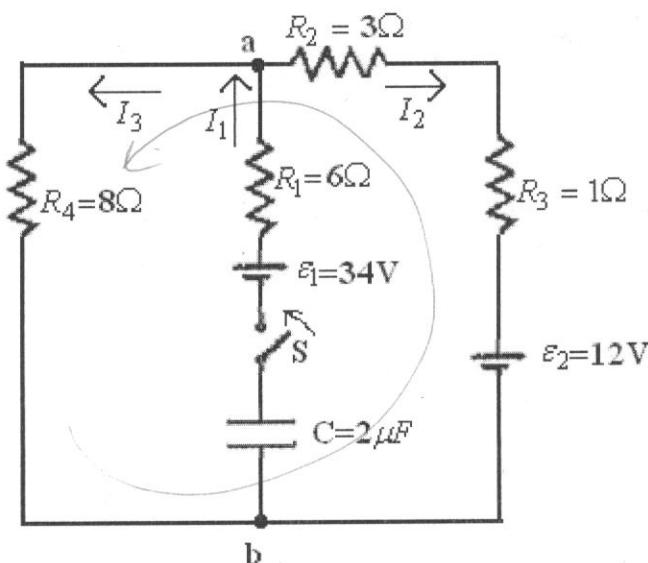Consider the circuit given in the figure. The capacitor is initially uncharged and the switch S is closed at $t=0$. Long time after (t goes to infinity) the switch S is closed, find the potential difference $V_a - V_b$. What is the maximum charge on the $2 \mu F$ capacitor?



If we wait enough, the capacitor is fully charged. Then, the capacitor behaves as open circuit. ($I_1 = 0$)

The current flows from the outer loop only.

$$12V + I_2 \cdot 1\Omega + I_2 \cdot 3\Omega - I_3 \cdot 8\Omega = 0$$

$$2I_3 - I_2 = 3A$$

Due to junction rule: $I_1 = I_2 + I_3$ & $I_1 = 0$


$$I_2 = -I_3$$

$$2I_3 - (-I_3) = 3A \Rightarrow \boxed{\begin{array}{l} I_3 = 1A \\ I_2 = -1A \\ I_1 = 0 \end{array}}$$

Potential across the capacitor

$$\text{is: } V_{ab} = I_3 \cdot R_4 = 1A \cdot 8\Omega = 8V$$

$$Q_{\max} = C \cdot V = 2\mu F \cdot 8V = 16\mu C$$

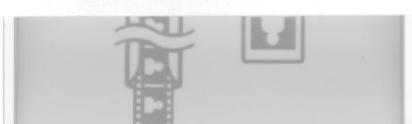

Section 2

Quiz 6

21 March 2013

Closed book. No calculators are to be used for this quiz.


Quiz duration: 10 minutes

Name:

Student ID:

Signature:

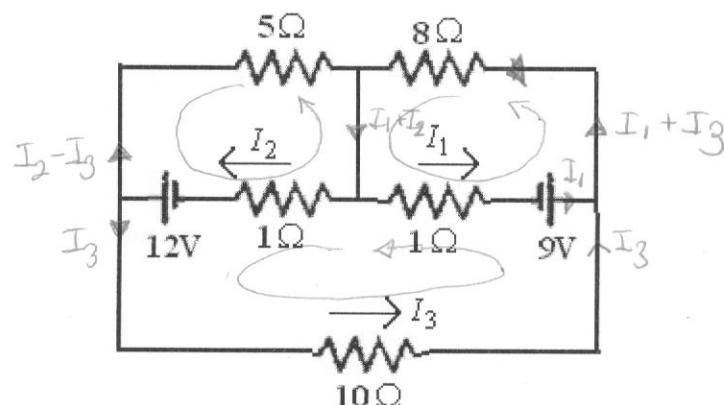Calculate the three currents I_1 , I_2 and I_3 indicated in the circuit diagram.



*The currents in the branches are written due to junction rule!

Top left loop:

$$-12V + I_2 \cdot 1\Omega + (I_2 - I_3) \cdot 5\Omega = 0 \\ 6I_2 - 5I_3 = 12A \quad (1)$$

Top right loop:

$$-I_1 \cdot 1\Omega + 9V - (I_1 + I_3) \cdot 8\Omega = 0 \\ 9I_1 + 8I_3 = 9A \quad (2)$$

Bottom loop:

$$-I_3 \cdot 10\Omega - 9V + I_1 \cdot 1\Omega - I_2 \cdot 5\Omega + 12V = 0 \\ -I_1 + I_2 + 10I_3 = 3A \quad (3)$$

(Solve (1) for I_2 : $I_2 = 2A + \frac{5}{6}I_3$)

(Solve (2) for I_1 : $I_1 = 1A - \frac{8}{9}I_3$)

Substitute into (3):

Then:
 $I_2 = 2A + \frac{5}{6}(0.171A) = 2.16A$

$I_1 = 1A - \frac{8}{9}(0.171A) = 0.188A$

$I_3 = 0.171A$

$\rightarrow -\left(1A - \frac{8}{9}I_3\right) + \left(2A + \frac{5}{6}I_3\right) + 10I_3 = 3A$

(2) (3) (1.8)

$\left(\frac{16+15+180}{18}\right)I_3 = 2A \Rightarrow I_3 = 0.171A$

$I_2 = 2.16A$

$I_3 = 0.171A$

Section 3

Quiz 6

21 March 2013


Closed book. No calculators are to be used for this quiz.
 Quiz duration: 10 minutes

Name:

Student ID:

Signature:

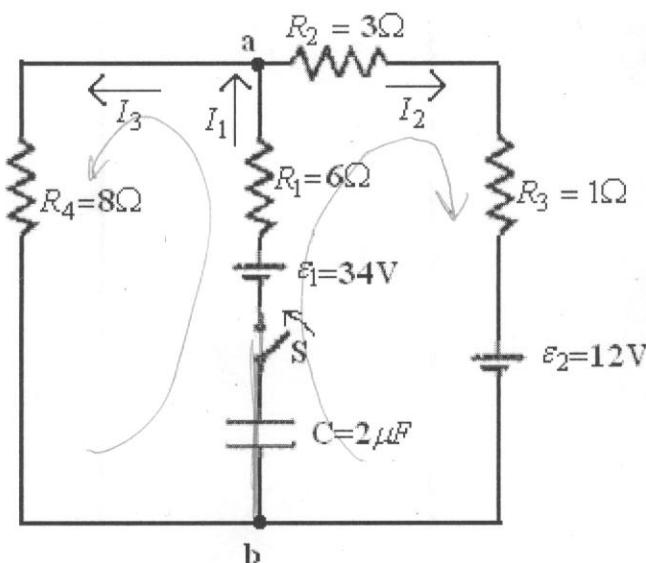Consider the circuit in given the figure. The capacitor is initially uncharged and the switch S is closed at $t=0$. Find the currents I_1 , I_2 and I_3 just after the switch S is closed.



Since the capacitors are initially uncharged, just after the switch is closed the potential across the capacitor is zero:

$$V_C = \frac{Q}{C} = 0 \quad (1)$$

The capacitor behave as on short circuit.

$$\text{Left loop: } 34 - 6I_1 - 8I_3 = 0 \rightarrow [3I_1 + 4I_3 = 17A] \quad (2)$$

$$\text{Right loop: } 34 - 6I_1 - 3I_2 - I_2 = 12 = 0 \rightarrow [3I_1 + 2I_2 = 12] \quad (4)$$

$$\text{Junction Rule: } [I_1 = I_2 + I_3] \quad (3)$$

Substitute (3) into (1) & (2)

$$3I_2 + 3I_3 + 4I_3 = 17A \rightarrow [3I_2 + 7I_3 = 17A]$$

$$3I_2 + 3I_3 + 2I_2 = 11A \rightarrow [5I_2 + 3I_3 = 11A]$$

$$26I_3 = 52A$$

$$\Rightarrow I_3 = 2A$$

$$3I_1$$

$$3I_1 + 4I_3 = 17A \Rightarrow [I_1 = 3A] \& [I_2 = I_1 - I_3 = 1A]$$

Section 4

Quiz 6

21 March 2013


Closed book. No calculators are to be used for this quiz.
 Quiz duration: 10 minutes

Name:

Student ID:

Signature:

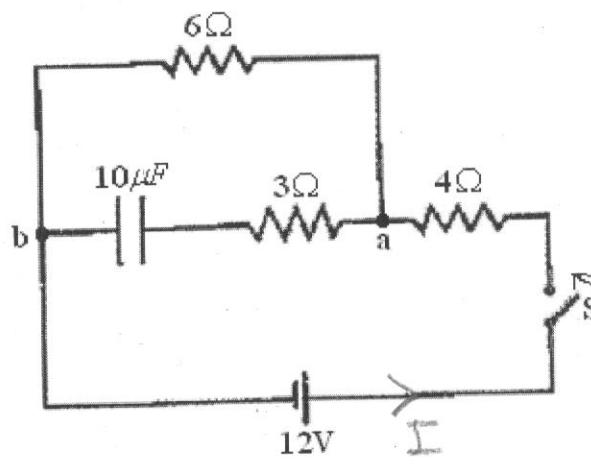Consider the circuit given in the figure. The capacitor is initially uncharged and the switch S is closed at $t=0$. Long time after (t goes to infinity) the switch S is closed, find the potential difference $V_a - V_b$. What is the maximum charge on the $10 \mu F$ capacitor?



* After we close switch the circuit, and wait enough, the capacitor gets fully charged.
 The capacitor behave as open circuit.

The current flows from the outer loop (as $t \rightarrow \infty$)

$$I = \frac{12V}{6\Omega + 4\Omega} = 1.2A$$

$$V_a - V_b = IR = 1.2A \times 6\Omega = 7.2V \quad (\text{point } a \text{ is @ higher potential})$$

The max. charg. on the capacitor is then,

$$Q_{\max} = CV = 10\mu F \times 7.2V = 72\mu C$$



Section 5

Quiz 6

21 March 2013


Closed book. No calculators are to be used for this quiz.**Quiz duration: 10 minutes**

Name:

Student ID:

Signature:

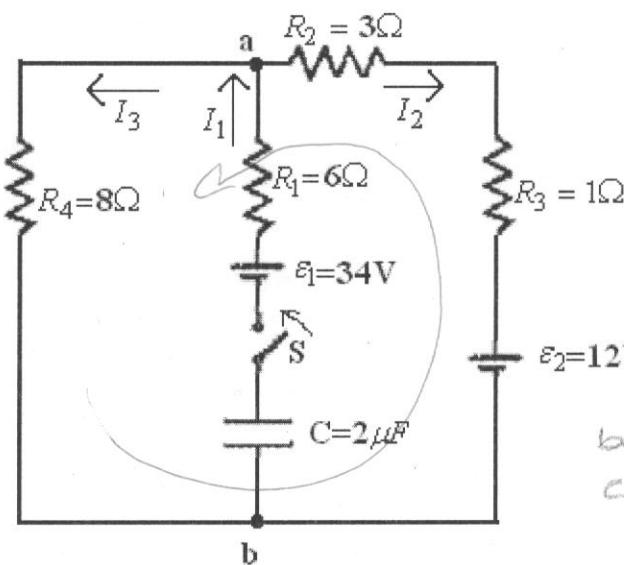Consider the circuit in the figure. The capacitor is initially uncharged and the switch S is closed at $t=0$. Find the currents I_1 , I_2 and I_3 long time after (t goes to infinity) the switch S is closed.



If we wait enough after the switch is closed, the capacitor gets fully charged.

The capacitor behaves as an open circuit then.

The current flows from the outer loop only;

$$12V + I_2 \cdot 1\Omega + I_2 \cdot 3\Omega - I_3 \cdot 8\Omega = 0$$

$$4I_2 - 8I_3 = -12V$$

$$2I_3 - I_2 = 3V$$

On the other hand, $I_1 = I_2 + I_3$ due to junction rule.

But $I_1 = 0$, since Capacitor behaves as an open circuit. Thus $I_2 = -I_3$

$$2I_3 - (-I_3) = 3A \Rightarrow 3I_3 = 3A \Rightarrow \boxed{\begin{array}{l} I_3 = 1A \\ I_2 = -1A \\ I_1 = 0A \end{array}}$$

