

Closed book. No calculators are to be used for this quiz.


Quiz duration: 10 minutes

Name:

Student ID:


Signature:

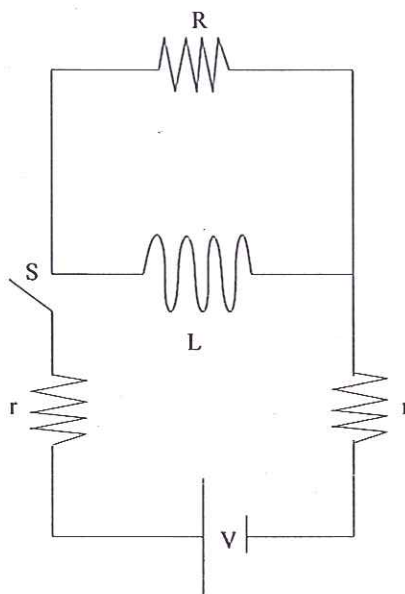The switch S is closed at time $t = 0$. What is the power dissipated through the resistor R just after $t = 0$? What is the maximum energy that can be stored in such a circuit?



(Corrected)

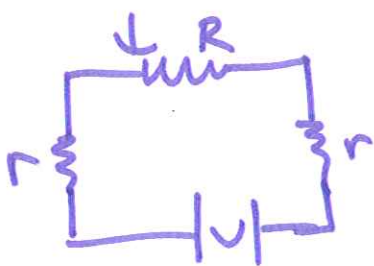
Just after $t=0$, $i_L(0) = 0$. So $i_R = \frac{V}{R_{eq}} = \frac{V}{2r+R}$



$$\rightarrow P_R = i^2 R = \left(\frac{V}{2r+R}\right)^2 \cdot R$$

$i_{(max)L} \Rightarrow$ when R has no current through it. \leftarrow (as $t \rightarrow \infty$)

$$i_{(max)L} = \frac{V}{2r}$$

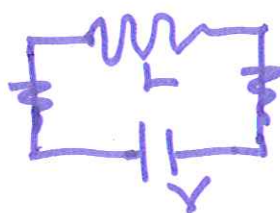

$$U_{max} = \frac{1}{2} L i_{(max)}^2 = \left(\frac{V}{2r}\right)^2 L \cdot \frac{1}{2} = \frac{V^2 L}{8r}$$

Closed book. No calculators are to be used for this quiz.


Quiz duration: 10 minutes

Name:

Student ID:



Signature:

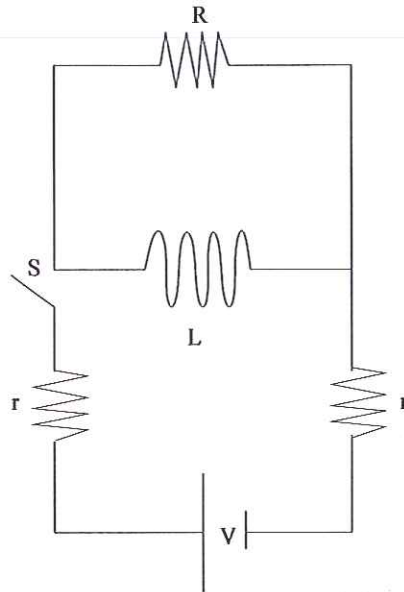The switch S is closed at time $t = 0$. Find the time constant of this circuit. Explain your reasoning.



The switch S is closed at $t = 0$.

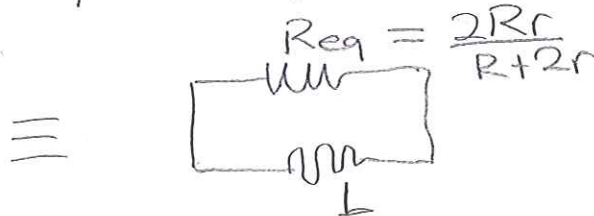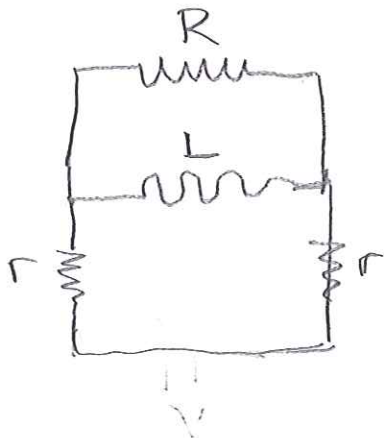The discharging and charging LC circuit should have the same time constant. Since it is easier to see the time constant from a discharging LC circuit we'll work on equivalently work on:



$$\Rightarrow \tau = \frac{L}{R_{eq}} = \frac{L(R+2r)}{2Rr}$$

Closed book. No calculators are to be used for this quiz.


Quiz duration: 10 minutes

Name:


Student ID:

Signature:

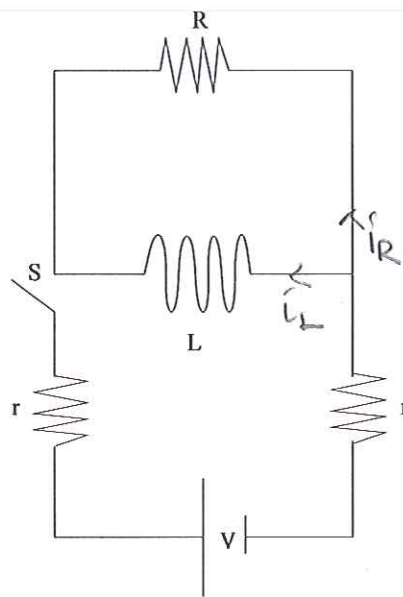Suppose the switch S is closed for a long time and the equilibrium is reached. Then, all of a sudden, if the switch S is reopened at time $t = 0$, find the power dissipated through the resistor R as a function of time.



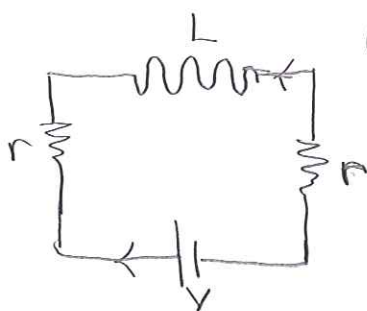
When switch S is closed for a long time $i_R \rightarrow 0$.



(L is short circuit)

$$i = \frac{V}{2r}$$

After S is opened at time $t = 0$

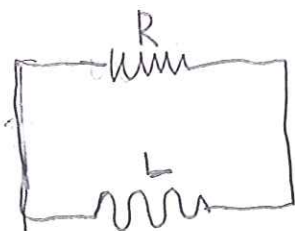

$$i(t) = i_0 e^{-t/\tau} \quad \tau = \frac{L}{R}$$

$$i_0 = \frac{V}{2r} = i$$

$$\Rightarrow P_R = i^2(t)R = \left(\frac{V}{2r}\right)^2 R e^{-2t/\tau}$$

Closed book. No calculators are to be used for this quiz.


Quiz duration: 10 minutes

Name:

Student ID:

Signature:

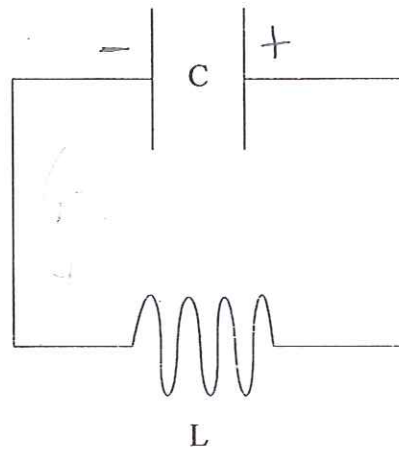Consider the LC circuit shown in the figure. If the charge on the left plate of the capacitor is known to be $q = -Q_{\max}/2$ and decreasing at time $t = 0$, find expressions for the charge on the left plate and current as a function of time. Here, Q_{\max} is the maximum charge the capacitor can have in such a circuit.



$dq < 0$ on left plate
 (C is charging)
 (negativeness increases)

$$q = Q_{\max} \cos(\omega t + \phi) \quad , \quad \omega = \frac{1}{\sqrt{LC}}$$

$$q(0) = Q_{\max} \cos \phi = -Q_{\max}/2$$

$$\cos(\phi) = -1/2$$

$$\phi = \frac{2\pi}{3} \quad \text{or} \quad \frac{4\pi}{3} \equiv -\frac{2\pi}{3}$$

$$q = Q_{\max} \cos\left(\omega t \pm \frac{2\pi}{3}\right)$$

since $dq < 0$ (capacitor charging)
 \downarrow
 \equiv the solution should decrease w.r. $t > 0$

$$\Rightarrow \phi = +\frac{2\pi}{3}$$


Closed book. No calculators are to be used for this quiz.
Quiz duration: 10 minutes

Name:

Student ID:

Signature:

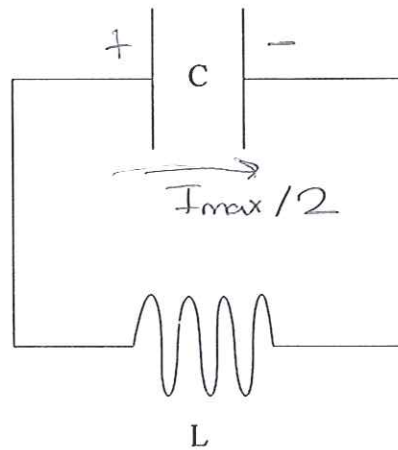Consider the LC circuit shown in the figure. If the current $i = I_{\max} / 2$ is known to flow in the clockwise direction and the charge on the left plate is known to be positive at time $t = 0$, find expressions for the current and charge on the right plate of the capacitor as a function of time. Here, I_{\max} is the maximum current in such a circuit.



charge at right plate < 0 at time $t = 0$

$$q(t) = Q_{\max} \cos(\omega t + \phi)$$

$$i(t) = -Q_{\max} \omega \sin(\omega t + \phi) = I_{\max} \sin(\omega t + \phi)$$

$$q(0) = Q_{\max} \cos(\phi) < 0$$

$$i(0) = I_{\max} \sin(\phi)$$

$$= \frac{I_{\max}}{2}$$

$$\Rightarrow \sin \phi = \frac{1}{2} \Rightarrow \phi = \frac{\pi}{6} \text{ or } \pi - \frac{\pi}{6}$$

$$dq > 0, i > 0$$

$$\phi = \pi - \frac{\pi}{6} = \frac{5\pi}{6}$$

$$\Rightarrow q(t) = Q_{\max} \cos\left(\omega t + \frac{5\pi}{6}\right)$$

$$i(t) = I_{\max} \sin\left(\omega t + \frac{5\pi}{6}\right)$$

Closed book. No calculators are to be used for this quiz.


Quiz duration: 10 minutes

Name:

Student ID:

Signature:

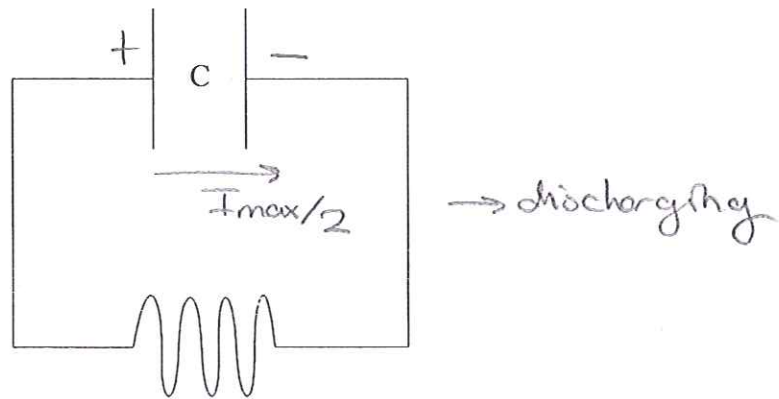Consider the LC circuit shown in the figure. If the current $i = I_{\max} / 2$ is known to flow in the clockwise direction and the charge on the left plate is known to be positive at time $t = T/2$ where T is the period of an LC circuit, find expressions for the current and charge on the right plate of the capacitor as a function of time. Here, I_{\max} is the maximum current in such a circuit.



$$q(t) = Q_{\max} \cos(\omega t + \phi) \quad \text{(on the right plate of capacitor)}$$

$$i(t) := \frac{dq}{dt} = -\omega Q_{\max} \sin(\omega t + \phi)$$

$$T = \frac{2\pi}{\omega} \Rightarrow \frac{T}{2} = \frac{\pi}{\omega} \quad , \quad I_{\max} = -\omega Q_{\max}$$

$$i\left(\frac{T}{2}\right) = -\omega Q_{\max} \sin\left(\omega \frac{\pi}{\omega} + \phi\right) = \frac{I_{\max}}{2} \Rightarrow \sin(\pi + \phi) = \frac{1}{2}$$

$$\Rightarrow \phi = -\frac{\pi}{6} \quad \text{or} \quad \frac{\pi}{6} - \pi$$

\Rightarrow Since $dq > 0$ (negativeness on right plate decreases)

$$i > 0 \Rightarrow i(t) = I_{\max} \sin\left(\omega t - \frac{5\pi}{6}\right)$$

$$q(t) = -\frac{I_{\max}}{\omega} \cos\left(\omega t - \frac{5\pi}{6}\right)$$