

PHYS 102: General Physics - KOÇ UNIVERSITY
College of Sciences
Quiz 5 Nov 11, 2016

Closed book. No calculators are to be used for this quiz.


Quiz duration: 15 minutes

Name:

ID #:

Signature:

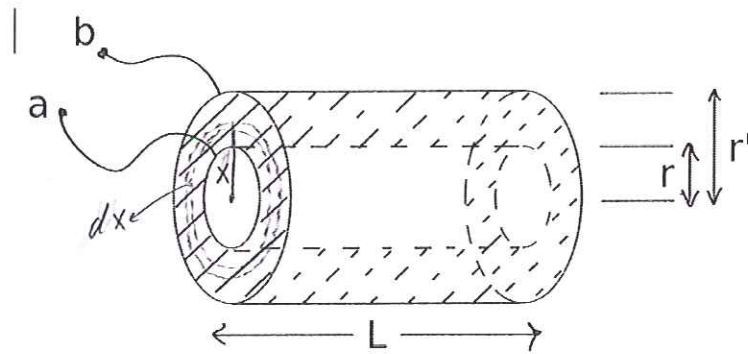Q. The (shaded) volume between two coaxial conducting cylinders with radii r and r' ($r < r'$) is filled with a material with resistivity ρ . Express the resistance R_{ab} measured between the cylinders as an integral. Hint: Consider the object as composed of stacked cylindrical sheets of infinitesimal thickness which are connected in series.



$$A = 2\pi x L$$

$$dR = \frac{\rho dx}{2\pi x L} \Rightarrow R = \frac{\rho}{2\pi L} \int_r^{r'} \frac{dx}{x} = \frac{\rho}{2\pi L} \ln\left(\frac{r'}{r}\right)$$

PHYS 102: General Physics - KOÇ UNIVERSITY
 College of Sciences
 Quiz 5 Nov 11, 2016

Closed book. No calculators are to be used for this quiz.


Quiz duration: 15 minutes

Name:

ID #:

Signature:

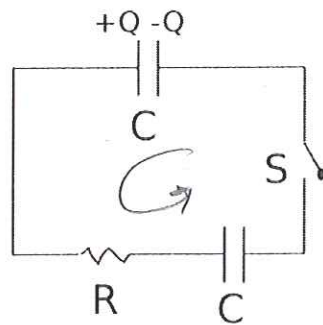Q. The upper capacitor in the circuit below carries an initial charge of Q while the lower capacitor is initially uncharged. The switch is closed at $t = 0$. Write down the differential equation for the charge $q(t)$ on the lower capacitor by using Kirchoff's loop rule.



$q(t)$ is the charge of lower capacitor, Then the charge of upper capacitor is $Q - q(t)$.

$$\text{Loop: } \frac{Q - q(t)}{C} - IR - \frac{q(t)}{C} = 0$$

$$I = \frac{dq(t)}{dt} \Rightarrow \frac{Q - q(t)}{C} - R \frac{dq(t)}{dt} - \frac{q(t)}{C} = 0$$

$$\frac{dq(t)}{dt} + \frac{2}{RC} q(t) - \frac{Q}{RC} = 0 \quad \text{Differential equation}$$

$$\text{solution} \Rightarrow q(t) = \frac{Q}{2} (1 - e^{-2t/RC})$$

PHYS 102: General Physics - KOÇ UNIVERSITY
College of Sciences
Quiz 5 Nov 11, 2016

Closed book. No calculators are to be used for this quiz.


Quiz duration: 15 minutes

Name:

ID #:

Signature:

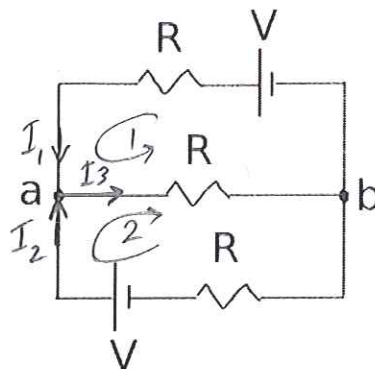Q. Find the electric potential difference V_{ab} in the circuit below.



$$\text{Point } a : I_1 + I_2 = I_3$$

$$\text{Loop 1 : } V - I_1 R - I_3 R = 0$$

$$\text{Loop 2 : } V - I_3 R - I_2 R = 0$$

$$\Rightarrow I_1 = \frac{1}{3} \frac{V}{R} , I_2 = \frac{1}{3} \frac{V}{R} , I_3 = \frac{2}{3} \frac{V}{R}$$

$$\Rightarrow V_a - I_3 R = V_b \rightarrow V_{ab} = V_a - V_b = I_3 R = \frac{2}{3} V$$

PHYS 102: General Physics - KOÇ UNIVERSITY
 College of Sciences
 Quiz 4 Nov 11, 2016

Closed book. No calculators are to be used for this quiz.

Quiz duration: 15 minutes


Name:

ID #:

Signature:

Q. The circuit below is called a *Wheatstone Bridge*. It is used to find the resistance of an unknown resistor (here R). Express R in terms of the resistances P , S , T , if these three are chosen such that the ammeter in the middle reads zero current (that is, there is zero potential difference across its terminals).
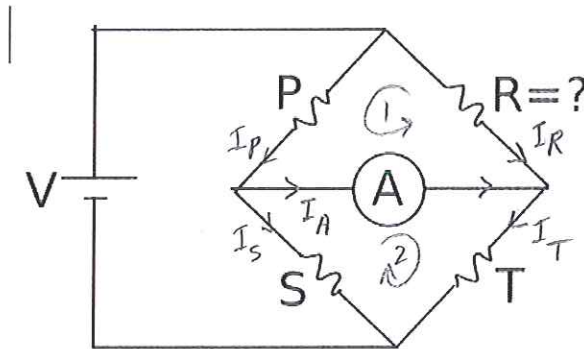
$$\begin{cases} I_P = I_A + I_S \\ I_R + I_A = I_T \end{cases}$$



$$\begin{cases} \text{Loop 1: } -I_P P - I_A R_A + I_R R = 0 \\ \text{Loop 2: } I_S S - I_A R_A - I_T T = 0 \end{cases}$$

$$\text{when } I_A = 0 \Rightarrow \begin{cases} I_R R = I_P P \\ I_S S = I_T T \end{cases} \Rightarrow R = \frac{I_P P I_T T}{I_R I_S S}$$

$$\Rightarrow R = \frac{P \cdot T}{S}$$