

PHYS 102: General Physics - KOÇ UNIVERSITY
 College of Sciences
 Quiz 4 Nov 4, 2016

Closed book. No calculators are to be used for this quiz.


Quiz duration: 15 minutes

Name:


ID #:

Signature:

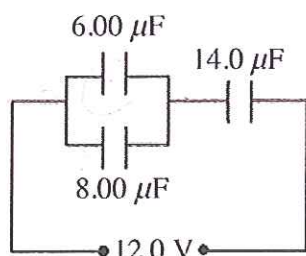
Q. Two capacitors of capacitance $6.00 \mu\text{F}$ and $8.00 \mu\text{F}$ are connected in parallel. The combination is then connected in series with a 12.0-V voltage source and a $14.0 \mu\text{F}$ capacitor, as shown in the figure. Find the charge on the $6.00 \mu\text{F}$ capacitor.




For parallel capacitors:

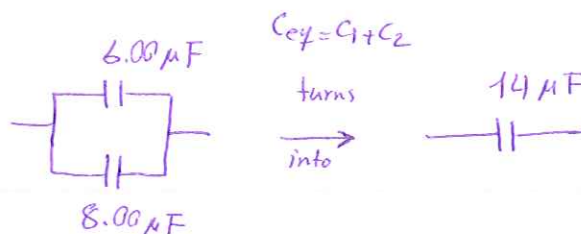

So the circuit will be like

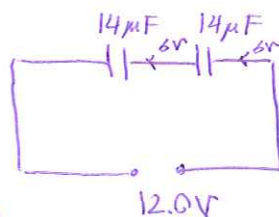

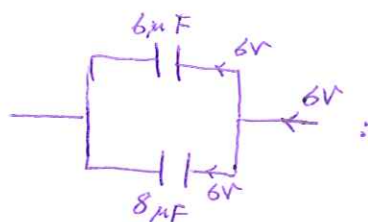They are series so every capacitor gets 6V!



For parallel capacitors, each will get same 6V voltage.

$$\text{Finally } \Rightarrow Q = CV = (6.00 \mu\text{F})(6 \text{ V}) = \underline{36 \mu\text{C}}$$

PHYS 102: General Physics - KOÇ UNIVERSITY
 College of Sciences
 Quiz 4 Nov 4, 2016

Closed book. No calculators are to be used for this quiz.

Quiz duration: 15 minutes

Name:


ID #:

Signature:

Q. Capacitance can be calculated also for a *single* conductor, by assuming the second conductor as being located at infinity. Using $u = \epsilon_0 E^2/2$ for electric field energy density and $U = Q^2/2C$ for the stored energy in a capacitor, calculate the capacitance of a conducting sphere with radius R .

Hint: Evaluate U by integrating the field energy density over spherical shells of volume $dV = 4\pi R^2 dr$.
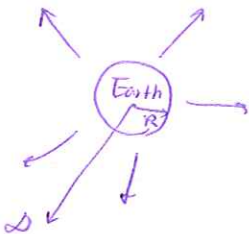
$$\begin{cases} u = \epsilon_0 \frac{E^2}{2} \\ u = \frac{Q^2}{C} \end{cases} \Rightarrow U = \int u dV$$



$$E = \frac{1}{4\pi\epsilon_0} \cdot \frac{Q}{R^2} \rightarrow E^2 = \frac{1}{(4\pi\epsilon_0)^2} \cdot \frac{Q^2}{R^4}$$

Using hint: $U = \int u dV = \int \frac{1}{2} \epsilon_0 E^2 (4\pi R^2 dr) = \frac{1}{2} \epsilon_0 \int \frac{1}{(4\pi\epsilon_0)^2} \cdot \frac{Q^2}{R^4} (4\pi R^2 dr)$

$$U = \frac{1}{2} \cdot \frac{Q^2}{4\pi\epsilon_0} \int_R^{\infty} \frac{dr}{R^2} = \frac{1}{2} \cdot \frac{Q^2}{4\pi\epsilon_0} \left[-\frac{1}{r} \right]_R^{\infty} = \frac{1}{2} \cdot \frac{Q^2}{4\pi\epsilon_0} \left(\frac{1}{\infty} + \frac{1}{R} \right)$$

Earth Surface
infinity
Zero

$$U = \frac{Q^2}{2} \cdot \frac{1}{4\pi\epsilon_0 R} \xrightarrow[\text{that}]{\text{we knew}} U = \frac{Q^2}{2C} \quad (\text{II})$$

$$(\text{I}), (\text{II}) \Rightarrow \boxed{C = 4\pi\epsilon_0 R}$$

Capacitance of Earth

PHYS 102: General Physics - KOÇ UNIVERSITY
College of Sciences
Quiz 4 Nov 4, 2016

Closed book. No calculators are to be used for this quiz.

Quiz duration: 15 minutes

Name:

ID #:

Signature:

Q. Capacitance can be calculated also for a *single* conductor, by assuming the second conductor as being located at infinity. Use this idea and the definition $C = Q/V$ to calculate the capacitance of a conducting sphere with radius R . Substitute $\epsilon_0 \simeq 9 \times 10^{-12}$ F/m and $R = 6400$ km to estimate Earth's (a good conductor) capacitance.

$$C = \frac{Q}{V} \quad \rightarrow \quad \text{for Earth} \quad V = k \frac{Q}{R}$$

$$\Rightarrow C = \frac{Q}{k \left(\frac{Q}{R} \right)} = \frac{R}{k} \Rightarrow \boxed{C = \frac{R}{k}} \quad \text{Capacitance of sphere with radius } R$$

$$k = \frac{1}{4\pi\epsilon_0} \quad \rightarrow \quad \boxed{C = 4\pi\epsilon_0 R} \quad \checkmark$$

PHYS 102: General Physics - KOÇ UNIVERSITY
 College of Sciences
 Quiz 4 Nov 4, 2016

Closed book. No calculators are to be used for this quiz.

Quiz duration: 15 minutes


Name:

ID #:

Signature:

Q. A parallel-plate capacitor with plate area A has the space between the plates filled with two slabs of dielectric, one with dielectric constant κ_1 and one with κ_2 as shown in the figure. Each slab has thickness $d/2$, where d is the plate separation. Find the capacitance in terms of ϵ_0 and given parameters.

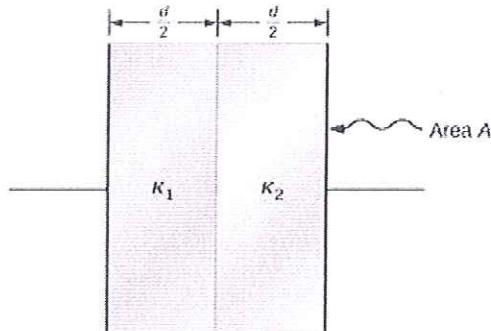Hint: Every point on the interface between the two dielectrics has the same electric potential. Then, one can assume them to be separated by a conductor surface, and think of the system as composed of two capacitors.



We can assume two series capacitors:

$$\left. \begin{aligned} C_1 &= \kappa_1 \frac{\epsilon_0 A}{(d/2)} = \frac{2\kappa_1 \epsilon_0 A}{d} \\ C_2 &= \kappa_2 \frac{\epsilon_0 A}{(d/2)} = \frac{2\kappa_2 \epsilon_0 A}{d} \end{aligned} \right\} \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\frac{1}{C_{eq}} = \frac{d}{2\epsilon_0 \kappa_1 A} + \frac{d}{2\epsilon_0 \kappa_2 A} = \frac{d}{2\epsilon_0 A} \left(\frac{\kappa_1 + \kappa_2}{\kappa_1 \kappa_2} \right) \Rightarrow C_{eq} = \frac{2\epsilon_0 A}{d} \left(\frac{\kappa_1 \kappa_2}{\kappa_1 + \kappa_2} \right)$$

PHYS 102: General Physics - KOÇ UNIVERSITY
 College of Sciences
 Quiz 4 Nov 4, 2016

Closed book. No calculators are to be used for this quiz.

Quiz duration: 15 minutes

Name:


ID #:

Signature:

Q. In the circuit shown below, with the switch S open, the $6.0 \mu\text{F}$ capacitor has an initial charge of $6.0 \mu\text{C}$ while the $3.0 \mu\text{F}$ capacitor is uncharged. The switch is then closed and left closed for a long time. Calculate the initial and final values of the total electric energy stored in the two capacitors.

Initial charge

$$Q_0 = 6.0 \mu\text{C}$$

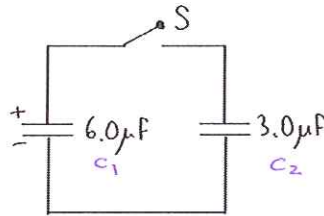

$$U = \frac{Q^2}{2C}$$

$$\frac{C_1}{C_2} = \frac{Q_1}{Q_2} = \frac{6.0 \mu\text{F}}{3.0 \mu\text{F}} = 2 \Rightarrow \frac{Q_1}{Q_2} = 2$$

$$\Rightarrow Q_0 = Q_1 + Q_2 \quad (\text{switch closed, capacitors share charge})$$

$$\Rightarrow Q_0 = Q_1 + \frac{Q_1}{2} \rightarrow Q_0 = \frac{3}{2} Q_1 \Rightarrow \begin{cases} Q_1 = 4.0 \mu\text{C} \\ Q_2 = \frac{1}{3} Q_0 \Rightarrow Q_2 = 2.0 \mu\text{C} \end{cases}$$

Energy stored: 1) When switch is open: $U_0 = \frac{Q_0^2}{2C_1} = \frac{(6.0 \mu\text{C})^2}{2 \times 6.0 \mu\text{F}} = 3 \times 10^{-6} \text{ J}$

2) When switch is closed:

$$U_{\text{tot}} = U_1 + U_2 = \frac{Q_1^2}{2C_1} + \frac{Q_2^2}{2C_2} = \frac{7.33 \times 10^{-6} \text{ J}}{2 \times (6.0 \mu\text{F})} + \frac{5 \times 10^{-7} \text{ J}}{2 \times (3.0 \mu\text{F})} = 1.83 \times 10^{-6} \text{ J}$$

Energy in (1) and (2) are not the same, so we don't have energy conservation!