

Chapter 26: Direct Current Circuits

Direct current (dc) circuits:


Current, electric potential in the circuit has no time dependence

5V DC Power Supply

9V DC Power Supply


Alternating current (ac) circuits

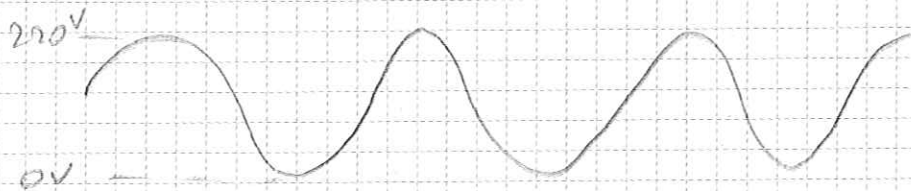Current, electric potential in the circuit oscillates with time.





220V AC Voltage

Resistors In Series and Parallel:

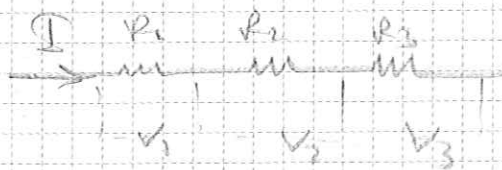

$$\begin{aligned}
 V &= V_1 + V_2 + V_3 \\
 &= IR_1 + IR_2 + IR_3 \\
 &= I(R_1 + R_2 + R_3) \\
 &\quad R_{eq}
 \end{aligned}$$

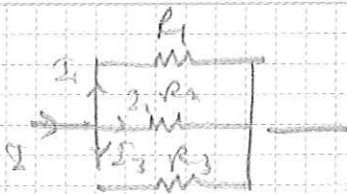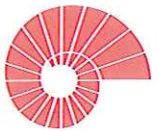$R_{eq} = R_1 + R_2 + R_3 + \dots$
Equivalent resistance of resistors connected in series



$I = I_1 + I_2 + I_3$ ← conservation of charge flow!

$V_1 = V_2 = V_3 = V$



$\Rightarrow I = I_1 + I_2 + I_3$

$= \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) = \frac{V}{R_{eq}}$

$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$

Equivalent resistance of resistors connected in parallel.

26.2 Kirchoff's Rules:

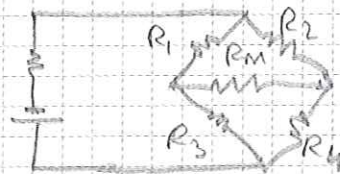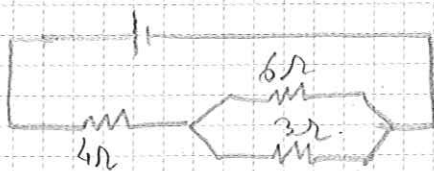

Many practical resistor networks cannot be solved using the simple series-parallel resistor reduction techniques.

Kirchoff's Rules help analyzing complicated circuits.

Kirchoff's Rules:


(i) The algebraic sum of the currents into any junction is equal to zero.

$\sum I = 0$, junction rule.


Junction: A point in the circuit where three or more conductors meet.



$I_1 + I_2 + I_3 = 0 \Rightarrow I_3 = -(I_1 + I_2)$
flows in the opposite direction

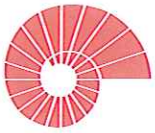

Prob 26.92

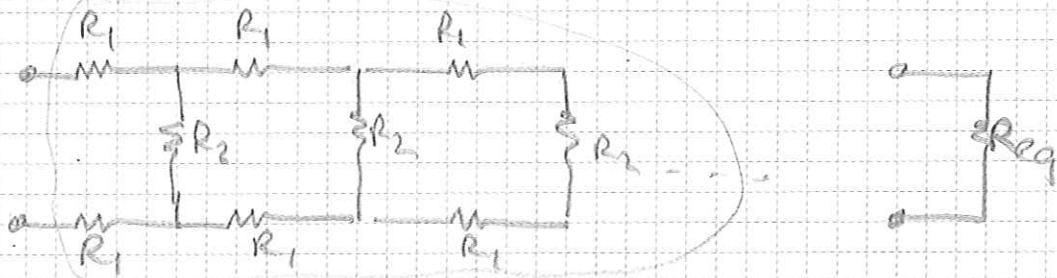

Equivalent resistance?



$$\frac{1}{R_2} + \frac{1}{R_{eq}} = \frac{R_2 + R_{eq}}{R_2 R_{eq}}$$

$$\Rightarrow R_{eq} = 2R_1 + \frac{R_2 R_{eq}}{R_2 + R_{eq}}$$

$$\Rightarrow (R_{eq} - 2R_1)(R_{eq} + R_2) = R_{eq} R_2$$


$$\Rightarrow R_{eq}^2 + R_{eq}(R_2 - 2R_1 - R_2) - 2R_1 R_2 = 0$$

$$R_{eq}^2 - 2R_1 R_{eq} - 2R_1 R_2 = 0$$

$$\Rightarrow R_{eq} = \frac{2R_1 \pm \sqrt{4R_1^2 + 8R_1 R_2}}{2} = R_1 \pm \sqrt{R_1^2 + 2R_1 R_2}$$

$$\Rightarrow \text{Solution is } \boxed{R_{eq} = R_1 + \sqrt{R_1^2 + 2R_1 R_2}}$$
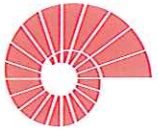
$$R_{eq} = R_1 - \sqrt{R_1^2 + 2R_1 R_2} \quad \text{is not a physical solution}$$




(1) The algebraic sum of the potential differences in any loop (associated with emfs, and resistive elements) must equal zero,

$$\sum V = 0, \text{ Kirchoff's Loop Rule}$$

Loop: A closed conducting path in the circuit.

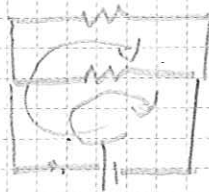
This is clear because electrostatic force is conservative.



$$W_{\text{elec}} = -\Delta U = U_a - U_c = 0$$

How to solve circuits using Kirchoff's laws:

Given a circuit:

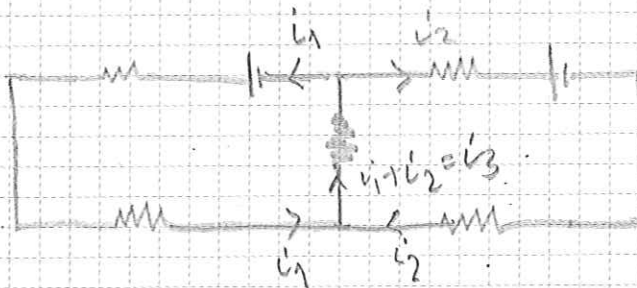


- Label currents with their directions. The directions need not be the correct directions.


Write the Kirchoff's Junction Law in the junctions:

$$i_1 + i_2 = i_3$$

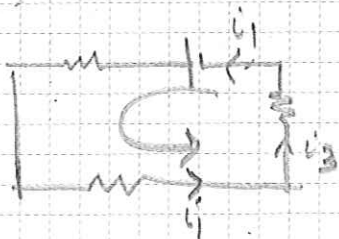- Choose any closed loop in the circuit, designate a direction of travel.




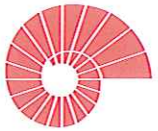Travel around the loop adding potential differences due to different elements.




Potential differences due to different elements:

emf

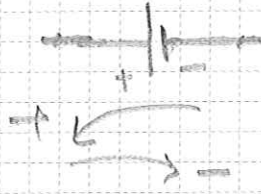


emf is counted + if you traverse from - to +.
emf is counted - if you traverse from + to -.

Resistance

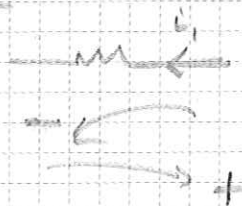

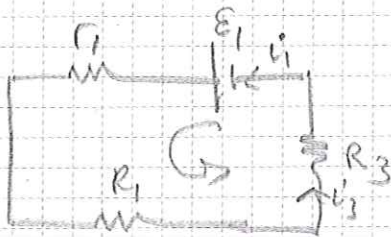Resistance is - if you traverse in the same direction as current flow.
Resistance is + if you traverse in the direction opposite to current.




$$V_a + E_1 - i_1 R_2 - i_1 R_1 - i_3 R_3 = V_a$$

$$E_1 - i_1 R_2 - i_1 R_1 - i_3 R_3 = 0$$

* Write as many linearly independent equations as the number of currents to solve for the circuit.

Ex 26.4; Consider the circuit:


What are the currents?

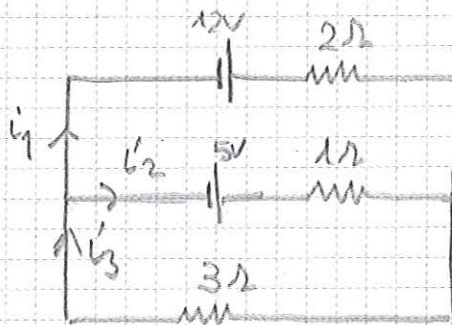


(i) Label currents with directions

(ii) Apply Kirchhoff's Junction Law

$$i_1 + i_2 = i_3$$

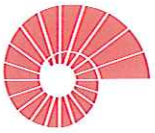


Apply Kirchhoff's Loop Law:

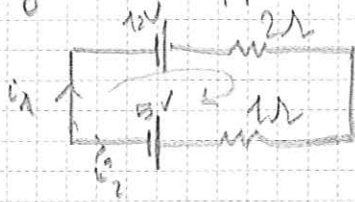


$$12 - 2i_1 + i_2 - 5 = 0$$

$$7 - 2i_1 + i_2 = 0$$

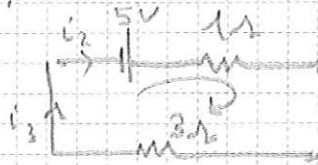

$$5 - i_2 - 3i_3 = 0$$

$$5 - i_2 - 3i_3 = 0$$

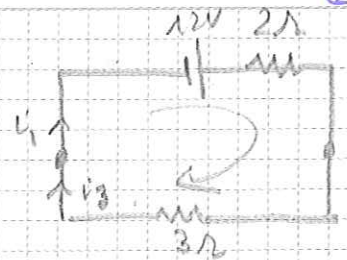

$$12 - 2i_1 - 3i_3 = 0$$

$$12 - 2i_1 - 3i_3 = 0$$

2 linearly independent equations,

Add the first 2:

$$7 - 2i_1 + i_2 = 0$$

$$5 - i_2 - 3i_3 = 0$$

$$12 - 2i_1 - 3i_3 = 0 \quad \checkmark$$

3. Use the equations:

$$i_1 + i_2 = i_3$$

$$7 - 2i_1 + i_2 = 0$$


$$5 - i_2 - 3i_3 = 0 \Rightarrow 5 - i_2 - 3i_1 - 3i_2 = 5 - 3i_1 - 4i_2 = 0$$

$$\Rightarrow i_2 = \frac{5}{4} - \frac{3}{4}i_1$$

$$\Rightarrow 7 - 2i_1 + \frac{5}{4} - \frac{3}{4}i_1 = \frac{33}{4} - \frac{11}{4}i_1 = 0 \Rightarrow \underline{i_1 = 3A}$$



$$i_2 = \frac{5}{4} - \frac{3}{4}i_1 = \frac{5}{4} - \frac{9}{4} = \underline{-1A}$$

$$\underline{i_3 = 2A}$$

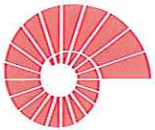

Prob 26.77

Show that $X = \frac{MP}{N}$

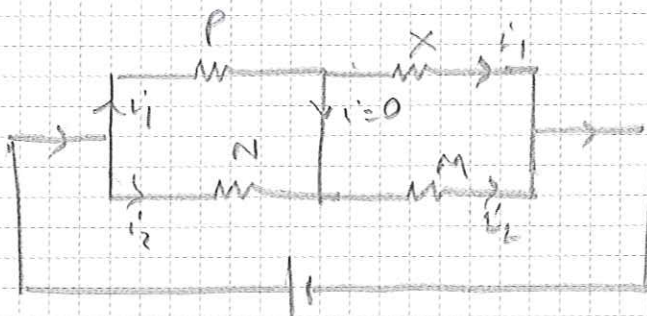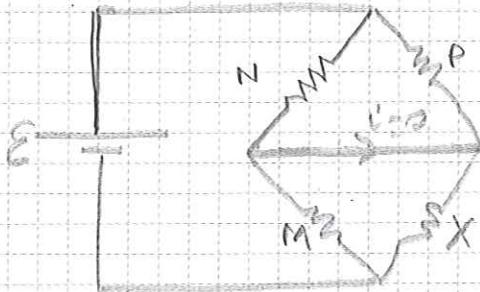

$$i_1 P = i_2 N \rightarrow \frac{i_1}{i_2} = \frac{N}{P}$$

$$i_1 X = i_2 M$$


$$\frac{i_1}{i_2} = \frac{M}{X}$$

$$\frac{M}{X} = \frac{N}{P} \rightarrow \boxed{X = \frac{MP}{N}}$$


Wheatstone Bridge

Ex 26.6:


Find the currents in each resistor.

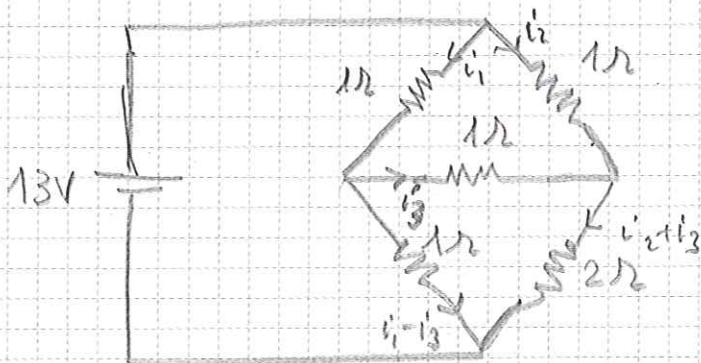


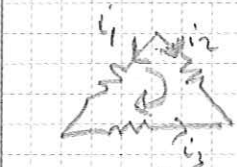
3 Unknowns $i_1, i_2, i_3 \Rightarrow$ Write 3 equations using Kirchhoff's Loop Law:



$$-i_2 + i_3 - 1i_1 = 0$$

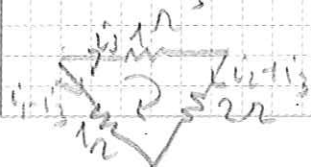

$$-2(i_2 + i_3) + i_1 - i_3 - i_3 = 0$$

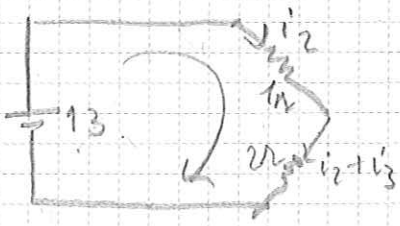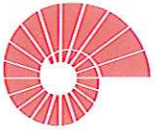

$$-i_2 - 2(i_2 + i_3) + 13 = 0$$

$$\Rightarrow i_1 - i_2 + i_3 = 0$$

$$i_1 - 2i_2 - 4i_3 = 0$$

$$-3i_2 - 2i_3 = -13$$

$$2i_1 - i_3 = 13 \Rightarrow i_3 = 2i_1 - 13$$


$$\Rightarrow i_1 - i_2 + 2i_1 - 13 = 0 \Rightarrow 3i_1 - i_2 = 13$$

$$i_1 - 2i_2 - 4(2i_1 - 13) = 0 \Rightarrow -7i_1 - 2i_2 = -52$$

$$-13i_1 = -52 - 26 = -78 \Rightarrow i_1 = 6A$$


$$i_2 = 3i_1 - 13 = 18 - 13 = 5A //$$

$$i_3 = 2i_1 - 13 = 12 - 13 = -1A //$$

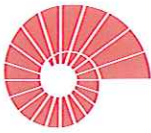

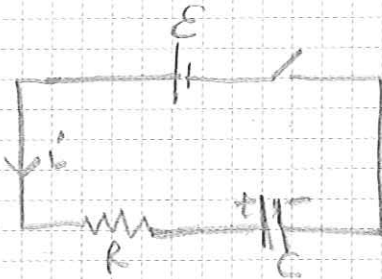26.4 R-C Circuits

Circuits that involve charging or discharging of capacitors.



Charging a Capacitor:

Consider the capacitor being initially uncharged.

Then at time $t=0$ the switch is closed.

→ Capacitor then starts being charged.

$$C = \frac{Q}{V} \Rightarrow Q = CV \Rightarrow \frac{dQ}{dt} = C \frac{dV}{dt} = i$$

$$E - iR - V = 0 \Rightarrow E - R C \frac{dV}{dt} - V = 0$$



$$RC \frac{dV}{dt} + V - E = 0 \Rightarrow \int_0^t \frac{dV}{E-V} = \int_0^t \frac{dt}{RC}$$



$$\Rightarrow -\ln(E-V) \Big|_0^t = + \frac{t}{RC} \Rightarrow -\ln(E-V) - \ln(E) = \frac{t}{RC}$$

$$\Rightarrow -\ln\left(\frac{E-V}{E}\right) = \frac{t}{RC} \Rightarrow \frac{E-V}{E} = e^{-t/RC} \Rightarrow V = E - E e^{-t/RC}$$

$$Q = CV \Rightarrow \frac{dQ}{dt} = C E (1 - e^{-t/RC}) //$$

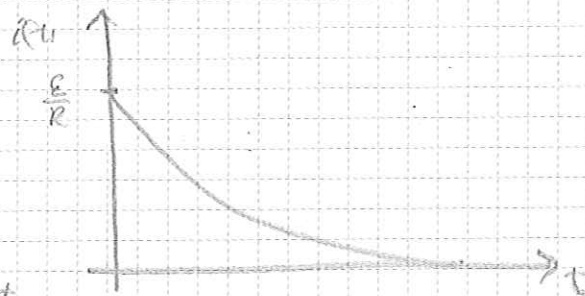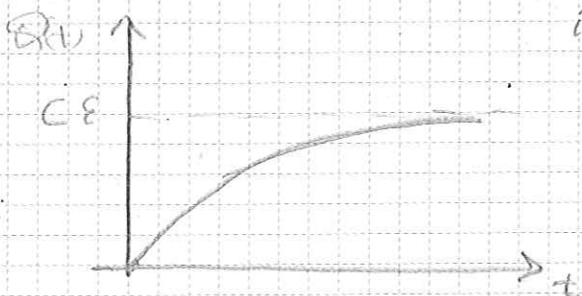
$$i = \frac{dQ}{dt} = \frac{dQ}{dt} = \frac{d}{dt} \left(\frac{1}{R} e^{-t/RC} \right) = \frac{E}{R} e^{-t/RC} //$$



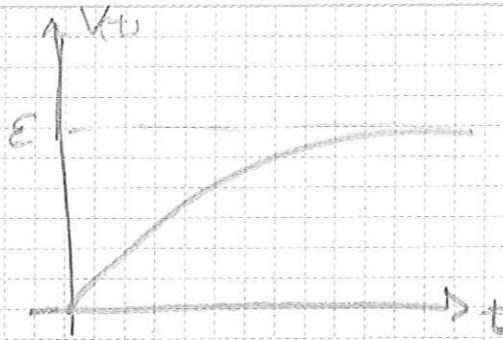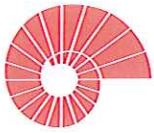

At time $t=RC$, current drops to $\frac{1}{e}$ of its initial value
 $\tau=RC$ is called the time constant of the R-C circuit.

Discharging a Capacitor:

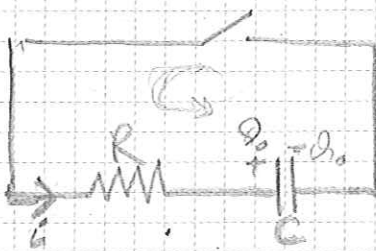

Consider an initially charged capacitor.
 At time $t=0$ the switch is closed.

$$C = \frac{Q(t)}{V(t)}$$



$$V(t) + i(t)R = 0 \Rightarrow \frac{Q(t)}{C} + \frac{dQ(t)}{dt}R = 0$$

$$\Rightarrow Q(t) = -RC \frac{dQ(t)}{dt} \Rightarrow \frac{dQ(t)}{Q(t)} = -\frac{dt}{RC} \Rightarrow \ln Q \Big|_{Q_0}^Q = -\frac{t}{RC} \Big|_0^t$$

$$\Rightarrow \ln \left(\frac{Q}{Q_0} \right) = -\frac{t}{RC} \Rightarrow \boxed{Q = Q_0 e^{-t/RC}}$$

$$V(t) = \frac{Q(t)}{C} = \boxed{\frac{Q_0}{C} e^{-t/RC}}$$
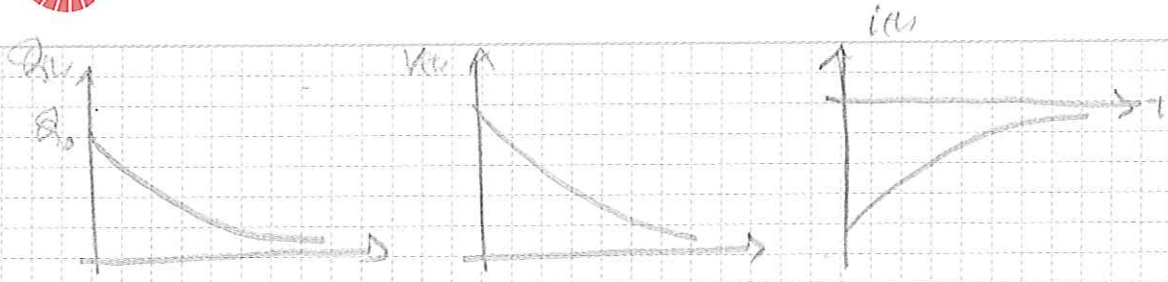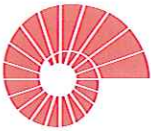
$$i(t) = + \frac{V(t)}{R} = \boxed{+ \frac{Q_0}{RC} e^{-t/RC}}$$




Time constant : $\tau = RC$

time at which the stored charge drops to $\frac{1}{e}$ of its initial value.

Energy Considerations

In charging of a capacitor:

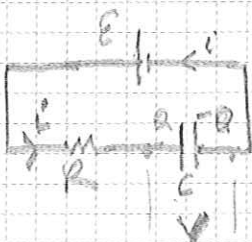

Ei , rate at which the battery delivers energy to the circuit.

$$Ei = i^2R + V\dot{Q} = i^2R + \frac{Q}{C}\dot{Q}$$

Total energy supplied by the battery during charging of the capacitor:

$$\int P dt = \int E \frac{dQ}{dt} dt = \int E dQ = EQ_f$$

↑ Final charge of the capacitor


Total energy stored in the capacitor

$$U = \frac{1}{2} Q_f V = \frac{1}{2} Q_f E$$

← Half of the energy is stored in the capacitor. Half is dissipated in the resistor.

$$U = \int \frac{Q}{C} i dt = \int \frac{Q}{C} \frac{dQ}{dt} dt = \int \frac{Q}{C} dQ = \frac{1}{2C} Q_f^2 = \frac{1}{2} Q_f E$$

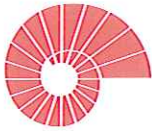∴ This ^{result} does not depend on the values of R , E and C .



Discharging of a Capacitor



Power dissipated by the capacitor:

$$i \frac{dQ}{dt} = i^2 R$$

$$\int i \frac{dQ}{dt} dt = \int -\frac{dQ}{C} = -\frac{1}{2C} Q^2 \Big|_{Q_0}^0 = +\frac{1}{2C} Q_0^2 \leftarrow \text{Total energy}$$

Capacitor delivers to the circuit.


$$\int i^2 R dt = \int \frac{Q_0^2}{RC^2} e^{-2t/RC} R dt = \frac{Q_0^2}{RC^2} \int e^{-2t/RC} dt$$

$$= \frac{Q_0^2}{RC^2} \left[-\frac{RC}{2} e^{-2t/RC} \right]_0^\infty = \frac{Q_0^2}{C} \left(\frac{-1}{2} \right) (0 - 1) = \frac{Q_0^2}{2C}$$

Energy dissipated in the resistor

RC - Circuits:

Charging a capacitor

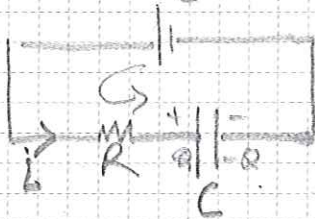


$\frac{dQ}{dt} = i$ ← direction is important

$$E - iR - \frac{Q}{C} = 0 \Rightarrow E = \frac{dQ}{dt} R + \frac{Q}{C}$$

$$\Rightarrow Q = CE (1 - e^{-t/RC})$$

$$i = \frac{dQ}{dt} = \frac{E}{R} e^{-t/RC}$$

Discharging a capacitor:

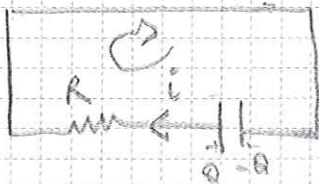

$$i = -\frac{dQ}{dt}$$

$$\rightarrow -iR + \frac{Q}{C} = 0$$


$$\Rightarrow -\frac{dQ}{dt} R = -\frac{Q}{C} \Rightarrow Q = Q_0 e^{-t/RC}$$

$$V = \frac{Q}{C} = \frac{Q_0}{C} e^{-t/RC}$$

$$i(t) = \frac{dQ}{dt} = \frac{Q_0}{RC} e^{-t/RC}$$

RC - time constant

Energy Considerations:

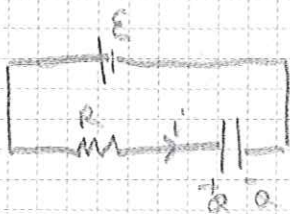

rate of energy dissipated is: $i^2 R + Vi$

rate of energy delivered is: Ei

stored in the capacitor: $U = \int V dq = \int \frac{q}{C} dq = \frac{1}{C} \frac{Q_f^2}{2}$

$$= \frac{1}{2} Q_f V_f = \frac{1}{2} Q_f E$$

delivered by E: $\int E i dt = \int E dq = EQ_f$