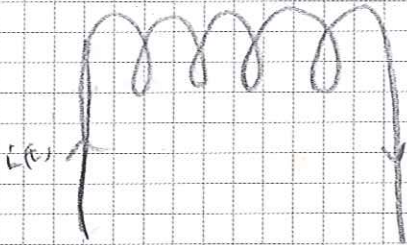




Chapter 30: Inductance

Consider a copper wire wrapped to form a coil



Changing current in the coil will induce an emf in the coil itself.


Such a coil is called an inductor and the relationship between the current and emf reveals the inductance.

Total induced emf $\Rightarrow \mathcal{E} = -N \frac{d\Phi_B}{dt}$
Faraday's Law

$$i(t) = \frac{N}{L} \Phi_B \Rightarrow \frac{d\Phi_B}{dt} = \frac{L}{N} \frac{di}{dt}$$

we define $L = \frac{N \Phi_B}{i}$ as ^{the} self-inductance
Flux flowing through one winding
with this definition, Faraday's Law can be written

as $\mathcal{E} = -L \frac{di}{dt}$

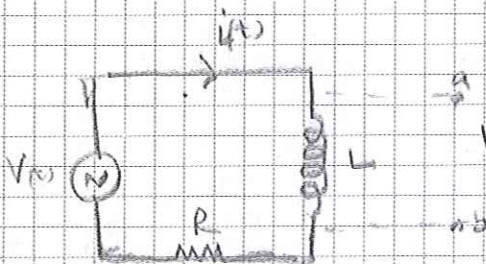


$$V_{ab} = L \frac{di}{dt}$$


Inductor opposes to the variations in the current flowing through the circuit.

For a solenoid:

$$B = \mu_0 n i \Rightarrow \Phi_B = \mu_0 n i A \Rightarrow L = \frac{N \mu_0 n^2 A}{l} = \mu_0 n N A = \mu_0 \frac{N^2 A}{l}$$

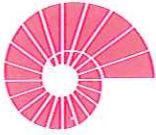

Ex. 30.3:

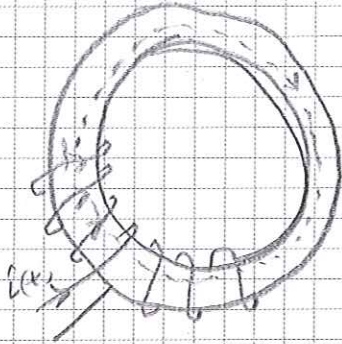

A toroidal solenoid with cross-sectional area A and mean radius r is closely wound with N turns.
What is L ?

Use $L = \frac{N\Phi_B}{i}$

\vec{B} is along the tangential direction with constant magnitude.

Remember: $\oint \vec{B} \cdot d\vec{\ell} = B(2\pi r) = \mu_0 N i \Rightarrow B(2\pi r) = \frac{\mu_0 N i}{2\pi r}$

$\Rightarrow \Phi_B = \int \vec{B}(r) \cdot d\vec{A} \approx A \frac{\mu_0 N i}{2\pi r}$ — mean radius


flux through one winding

$\Rightarrow L = \frac{N\Phi_B}{i} = \frac{N}{i} \frac{A \mu_0 N i}{2\pi r} = \frac{\mu_0 N^2 A}{2\pi r} //$

Mutual Inductance:

A changing current in one coil can also induce an emf in another coil.

Consider two coils:

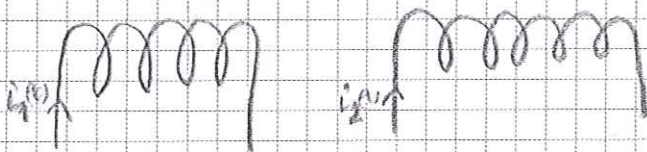

$\mathcal{E}_2(t) = -N_2 \frac{d\Phi_{12}}{dt}$



We define the mutual inductance:


$$M_{21} = \frac{N_2 \Phi_2}{I_1}, \text{ mutual inductance}$$

compare with $(L = \frac{N\Phi}{I})$

$$\Rightarrow \boxed{E_2(t) = -M_{21} \frac{di_1}{dt}}$$

induced emf in coil 2 due to changing current in coil 1.

Ex 32.1:

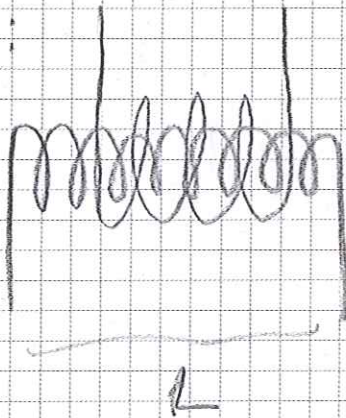

A long solenoid with length L and cross-sectional area A is closely wound with N_1 turns. A coil with N_2 turns surrounds the first coil.

What is the mutual inductance?

$$M_{21} = \frac{N_2 \Phi_2}{I_1}$$


$$\begin{aligned} \Phi_2 &= BA, & B &= \mu_0 \mu_1 \frac{N_1}{L} \\ &= \mu_0 \mu_1 \frac{N_1}{L} A \end{aligned}$$

$$\Rightarrow \boxed{M_{21} = \mu_0 \frac{N_1 N_2}{L} A}$$



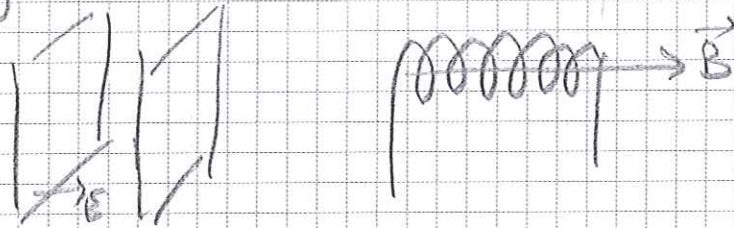
30.3 Magnetic Field Energy!

An inductor carrying current has energy stored in it.
In a capacitor an electric field is built up due to the stored energy.



In an inductor magnetic field is built up due to the stored energy.

Consider an inductor in a circuit:

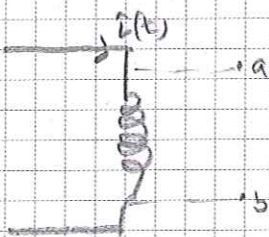

$$V_{ab} = L \frac{di}{dt}$$

Power stored in the inductor

$$\hookrightarrow P = V_{ab} i = L i \frac{di}{dt} = \frac{dU}{dt}$$

$$\Rightarrow \int_0^U dU = \int_0^I L i di$$


$$\boxed{U = \frac{1}{2} L i^2}$$

Energy stored in an inductor.

⇒ When current increases from 0 to I energy is stored in the inductor.

When current decreases from I to 0 inductor acts as a source supplying total energy of $\frac{1}{2} L i^2$

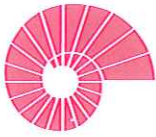When a steady current flows through an inductor, no energy flows into or out from the inductor.



Energy stored in the inductor can be viewed as stored in the magnetic field.

→ Consider the ideal toroidal solenoid

$$L = \frac{\mu_0 N^2 A}{2\pi r}$$

$$\Rightarrow U = \frac{1}{2} L i^2 = \frac{1}{2} \frac{\mu_0 N^2 A}{2\pi r} i^2$$

This energy is localized in a volume of $2\pi r A$

$$\Rightarrow \text{energy density } u = \frac{U}{2\pi r A} = \frac{1}{2} \mu_0 \frac{N^2 i^2}{(2\pi r)^2}$$

$$B = \frac{\mu_0 N i}{2\pi r} \text{ inside the toroid } \Rightarrow \frac{N^2 i^2}{(2\pi r)^2} = \frac{B^2}{\mu_0^2}$$

$$\Rightarrow \boxed{u = \frac{B^2}{2\mu_0}} \quad \text{Magnetic energy density in vacuum}$$


This is in general true. For a material with magnetic permeability μ , the energy density is:

$$u = \frac{B^2}{2\mu}$$



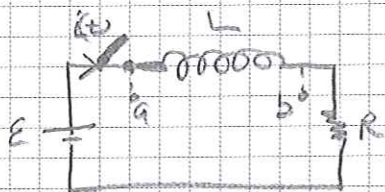30.4 RL Circuit:

A circuit that includes a resistor and an inductor.



What is $i(t)$?

At $t=0$ current ^{should remain} continuous
 $i(0) = 0$

$$E = V_{ab} + V_{bc} \quad \text{"Kirchoff's Loop Rule"}$$


$$E = L \frac{di}{dt} + iR \quad \text{First order DE.}$$

$$\Rightarrow \frac{E}{L} - \frac{iR}{L} = \frac{di}{dt}$$

$$\Rightarrow \int \frac{di}{E - iR} = \int \frac{dt}{L} \Rightarrow -\frac{1}{R} \ln(E - iR) \Big|_0^{i(t)} = \frac{t}{L}$$

$$\Rightarrow \ln\left(\frac{E - i(t)R}{E}\right) = -\frac{R}{L}t$$
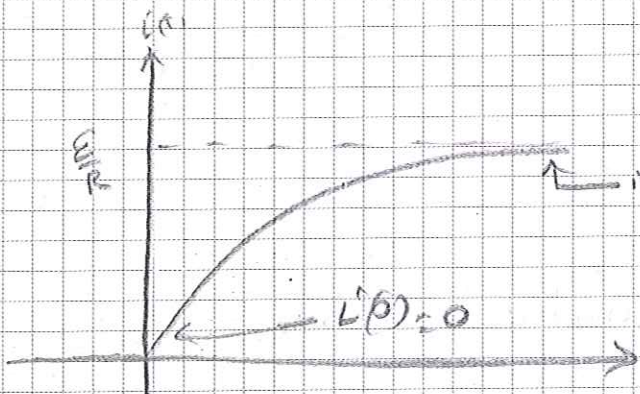
$$\Rightarrow 1 - i(t) \frac{R}{E} = e^{-\frac{R}{L}t} \Rightarrow i(t) = \frac{E}{R} \left(1 - e^{-\frac{R}{L}t}\right)$$




inductor behaves like a short circuit

The time constant is

$$\tau = \frac{L}{R}$$



Energy wise:

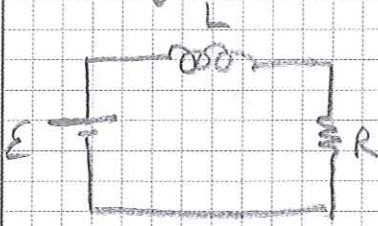


$$\begin{aligned}
 & i^2 R + L i \frac{di}{dt} = \\
 & = \frac{E^2}{R} (1 - e^{-\frac{R}{L}t})^2 + \cancel{L} \frac{E}{R} (1 - e^{-\frac{R}{L}t}) \frac{E}{R} \frac{R}{L} e^{-\frac{R}{L}t} \\
 & = \frac{E^2}{R} \left(1 - 2e^{-\frac{R}{L}t} + e^{-\frac{2R}{L}t} + e^{-\frac{2R}{L}t} - e^{-\frac{2R}{L}t} \right) \\
 & = \frac{E^2}{R} (1 - e^{-\frac{R}{L}t}) = \underline{\underline{E i}}
 \end{aligned}$$

$\Rightarrow \underbrace{E i}_{\substack{\text{power supplied} \\ \text{by the battery}}} = \underbrace{i^2 R}_{\substack{\text{power} \\ \text{dissipated} \\ \text{in } R}} + \underbrace{L i \frac{di}{dt}}_{\substack{\text{power stored} \\ \text{in } L}}$



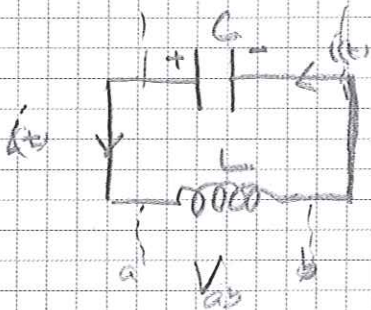30.5 L - C Circuit:

A circuit containing an ^{ideal} inductor and capacitor.



There is no energy dissipating component in the circuit so the energy will be oscillating between the capacitor and inductor.

$$V_C = V_{ab} \Rightarrow \frac{Q}{C} = L \frac{di}{dt}$$

$$i(t) = -\frac{dQ}{dt} \Rightarrow \frac{Q}{C} = -L \frac{d^2Q}{dt^2} \Rightarrow \boxed{\frac{d^2Q}{dt^2} = -\frac{1}{LC} Q}$$

solution: $Q(t) = A \cos\left(\frac{1}{\sqrt{LC}} t\right) + B \sin\left(\frac{1}{\sqrt{LC}} t\right)$

A, B are constants which depend on the initial conditions. For example if the initial conditions are: $Q(0) = Q_0$, $i(0) = 0$

$$\Rightarrow Q(0) = A = Q_0$$

$$i(0) = -\left. \frac{dQ}{dt} \right|_{t=0} = -\left\{ \frac{1}{\sqrt{LC}} B \right\} = 0 \Rightarrow B = 0$$


$$\Rightarrow \boxed{Q(t) = Q_0 \cos\left(\frac{1}{\sqrt{LC}} t\right)}$$

$\omega = \frac{1}{\sqrt{LC}}$, angular frequency of oscillations

Power stored in L: $\frac{1}{2} L i^2 = \frac{1}{2} L \frac{Q_0^2}{LC} \sin^2\left(\frac{1}{\sqrt{LC}} t\right) = \frac{1}{2} \frac{Q_0^2}{C} \sin^2\left(\frac{1}{\sqrt{LC}} t\right)$

Power stored in C: $\frac{1}{2} C Q^2 = \frac{1}{2} \frac{Q_0^2}{C} \cos^2\left(\frac{1}{\sqrt{LC}} t\right)$

$$\Rightarrow \boxed{P_L + P_C = \frac{1}{2} \frac{Q_0^2}{C} = \text{constant}}$$

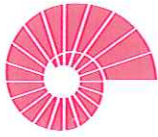

Ex 30.9: A 300V dc power is used to charge a $27\mu\text{F}$ capacitor. After the capacitor is fully charged, it is disconnected from the power supply, and connected across a 10mH inductor.

- Frequency and period of oscillations?
- Capacitor charge and the circuit current 1.2ms after the inductor and capacitor are connected?

$$a) \omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10 \times 10^{-3} \times 27 \times 10^{-6}}} = 2.0 \times 10^3 \text{ rad/s}$$

$$\Rightarrow f = \frac{\omega}{2\pi} = 320 \text{ Hz}$$

$$T = \frac{1}{f} = 3.1 \text{ ms}$$


$$b) Q_0 = C.V = 27 \times 10^{-6} \times 300 = 81 \times 10^{-4} \text{ C}$$

$$\begin{aligned} \Rightarrow Q(t) &= Q_0 \cos(\omega t) \Rightarrow Q(1.2\text{ms}) = 81 \times 10^{-4} \cos(2.0 \times 10^3 \times 1.2 \times 10^{-3}) \\ &= 81 \times 10^{-4} \cos(2.4) \\ &= -5.5 \times 10^{-3} \text{ C} \end{aligned}$$

$$\begin{aligned} i(t) &= -\frac{dQ}{dt} = Q_0 \omega \sin \omega t \Rightarrow i(1.2\text{ms}) = 81 \times 10^{-4} \times 2 \times 10^3 \sin(2.4) \\ &= 10 \text{ A} \end{aligned}$$



30.6. R-L-C Circuit

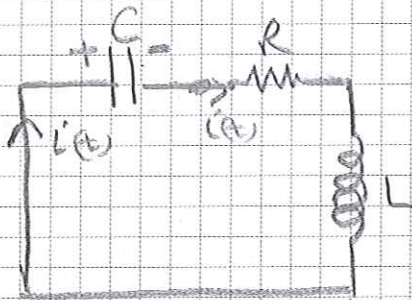

This time there is an energy dissipating term in the circuit. So, the initial energy stored in the C (or L) will reach to 0 at large times.

$$V_C + iR = -V_L \Rightarrow \frac{Q}{C} + iR = -L \frac{di}{dt}$$

$$i = \frac{dQ}{dt} \Rightarrow L \frac{d^2Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = 0$$

$$\Rightarrow \frac{d^2Q}{dt^2} + \frac{R}{L} \frac{dQ}{dt} + \frac{Q}{LC} = 0, \quad 2^{\text{nd}} \text{ order differential equation}$$


We try solutions of the form:

$$Q(t) = Ae^{kt} \Rightarrow k^2 + \frac{R}{L}k + \frac{1}{LC} = 0 \quad k_1, k_2$$


$$\Rightarrow k = \frac{-\frac{R}{L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - \frac{4}{LC}}}{2} = \frac{-R}{2L} \pm \frac{1}{2} \sqrt{\frac{R^2}{L^2} - \frac{4}{LC}}$$

$$\Rightarrow \text{General solution: } Q(t) = Ae^{k_1 t} + Be^{k_2 t}$$
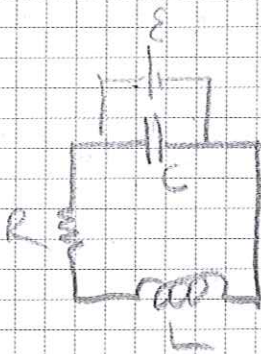
$$Q(t) = e^{-\frac{R}{2L}t} \left\{ A e^{\frac{1}{2} \sqrt{\frac{R^2}{L^2} - \frac{4}{LC}} t} + B e^{-\frac{1}{2} \sqrt{\frac{R^2}{L^2} - \frac{4}{LC}} t} \right\}$$



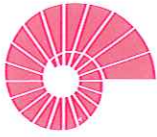In the circuit we first charge the capacitor using a battery. Then we disconnect the battery from the circuit.



$$Q(t) = e^{-\frac{R}{2L}t} \left\{ A e^{\frac{1}{2}\sqrt{\frac{R^2}{L^2} - \frac{4}{LC}}t} + B e^{-\frac{1}{2}\sqrt{\frac{R^2}{L^2} - \frac{4}{LC}}t} \right\}$$

There are 3 regimes of operation depending on the values of R, L, C .

(i) $\frac{R^2}{L^2} = \frac{4}{LC} \Rightarrow Q(t) = A e^{-\frac{R}{2L}t}$, critically damped case


(ii) $\frac{R^2}{L^2} > \frac{4}{LC} \Rightarrow$ overdamped case

(iii) $\frac{R^2}{L^2} < \frac{4}{LC} \Rightarrow$ under damped case

$$Q(t) = e^{-\frac{R}{2L}t} \left\{ A e^{\frac{1}{2}\sqrt{\frac{4}{LC} - \frac{R^2}{L^2}}t} + B e^{-\frac{1}{2}\sqrt{\frac{4}{LC} - \frac{R^2}{L^2}}t} \right\}$$

oscillations

$$Q(t) = A e^{-\frac{R}{2L}t} \cos\left(\sqrt{\frac{4}{LC} - \frac{R^2}{L^2}}t + \phi\right)$$

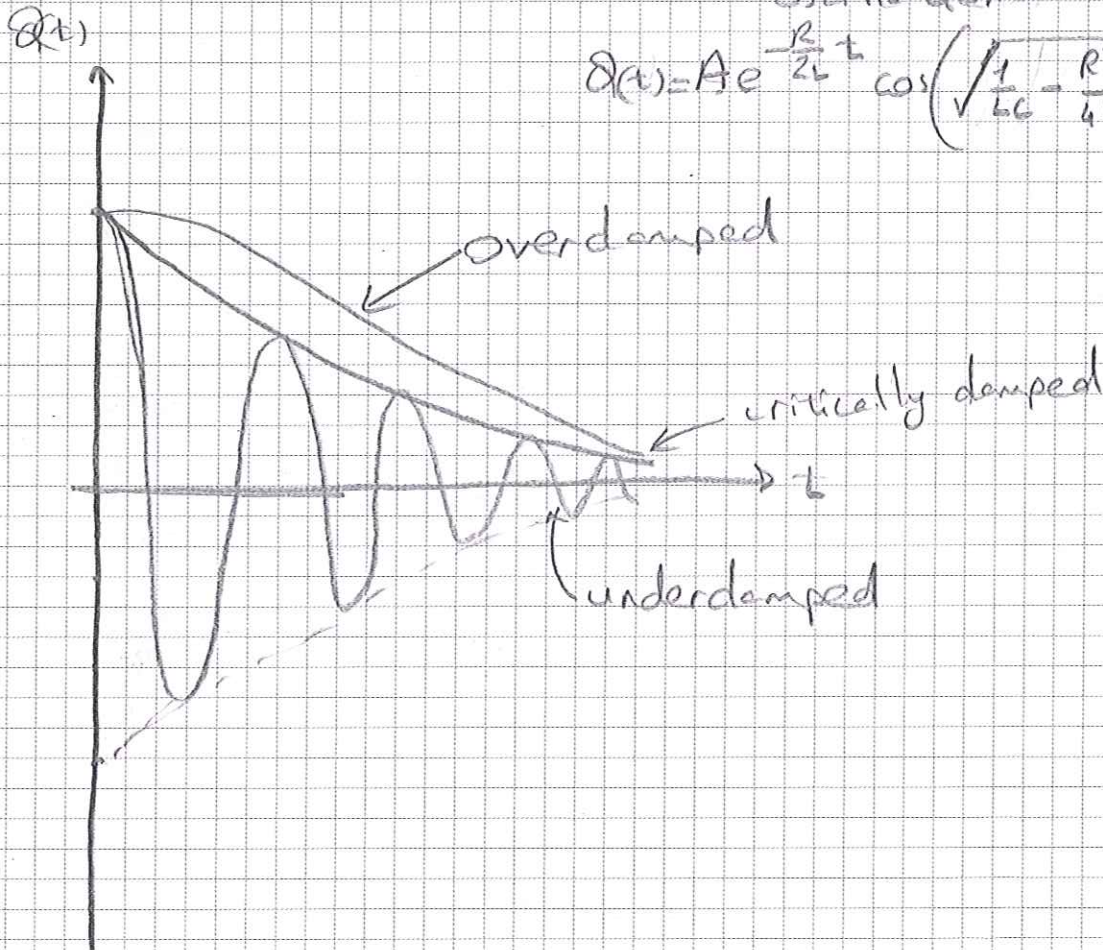



Ex 30.11: What is the R value required to give an R-L-C circuit a frequency that is $\frac{1}{2}$ of the undamped freq.?

Underdamped frequency

$$\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$


Undamped frequency, R=0

$$\sqrt{\frac{1}{LC}}$$

$$\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} = \frac{1}{2} \sqrt{\frac{1}{LC}} \Rightarrow \frac{1}{LC} - \frac{R^2}{4L^2} = \frac{1}{4} \frac{1}{LC}$$

$$\Rightarrow \frac{R^2}{4L^2} = \frac{3}{4} \frac{1}{LC} \Rightarrow R^2 = 3 \frac{L}{C} \Rightarrow R = \sqrt{\frac{3L}{C}}$$

Prob. 30.73:

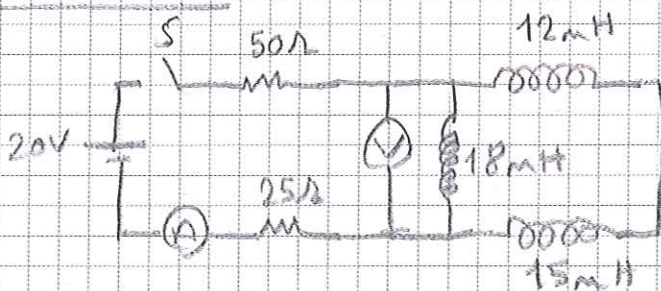


S has been open for a long time. S is suddenly closed.

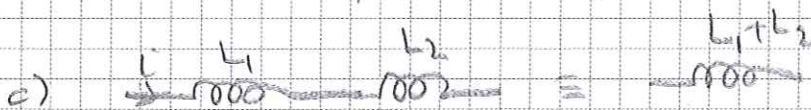
- a) What are the readings in A and V just after the switch is closed?
 - b) What " " " " after a long time?
 - c) " " " " at $t = 0,115 \text{ ms}$?
- b) As $t \rightarrow \infty$ all inductors behave like short circuits.

$$\Rightarrow V = 0, \quad A = \frac{20V}{75\Omega}$$

$$c) \text{ At } t=0 \quad A=0, \quad V=20V$$



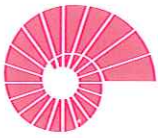
$$V = L_1 \frac{di_1}{dt} = L_2 \frac{di_2}{dt} = L_{eq} \frac{d(i_1 + i_2)}{dt}$$



$$\Rightarrow L_{eq} \left(\frac{V}{L_1} + \frac{V}{L_2} \right) = V \Rightarrow \frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} //$$

\rightarrow

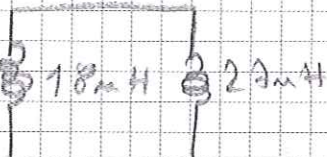
$$\frac{1}{L_{eq}} = \frac{1}{18} + \frac{1}{27} = \frac{5}{54} \Rightarrow L_{eq} = \frac{54}{5} \text{ mH} //$$


\rightarrow R-L circuit


$$V(t) = \frac{20}{75} \left(1 - e^{-\frac{75}{54 \times 10^{-3}} t} \right) //$$

$$V(t) = \left(\frac{54 \times 10^{-3}}{5} \right) \frac{di}{dt} //$$



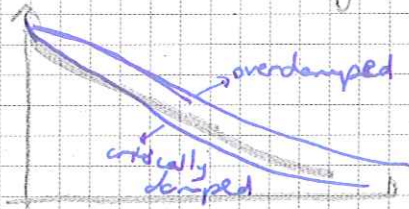When $R^2 = \frac{4L}{C}$, the system no longer oscillates.
↳ critically damped case.



When $R^2 > \frac{4L}{C}$, → overdamped. Capacitor charge approaches 0 even more slowly.

Ex: What resistance R is required to give an L-R-C circuit an oscillation frequency that is $\frac{1}{2}$ the undamped frequency.

undamped frequency: $\sqrt{\frac{1}{LC}}$

$$\frac{1}{2} \sqrt{\frac{1}{LC}} = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} \Rightarrow R = \frac{3L}{C}$$

Chap 31 : Alternating Current


Circuits in which voltages and currents vary sinusoidally are called as alternating current circuits.

Phasors and Alternating Currents


A sinusoidal voltage is described as:
 $v = V \cos \omega t$

"Most present day household and industrial power-distribution systems operate with alt. current."
"In Turkey $f = 50Hz$ "

A sinusoidal current is described as:

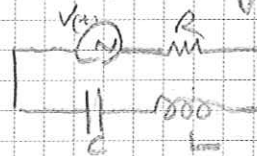

$i = I \cos \omega t$

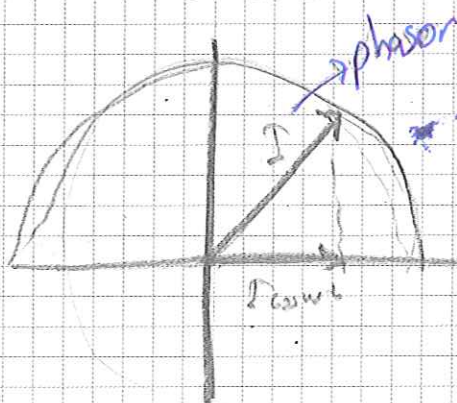

We use phasor diagrams to represent sinusoidally varying voltages and currents.
→ The instantaneous value of a quantity that varies sinusoidally with time is represented by the projection onto a horizontal axis of a vector with a length I.

"Phasor is the vector in 2D whose projection to the horizontal axis gives the instantaneous value of the variable."