

Closed book. No calculators are to be used for this quiz.  
Quiz duration: 10 minutes


Name:

Student ID:

Signature:

Two inductors ( $L_1 = L$ ,  $L_2 = L/2$ ) in series with zero current are connected through a switch to a capacitor with initial charge  $Q$  and the switch is closed at  $t = 0$ . Calculate the maximum voltage occurring across the inductor  $L_1$ .

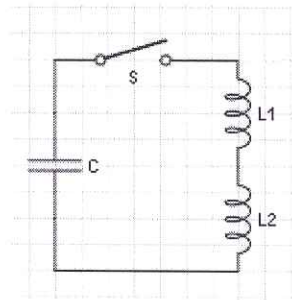(Hint: First find the equivalent inductance of two inductors in series. Then, for a simple LC circuit (one inductor – one capacitor)  $-L \frac{di}{dt} - \frac{q}{C} = 0$  and  $q = Q \cos(\omega t + \phi)$ . In this problem, take  $\phi = 0$ )



$$L_{eq} = L_1 + L_2 = L + \frac{L}{2} = \frac{3L}{2}$$

$$-L_{eq} \frac{di}{dt} = \frac{q}{C} = V = V_{L1} + V_{L2}$$

$$-\frac{3L}{2} \frac{di}{dt} = \frac{Q \cos(\omega t)}{C}$$

$$V_{L1} = -L \frac{di}{dt} = \frac{2Q \cos(\omega t)}{3C}$$

Maximum value cosine can take is 1. Therefore:

$$(V_{L1})_{max} = \frac{2Q}{3C}$$


Closed book. No calculators are to be used for this quiz.  
Quiz duration: 10 minutes

Name: *Vahdet Ünal*

Student ID:

Signature:

An inductor with initial current  $I$  (indicated by the arrow) is connected through a switch to two capacitors in series with zero initial charge and the switch is closed at  $t = 0$ . Calculate the maximum voltage across the capacitor with capacitance  $2C$ .  
(Hint: For a simple LC circuit (one inductor - one capacitor)  $-L \frac{di}{dt} - \frac{q}{C} = 0$  and  $q = Q \cos(\omega t + \varphi)$ . Be careful about the value of  $\varphi$  you have use in this problem)

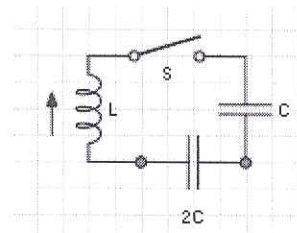

We need to find  $\varphi$  and  $Q$  using initial conditions.

$$q(t=0) = 0 = Q \cos(\varphi) \Rightarrow \varphi = \pi/2$$

$$i = \frac{dq}{dt} = -Q\omega \sin(\omega t + \pi/2)$$

$$i(t=0) = I = -Q\omega \sin(\pi/2) \Rightarrow Q = -\frac{I}{\omega}$$

Now we can find the voltage across capacitors.

$$V = \frac{q}{C_{eq}} = \frac{-\frac{I}{\omega} \cos(\omega t + \pi/2)}{\frac{2C}{3}} = -\frac{3I \cos(\omega t + \pi/2)}{2\omega C}$$

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2} = \frac{2C^2}{3C} = \frac{2C}{3}$$

$$V = V_1 + V_2 = \frac{q_1}{C} + \frac{q_2}{2C}$$

$q_1 = q_2$  since capacitors are connected in series.

$$V = \frac{q_2}{C} + \frac{q_2}{2C} = 2V_2 + V_2 = 3V_2 \Rightarrow V_2 = \frac{V}{3} = -\frac{I \cos(\omega t + \pi/2)}{2\omega C}$$

$V_{2max} = \frac{I}{2\omega C}$ . Solution is not over yet. We need to find  $\omega$  too.

$$\omega = \frac{1}{\sqrt{LC_{eq}}} = \frac{1}{\sqrt{L \frac{2C}{3}}} = \sqrt{\frac{3}{2LC}}$$

$$V_{2max} = \frac{I}{2\sqrt{\frac{3}{2LC}} C} = \frac{I}{\sqrt{\frac{6C}{L}}} = I \sqrt{\frac{L}{6C}}$$



Closed book. No calculators are to be used for this quiz.  
Quiz duration: 10 minutes

Name:

Student ID:

Signature:

Two inductors ( $L_1 = L$ ,  $L_2 = L/2$ ) in parallel with zero current are connected through a switch to a capacitor with initial charge  $Q$  and the switch is closed at  $t = 0$ . Calculate the maximum current occurring across the inductor  $L_1$ .  
(Hint: First find the equivalent inductance of two inductors in parallel. Then, for a simple LC circuit (one inductor – one capacitor)  $-L \frac{di}{dt} - \frac{q}{c} = 0$  and  $q = Q \cos(\omega t + \varphi)$ . In this problem, take  $\varphi = 0$ )

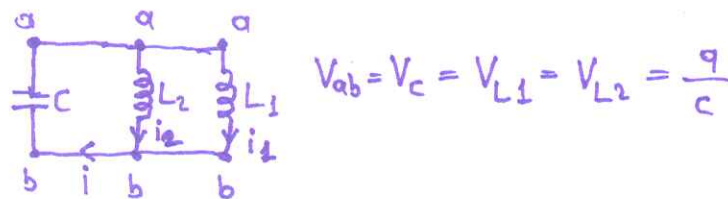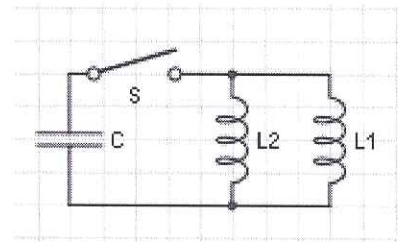

$$V_{L1} = -L_1 \frac{di_1}{dt} = \frac{q}{c}$$

$$V_{L1} = -L \frac{di_1}{dt} = \frac{Q \cos(\omega t)}{c} \Rightarrow \frac{di_1}{dt} = -\frac{Q \cos(\omega t)}{LC}$$

$$\int di_1 = -\frac{Q}{LC} \int \cos(\omega t) dt \Rightarrow i_1 = -\frac{Q}{LC\omega} \sin(\omega t) + \text{const.}$$

Integration constant should be 0 since  $i_1(t=0) = 0$ .

$$(i_1)_{\max} = \frac{Q}{LC\omega} \quad \text{since maximum value for } -\sin(\omega t) \text{ is } 1.$$

$$\omega = \frac{1}{\sqrt{L_{\text{eq}} C}} = \frac{1}{\sqrt{\left(\frac{1}{L_1} + \frac{1}{L_2}\right)^{-1} C}} = \frac{1}{\sqrt{\frac{LC}{3}}} = \sqrt{\frac{3}{LC}}$$

$$(i_1)_{\max} = \frac{Q}{LC \sqrt{\frac{3}{LC}}} = \frac{Q}{\sqrt{3LC}}$$