


Closed book. No calculators are to be used for this quiz.
Quiz duration: 10 minutes


Name:

Student ID:

Signature:

In the circuit shown below, find the current i using Kirchoff's Rules.

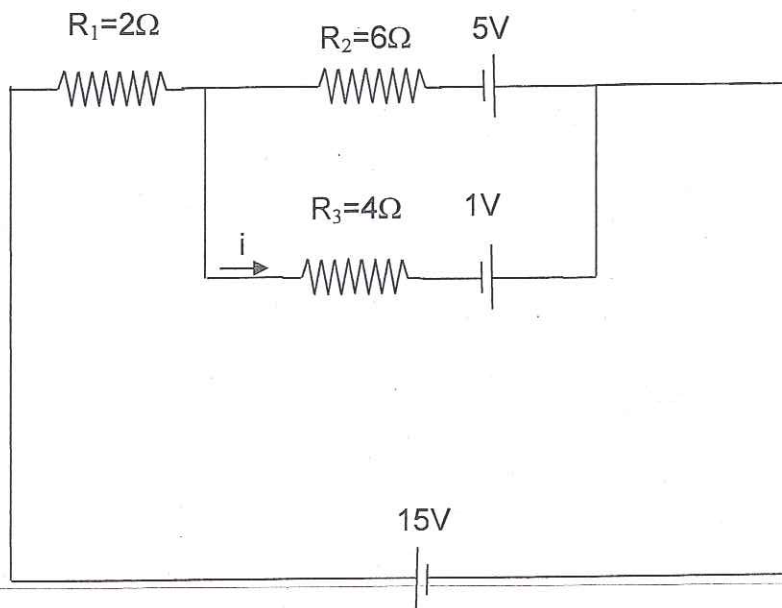

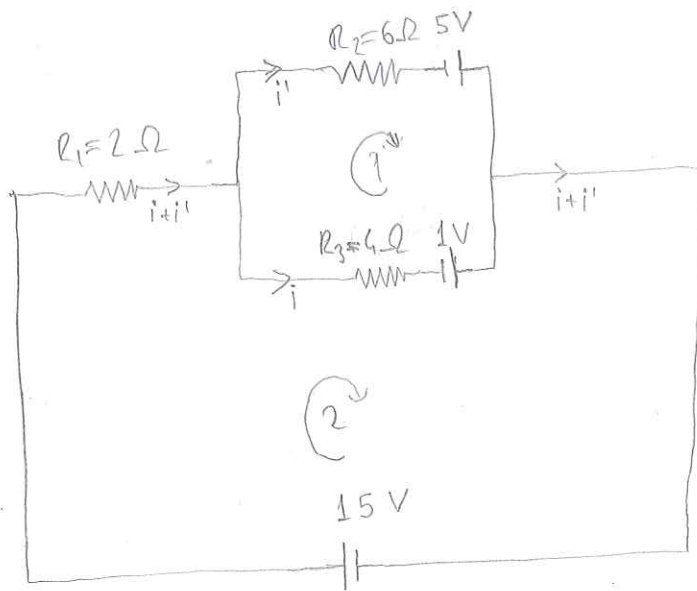

Loop 1:

$$-(6\Omega)i' + 5V - 1V + i(4\Omega) = 0$$

$$4i - 6i' = -4A \quad (1)$$

Loop 2:

$$15V - (i+i')2\Omega - i(4\Omega) + 1V = 0$$

$$6i + 2i' = 16A \quad (2)$$

Using (1) and (2)

$$4i - 6i' = -4A$$

$$18i + 6i' = 48A \quad +$$

$$22i + 0 = 44A$$

$$i = 2A$$


Closed book. No calculators are to be used for this quiz.
Quiz duration: 10 minutes


Name:

Student ID:

Signature:

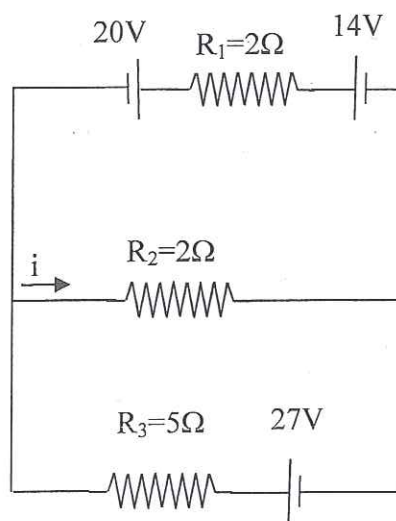In the circuit shown below, find the current i using Kirchoff's Rules.



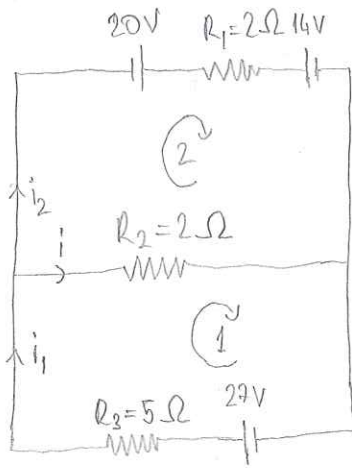

$$-i + i_1 - i_2 = 0 \quad (1)$$

Loop 1:

$$27V - i_1(5\Omega) - i(2\Omega) = 0$$

$$i_1 = \frac{27}{5}A - \frac{2}{5}i \quad (2)$$

Loop 2:

$$20V - i_2(2\Omega) - 14V + i(2\Omega) = 0$$

$$i_2 = 3A + i \quad (3)$$

Replacing (2) and (3) in (1):

$$-i + \frac{27}{5}A - \frac{2}{5}i - 3A + i = 0$$

$$\frac{12}{5}i = \frac{27}{5}A - 3A$$

$$12i = 27A - 15A \quad \cdot 6$$

$$i = 1A$$


Closed book. No calculators are to be used for this quiz.
Quiz duration: 10 minutes


Name:

Student ID:

Signature:

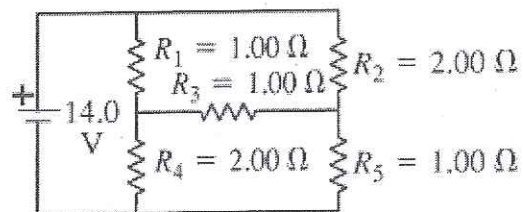- Find the current through the battery and each resistor in the circuit shown below.
- What is the equivalent resistance of the resistor network?



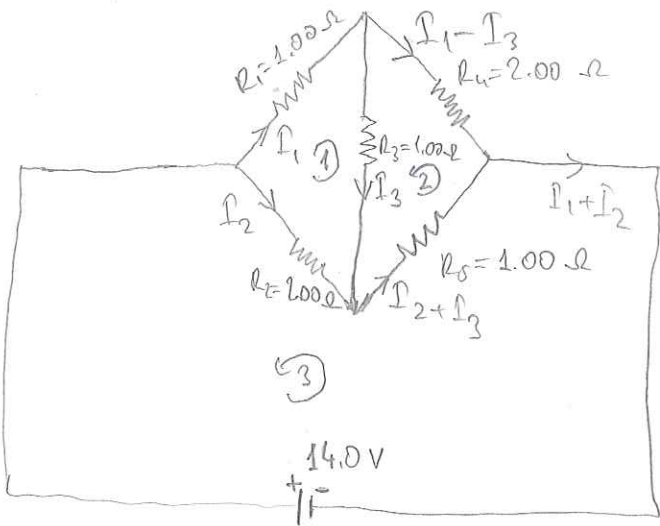

a) Loop 1:

$$I_1(1.00\ \Omega) - I_2(2.00\ \Omega) + I_3(1.00\ \Omega) = 0$$

$$I_1 - 2I_2 + I_3 = 0 \quad (1)$$

Loop 2:

$$-I_3(1.00\ \Omega) - (I_2 + I_3)(1.00\ \Omega) + (I_1 - I_3)(2.00\ \Omega) = 0$$

$$2I_1 - I_2 - 4I_3 = 0 \quad (2)$$

Loop 3:

$$-14.0\text{V} + (I_2 + I_3)(1.00\ \Omega) + I_2(2.00\ \Omega) = 0$$

$$3I_2 + I_3 = 14.0\text{A}$$

$$I_3 = 14.0\text{A} - 3I_2 \quad (3)$$

Replacing (3) inside (1) and (2) we get:

$$-2I_1 + 14.0\text{A} - 5I_2 = 0 \quad (4)$$

$$2I_1 - 56.0\text{A} + 11I_2 = 0 \quad (5)$$

$$0 - 84.0\text{A} + 24I_2 = 0$$

$$I_2 = 4.0\text{A}$$

From (3)

$$I_3 = 14.0 \text{ A} - 3 \times (4.0 \text{ A}) = 2.0 \text{ A}$$

From (2)

$$2I_1 - 4.0 \text{ A} - 4 \times (2.0 \text{ A}) = 0$$

$$I_1 = 6.0 \text{ A}$$

$$I_{R1} = I_1 = 6.0 \text{ A}$$

$$I_{R2} = I_2 = 4.0 \text{ A}$$

$$I_{R3} = I_3 = 2.0 \text{ A}$$

$$I_{R4} = I_1 - I_3 = 4.0 \text{ A}$$

$$I_{R5} = I_2 + I_3 = 6.0 \text{ A}$$

$$I_{\text{battery}} = I_1 + I_2 = 10.0 \text{ A}$$

$$b.) R_{\text{eq}} = \frac{V_{\text{battery}}}{I_{\text{battery}}} = \frac{14.0 \text{ V}}{10.0 \text{ A}} = 1.40 \ \Omega$$