

<b>Name:</b>	<b>Signature:</b>
<b>Surname:</b>	<b>Number:</b>

**KOÇ UNIVERSITY**  
**College of Sciences**  
**PHYS 102 General Physics 2**  
**Spring Semester 2017**  
**Final Exam**

**May 24, 2017      Wednesday, 08:30-10:10**

**Please read.**


- Count to make sure that there are 5 pages in this question booklet
- Check your **name, number, on front page, and student ID on each page.**
- This examination is conducted with closed books and notes.
- Put all your personal belongings underneath your seat and make sure that pages of books or notebooks are not open.
- Absolutely no talking or exchanging anything (like rulers, erasers) during the exam.
- You must show all your work to get credit; you will not be given any points unless you show the details of your work (this applies even if your final answer is correct).
- Write neatly and clearly; unreadable answers will not be given any credit.
- If you need more writing space, use the backs of the question pages and put down the appropriate pointer marks.
- Make sure that you include units in your results.
- Make sure that you label the axis and have units in your plots.
- You are not allowed to use calculators during this exam.
- Turn off your mobile phones, and put away.
- You are not allowed to leave the class during the first 15 minutes, and last 15 minutes.
- Answer the following questions. Show your calculations. Unjustified answers will not be given any score. Write your answers in the boxes.

**P102\_Index:**

1	2	3	4	Total

<b>ExamRoom:</b>	<b>P101_Index:</b>
<b>Student ID Number:</b>	<b>Signature:</b>

1- (25 Points) A conducting bar of length  $L$ , mass  $M$  and electrical resistance  $R$  can slide down a long conducting frame without friction. The frame is inclined by angle  $\theta$  from the horizontal and has no electrical resistance. The whole system is in a constant downward magnetic field  $\vec{B} = -B_0\hat{j}$ , and there is also the gravitational field  $-g\hat{j}$ . The bar starts sliding down.

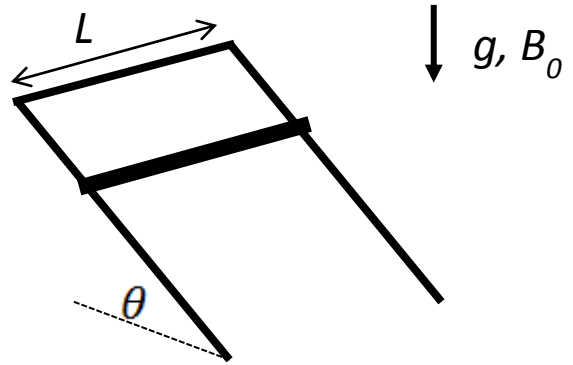

a) What is the magnitude of the EMF induced in the closed circuit at the moment when the bar has speed  $v$ ?

b) What is the magnetic force on the bar at the moment when the bar has speed  $v$ ?

c) What is the maximal speed the bar can reach?

<b>ExamRoom:</b>	<b>P101_Index:</b>
<b>Student ID Number:</b>	<b>Signature:</b>

**2-(25 Points)**

*Unjustified answers will not be given any score. Write your answers in the boxes; answers outside the boxes will not be given any score.*

Consider an RL-series circuit, with  $L = 200 \text{ mH}$  and  $R = 100 \text{ m}\Omega$ , driven by a constant voltage source with  $V = 300 \text{ mV}$ . Assume initially there is no current in the circuit. Find

(take  $e = 3$ )

- (i) the time constant of the circuit,
- (ii) the current in the circuit after 2 seconds,
- (iii) the current in the circuit after very long time.

(i)
-----

(ii)
------

(iii)
-------

<b>ExamRoom:</b>	<b>P101_Index:</b>
<b>Student ID Number:</b>	<b>Signature:</b>

**3-(25 Points)**

*Unjustified answers will not be given any score. Write your answers in the boxes; answers outside the boxes will not be given any score.*

A capacitor is connected to an inductor to form an LC circuit. Initially the capacitor is uncharged and there is current in the circuit. After a while a measurement is performed which indicates that the charge on the capacitor is 4 C and the current in the circuit is 1 A. The period of LC oscillations is observed to be 24 s. Calculate (take  $\pi = 3$ )

- (i) the maximum charge on the capacitor;
- (ii) the earliest time when measurement is performed.

(i)
-----


(ii)
------

<b>ExamRoom:</b>	<b>P101_Index:</b>
<b>Student ID Number:</b>	<b>Signature:</b>

4- (25 Points) A resistor R and an inductor L are connected in series (as in the figure) to an AC current source which supplies a current

$$i(t) = I \cos(\omega t)$$

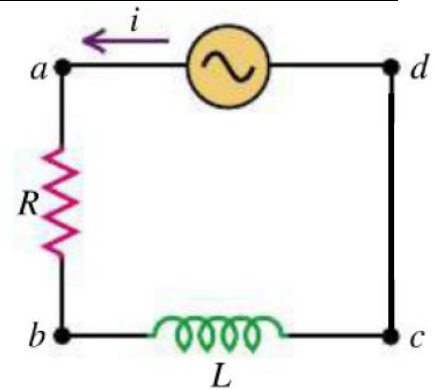(a) Draw the phasor diagram for the current  $i(t)$  and the voltages  $v_{ab}(t)$ ,  $v_{bc}(t)$ , and  $v_{ad}(t)$ .



(b) The source voltage  $v_{ad}$  can be expressed as:

$$v_{ad}(t) = V_s \cos(\omega t + \phi)$$

Calculate  $V_s$  and  $\phi$  in terms of  $I$ ,  $R$ ,  $L$ , and  $\omega$ .

(c) How much power is delivered by the AC source on average?