


Closed book. No calculators are to be used for this quiz.
Quiz duration: 10 minutes

Name: SOLUTION KEY

Student ID:


Signature:

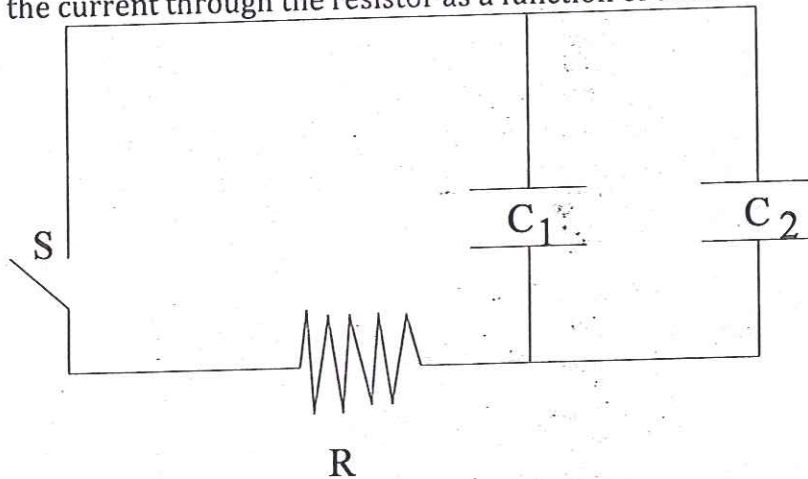Both capacitors are initially charged with Q and the switch S is closed at time $t = 0$. Find the current through the resistor as a function of time.



Discharging capacitor: $Q(t) = Q e^{-t/\tau}$

$$\tau = RC_{eq} = R(C_1 + C_2)$$

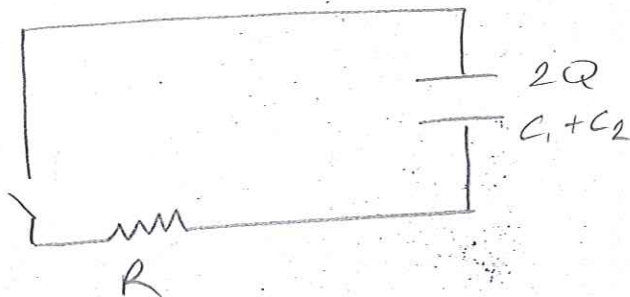

$$I(t) = \frac{dQ}{dt} = -Q \frac{1}{\tau} e^{-t/\tau}$$

$$I(t) = -2Q \frac{1}{R(C_1 + C_2)} e^{-t/R(C_1 + C_2)}$$

Section 1

Quiz 5

17 March 2016


Closed book. No calculators are to be used for this quiz.
Quiz duration: 10 minutes

Name: SOLUTION KEY

Student ID:

Signature:

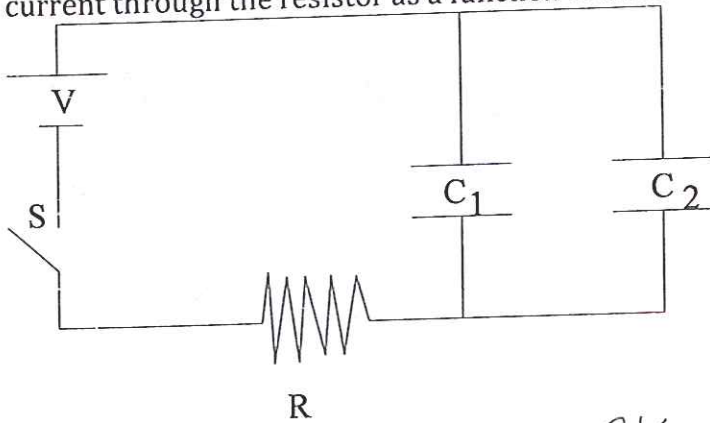The capacitors are initially uncharged and the switch S is closed at time $t = 0$. Find the current through the resistor as a function of time.




$$Q_{\max} = CV$$

Charging capacitor: $Q(t) = Q_{\max}(1 - e^{-t/\tau})$

$$\tau = R(C_1 + C_2)$$

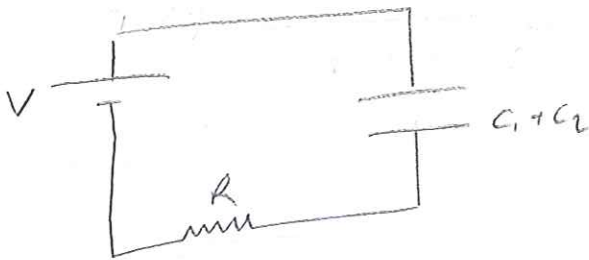
$$I(t) = \frac{dQ}{dt} = Q_{\max} \frac{1}{\tau} e^{-t/\tau}$$



$$I(t) = (C_1 + C_2)V \frac{1}{R(C_1 + C_2)} e^{-t/R(C_1 + C_2)}$$

Closed book. No calculators are to be used for this quiz.
Quiz duration: 10 minutes

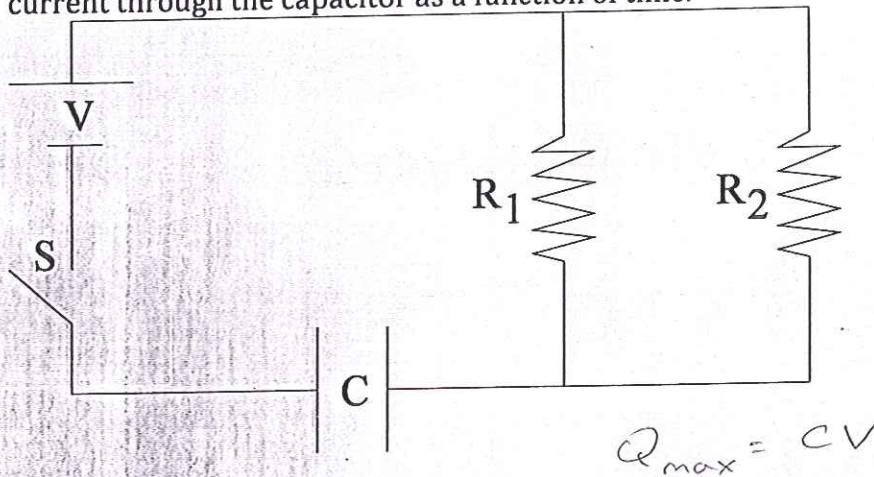Name: SOLUTION KEY Student ID: Signature:
The capacitor is initially uncharged and the switch S is closed at time $t = 0$. Find the current through the capacitor as a function of time.



Charging capacitor: $Q(t) = Q_{\max} (1 - e^{-t/\tau})$

$$\tau = \frac{R_1 R_2 C}{R_1 + R_2}$$

$$I(t) = \frac{dQ}{dt} = Q_{\max} \frac{1}{C} e^{-t/\tau}$$

$$I(t) = CV \frac{R_1 + R_2}{R_1 R_2 C} e^{-t / \left(\frac{R_1 R_2 C}{R_1 + R_2} \right)}$$


Closed book. No calculators are to be used for this quiz.

Quiz duration: 10 minutes

Name: SOLUTION KEY Student ID:

Signature:

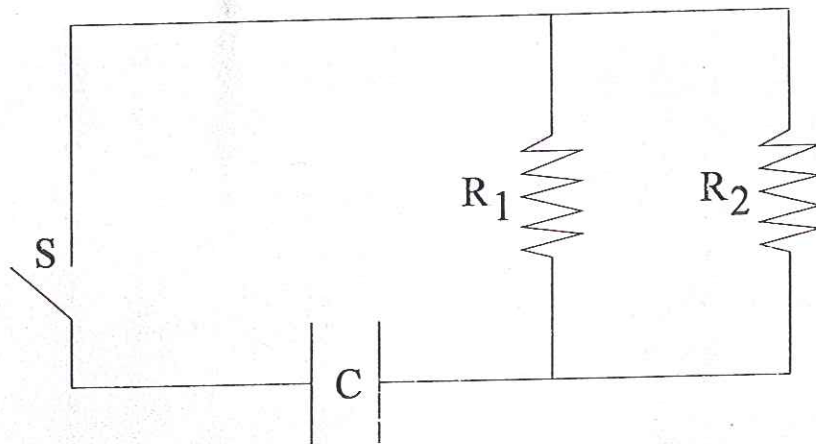The capacitor is initially charged with Q and the switch S is closed at time $t = 0$. Find the current through the capacitor as a function of time.



Discharging capacitor: $Q(t) = Q e^{-t/\tau}$

$$\tau = R_{eq} C = \frac{R_1 R_2 C}{R_1 + R_2}$$

$$I(t) = \frac{dQ}{dt} = Q \frac{-1}{\tau} e^{-t/\tau}$$

$$I(t) = -Q \left(\frac{R_1 + R_2}{R_1 R_2 C} \right) e^{-t/\frac{R_1 R_2 C}{R_1 + R_2}}$$